

# INTRODUCTION TO ELECTRONICS <sup>CSE-A</sup>

## ENGINEERING:


### ASSIGNMENT-1

1. Discuss the necessity and types of electronic filters used at the output of rectifiers:


Ans: The output of a rectifier contains d.c. component as well as a.c. component. Filters are used to minimise the undesirable a.c. i.e. ripple leaving only the d.c. component to appear at the output.

#### TYPES OF FILTERS:


1) Capacitor Filter →

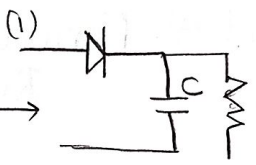


2) Inductor Filter →

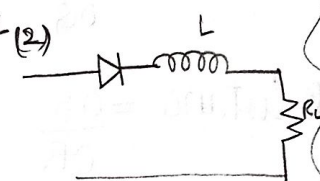

3) L- TYPE Filter →

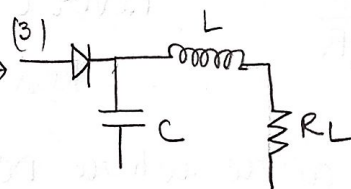


4)  $\pi$ - TYPE Filter

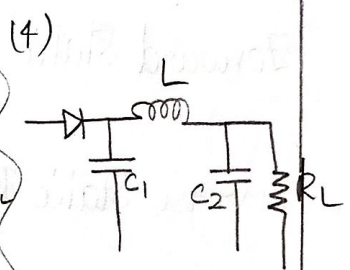


2. Explain the V-I characteristics of PN junction diode.

Ans:

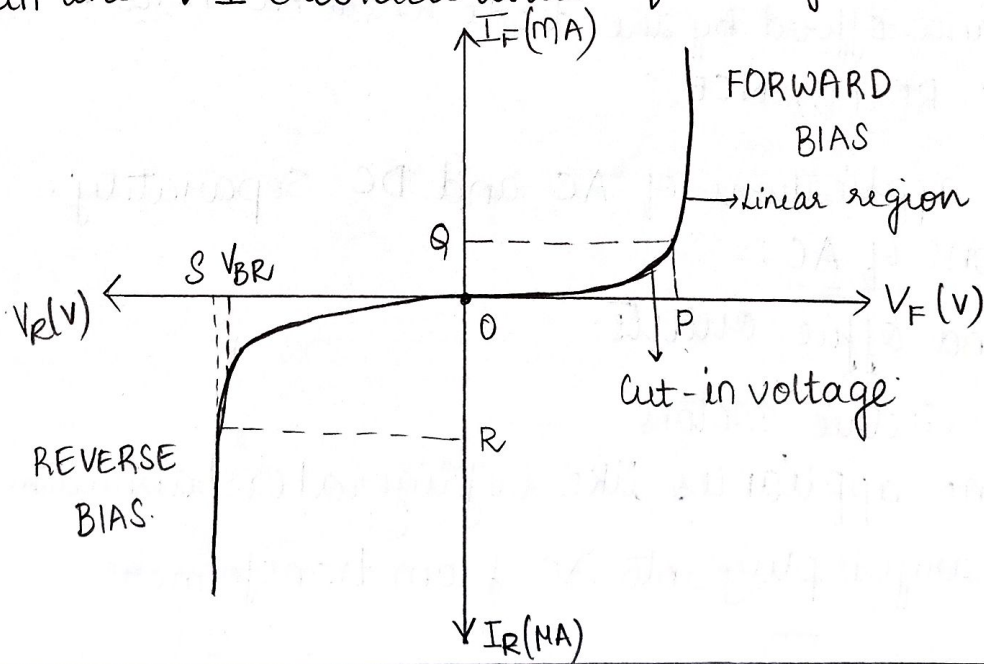

3. How do you find the static and dynamic resistances of a diode? Explain with the help of a graph?

Ans:

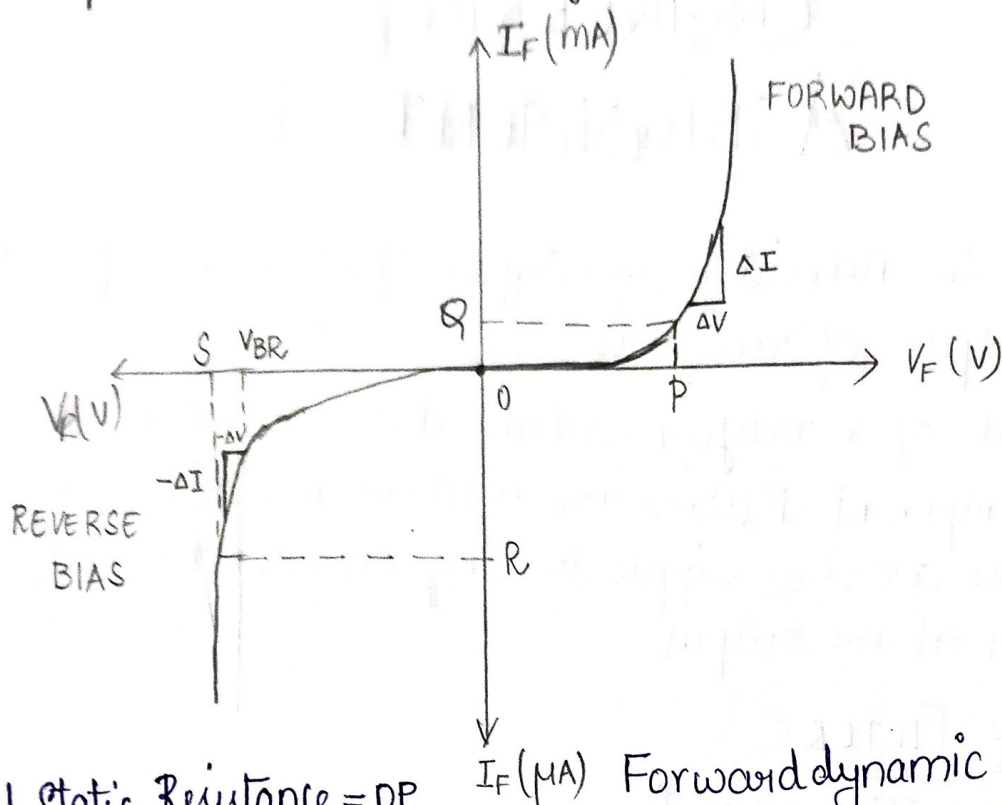

Forward Static Resistance =  $\frac{OP}{OQ}$

Forward dynamic Resistance =  $\frac{\Delta V}{\Delta I}$

Reverse Static Resistance =  $\frac{OS}{OR}$

Reverse dynamic Resistance =  $-\frac{\Delta V}{-\Delta I} = \frac{\Delta V}{\Delta I}$

- \* The resistance offered by the diode where DC flows is called STATIC RESISTANCE.
- \* The resistance offered by the diode where AC flows is called DYNAMIC RESISTANCE.

4. List the applications of AC and DC Separately.

Ans: Applications of AC:

- 1) Home and office outlets.
- 2) Powering electric motors.
- 3) Large home appliances like refrigerators, dishwashers, get AC current.
- 4) Mobile chargers plug into AC from transformers.

### Applications of DC:

- 1) Cell Phones; Flash lights.
- 2) Hybrid and electric vehicles.
- 3) Laptops; lifts finally gets DC as adapters convert AC to DC.

5: Determine the values of  $I_C$  and  $I_E$  for the transistor circuit of  $\beta = 200$  and  $I_B = 0.125 \text{ mA}$ .

Ans:

$$I_B = 0.125 \text{ mA}$$

$$\beta = 200$$

$$\beta = \frac{I_C}{I_B}$$

$$I_C = \beta \cdot I_B$$

$$= 200 \times 0.125 \text{ mA}$$

$$= 12.5 \times 10^{-3} \times 2$$

$$= 25.0 \times 10^{-3}$$

$$\boxed{I_C = 25 \text{ mA}}$$

$$I_E = I_C + I_B$$

$$= 25 \text{ mA} + 0.125 \text{ mA}$$

$$\boxed{I_E = 25.125 \text{ mA}}$$