

09/05/2022 LOGIC & SWITCHING THEORY

* Digital: works with electricity, numbers, Eg: Gadgets
Series of digits; works with zeroes & ones.

* Analog: physical appearance, some mechanism,
continuous wave, signals

⇒ use of ~~analog~~ digital over analog:

- digital: discretion of signal
- quality of signal: accurate
 - more cable | circuit design is simple
 - time / speed (processing)
 - loss of data is less \Rightarrow problem is solved by changing it to digits
 - Processing is easy

* Logic: Reasoning & Connecting the given things effectively

UNIT-1: Boolean Algebra

UNIT-1 & 2: Designing effectively / Minimization

UNIT-2: Components / Logic Gates

UNIT-3: Combinational Design

UNIT-4: Sequential Design (Memory element involved)

UNIT-5: Programmable logic Device

12/05/2022 * Purpose: To design digital circuits.

* Analog: Continuous data


* Digital: Discrete data

* Most of digital circuits take 5V (or) 12V.

for 5V $0-2V \rightarrow 0 \rightarrow \text{logic 0}$

$32-5V \rightarrow 1 \rightarrow \text{logic 1}$

* Digital Circuits:

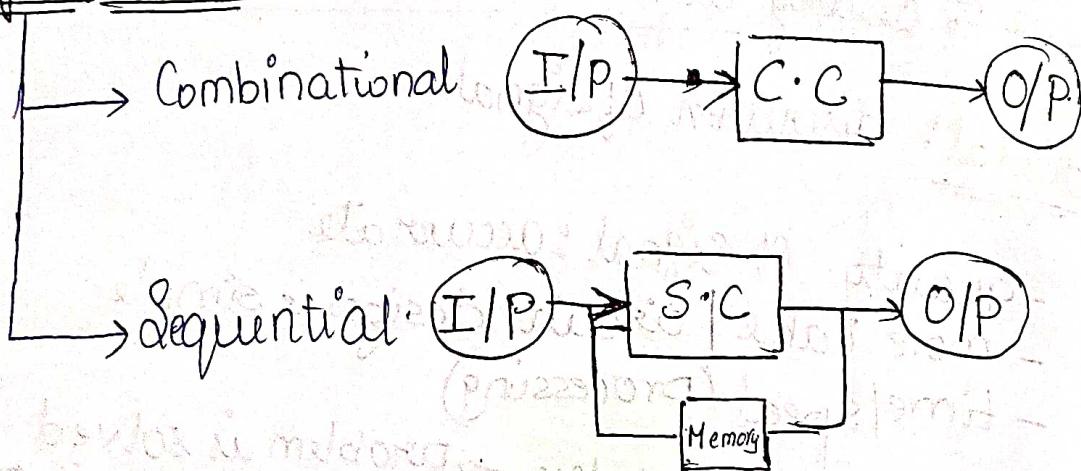

$$1) (63)_{10} = \cancel{100} (11111)_2$$

$$\begin{array}{r} 2 | 63 \\ 2 | 31 - 1 \\ 2 | 15 - 1 \\ 2 | 7 - 1 \end{array}$$

$$2 | 7$$

$$2) (111)_2 = 4 + 2 + 1 = (7)_{10} = 2 | 3 - 1$$

$$3) (63)_{10} = (77)_8$$

$$\begin{array}{r} 8 | 63 - 7 \\ 7 \end{array}$$

$$(3F)_{16}$$

$$16 | \frac{63 - 15}{3}$$

$$(77)_8 = 56 + 7 = 63.$$

$$\begin{array}{r} 5 | 13 \\ 63 \\ 48 \\ \hline 15 \end{array}$$

$$(3F)_{16} = 48 + 15 = 63$$

$$4) (1F4)_{16} = (500)_{10}$$

$$16^2 | 16$$

$$\begin{array}{r} 256 + 240 + 4 = 500. \\ 2041. \end{array}$$

$$5(193)_{10} = (\cancel{193})_{16} (C1)_{16} \cdot \begin{array}{r} 8 | 193 - 1 \\ 8 | 24 - 0 \\ \hline 3 | 16 | 193 - 1 \\ \hline 12 \end{array} \quad 24$$

$$(301)_8$$

13/05/2022

$$1) (1B2)_{16} = (\quad)_8$$

$$2) (765)_8 = (\quad)_{16}$$

$$2) (768)_8 = (\quad)_{16}$$

Not possible.

$$1) (1B2)_{16} = (434)_{10}$$

$$16^2 16^1 16^0$$

$$256 + 176 + 2$$

$$(434)_{10} = (662)_8$$

$$2) (765)_8 = (501)_{10}$$

$$8^2 8^1 8^0$$

$$(501)_{10} = (1F5)_{16}$$

$$\begin{array}{r} 16 | 434 - 2 & 434 \\ 16 | 27 & \frac{32}{414} \\ \hline 1 & \\ 8 | 434 - 2 & \frac{1}{414} \\ 8 | 54 - 6 & \frac{16}{\times 7} \\ \hline 6 & \frac{112}{\square} \end{array}$$

$$\begin{array}{r} 16 | 501 - 5 \\ 16 | 31 - 15 \\ \hline 1 & \end{array}$$

$$3) (110.011)_2 = (6.375)_{10}$$

$$2^2 2^1 2^0 \cdot 2^{-1} 2^{-2} 2^{-3}$$

$$4+2 \quad 0+0.25+0.125$$

30/05/2022

BOOLEAN ALGEBRA:

Properties:

1) $B = \{0, 1\}$

$$x, y, z \in B$$

x, y is closed under \cdot (or)

$\vdash \neg(\cdot)$ (and)

2) Commutative

Law:

$$x + y = y + x$$

$$x \cdot y = y \cdot x$$

3) Distributive Law: $x(y+z) = xy + xz$

$$x+yz = (x+y)(x+z).$$

4) $x \in B$

$$\exists x' \in B$$

} Unary Operator

5) $x + x' = 1 \in B$

$$x \cdot x' = 0 \in B$$

6) $x, y \in B$; then $x \neq y$


*

$\rightarrow \wedge$ - AND


$\rightarrow \vee$ - OR

$\rightarrow \neg$ - NOT

x	y	$x \cdot y$	$x+y$	x^y	y'
0	0	0	0	1	0
1	0	0	1	0	1
0	1	0	1	1	0
1	1	1	1	0	0

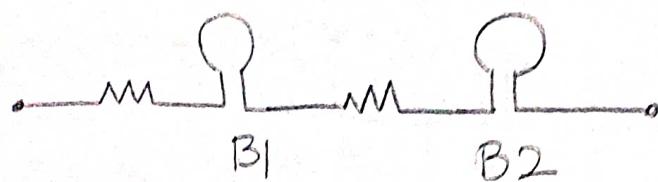

(and)

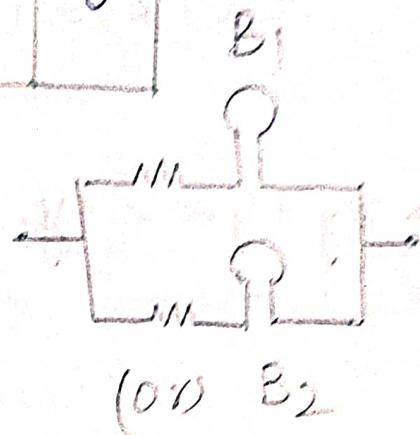

(or)

x	y	$x+y$	$y+x$	$x \cdot y$	$y \cdot x$	$x \cdot y \cdot z$	$x \cdot y \cdot z$
0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0
0	1	1	1	0	0	0	0
1	1	1	1	1	1	0	0

x	y	z	$y+z$	$x(y+z)$	$x \cdot y$	$y \cdot z$	$x \cdot y + y \cdot z$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	0	0	0	0	0	0	0
1	0	1	1	1	0	0	0
1	1	0	1	1	1	0	1

0	1	1	1	0	0	1	1
1	1	1	1	1	1	0	1


* Associative law:

$$\begin{aligned} x + (y + z) &= (x + y) + z & \left. \begin{array}{l} 1) x + x = x \\ 2) x \cdot x = x \\ 3) x + xy = xe \\ 4) x \cdot 1 = x \\ 5) xy + yx = xy \end{array} \right\} \\ x \cdot (y \cdot z) &= (x \cdot y) \cdot z \end{aligned}$$

* $xy + yx = xy$. $\because x + x = x$.

Proving - Postulates

- Using table

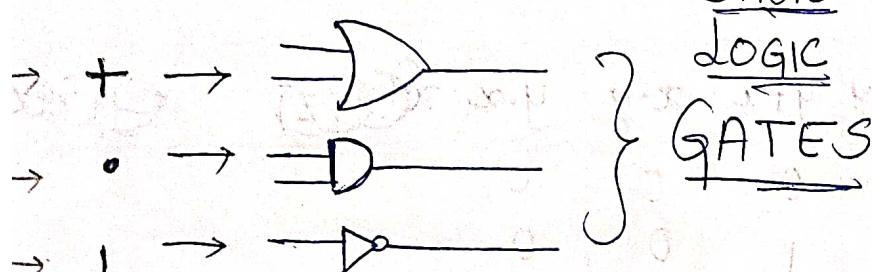

30/06/2022

$$x = 1 \quad x' = 0$$

$$x + x'y = x + y = 1$$

$$x = 0; y = 1; x' = 1$$

$$x + x'y = 1 = x + y$$

x	y	x'	$x'y$	$x+x'y$	$x+y$	0	1
0	0	1	0	0	0	0	0
0	1	1	0	1	1	0	1
1	0	0	0	1	1	0	0
1	1	0	0	1	1	1	1

$$\begin{aligned}
 &= x \cdot 1 + x'y \\
 &= x(1+y) + x'y \\
 &= x + xy + x'y \\
 &= x + y(1) \\
 &= \underline{\underline{x+y}}
 \end{aligned}$$

* $x'y'z + yz + xz$

$$x'y'z + yz \cdot 1 + xz \cdot 1$$

$$x'y'z + \underline{\underline{yz(x+y)}}$$

$$\begin{aligned}
 z[x'y' + x + y] &= z[x'(y') + x(1+y) \\
 &\quad + y(1+x)] \\
 &= z[x'y' + x + xy + y + xy]
 \end{aligned}$$

* $[x'y' + x + y]z$

$$z[x'y' + x + y] = z$$

x	y	$x + y$	$x + y + z$	$x(y + z) + x(y + z)$	$x'y'$	xy	yz	$x'y + x + y$	z
0	0	0	0	0	1	1	0	1	0
0	0	1	1	1	0	0	0	1	1
0	1	1	1	1	0	0	1	1	0
1	0	0	0	0	1	0	1	1	0
1	1	1	1	1	0	0	1	1	1
1	1	0	0	0	0	0	1	1	0
1	0	1	1	1	0	0	1	1	1
0	1	1	1	1	0	0	1	1	1

$$z[x'y' + x + y] \\ = z[x + y' + y] \\ = z[x + 1] = z.$$

$$* (x+y)[x'(y'+z')]' + x'y + x'z \\ (x+y)[x'y' + x'z']' + x'(y+z)$$

* De-Morgan's Theorem:

$$(x+y)' = x'y'$$

$$(xy)' = x'y'$$

$$(x+y)(x'y')' \cdot (x'z')' + x'(y+z)$$

$$(x+y)(x+y)(x+z) + x'(y+z)$$

$$(x+y)^2(x+z) + x'(y+z)$$

$$x(x+y)^2 + z(x+y)^2 + x'(y+z)$$

$$(x+y)^2(x+x'z) + x'y + x'z$$

$$* (x+y)[x'(xyz)']' + x'(y+z)$$

$$(x+y)(x+yz) + x'(y+z)$$

$$x + x'y + z + xy + x'y + x'z + yz$$

$$\begin{aligned}
 &= x + xy(1) + x'(y+z) + yz \\
 &= x + y(1) + x'z + yz \\
 &= x + y + x'z = \cancel{x} + \cancel{x'}z = \cancel{x} + \cancel{x'}(y+z) \\
 &= \cancel{x} + y + x'z + yz \\
 &= x + z + y(x'+z) \\
 &= x + x'y + zy + z \\
 &= x + y + yz + z \\
 &= x + y(1) + z \\
 &= \underline{\underline{x+y+z}}
 \end{aligned}$$

$* xy\bar{z} + x(y'+z')$ $x(yz+y') + x\bar{z}'$ $= x(y'+z) + x\bar{z}'$ $= xy' + x$ $= x(y'+1)$ $= \underline{\underline{x}}$	$* w'x(z'+y'\bar{z}) + x(w+w'y\bar{z})$ $w(x)(z'+y') + xw(w+y\bar{z})$ $w(x)(z'+y') + xwyz$ $w'x(z'+y') + x(w+y\bar{z})$ $\cancel{x}\cancel{z} + w$ $x[w'z' + w'y' + w + y\bar{z}]$ $x[w'(xy+z) + (w+y)(w+\bar{z})]$
--	--

$$* w'x(x'y + yz) + xe(w + w'y z) \\ w'(x)(x'y + yz) + xe(w + yz)$$

$$\begin{aligned} & xe[w'x' + w'y' + w + yz] \\ & = xe[w'(yz)' + w + yz] \\ & = xe[(w + yz)' + (w + yz)] = xe[1] = \underline{\underline{x}} \end{aligned}$$

$$* xy + x'z + yz = xy + x'z$$

$$= xy + z(x' + y) \quad \cancel{\text{LHS}}$$

$$= \cancel{xy + z(x' + y)}$$

$$= xy + x'z + zy$$

$$= y(x + z) + x'z \quad \text{LHS, RHS, RHS}$$

xz	$y + z$	xz'	$x + z$	$y(x+z)$	$x'z$	Sum	xy	$xy + x'z$
01	0	0	0	0	0	0	0	0
01	0	1	1	0	1	1	0	1
01	1	0	0	0	0	0	0	0
10	0	0	1	0	0	0	0	0
10	1	1	1	1	0	1	1	1
10	0	1	1	0	0	0	0	0
10	0	0	1	0	1	1	0	1
01	1	1	1	1	1	1	0	1

LHS=RHS

$$* \cancel{xy + x'z + yz} = xy + x'z$$

$$\cancel{xy + x'z + yz}$$

$$y(x+z) + x'z$$

$$y(x + x'z) + x'z$$

$$= xy + x'(z)(1+y).$$

$$= xy + x'z$$

$1. xy + yz + x'z \rightarrow \text{CONSENSUS THEOREM}$

$$(1+z)(xy) + yz + x'z$$

$$xy + xyz + yz + x'z$$

$$xy + x'z + yz$$

* CONSENSUS THEOREM: $\cancel{xy + x'z + yz} = xy + x'z$

$$\therefore xy + x'z + yz + 1$$

A function contains variables $x, y, z \in B$ and operators (and, or, not)

F

x	y	z	xy	x'z	yz	xy + x'z + yz
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	0	0	0
1	0	0	0	1	0	1
0	1	1	0	0	0	0
1	0	1	0	0	0	0
1	1	0	1	0	0	1
1	1	1	1	0	1	1

minterms:

$$F = \sum m(1, 3, 6, 7)$$

$$F = x'y'z + x'y\bar{z} + xy\bar{z}' + xy\bar{z}$$

term

For these four terms,
function evaluates to 1.

$$\begin{aligned}
 &= xy + x'\bar{z} + xy\bar{z} \\
 &= xy(\bar{z} + z') + x'\bar{z}(y + y') + xy\bar{z}(x + x') \\
 &= \underline{xy\bar{z}} + \underline{xyz'} + \underline{x'y'z} + \underline{xy\bar{z}} + \underline{x'y\bar{z}} \\
 &= \cancel{xy\bar{z} + xyz'} + \cancel{x'y'z} + \cancel{x'y\bar{z}} + \cancel{xy\bar{z} + x'y\bar{z}}
 \end{aligned}$$

Minterm: Combination of all the variables which are unknown in a given expression.

Function 'F' is referred to as Sum of Products form (SOP).

$$F = x'y'z + x'y\bar{z} + xy\bar{z}' + xy\bar{z} \Rightarrow \text{Sum of Minterms}$$

$$F = \sum m(0, 2, 4, 5)$$

$$F = 0$$

$x=0, y=0, z=0 \Rightarrow F' = 0$

max terms \Rightarrow to represent F'

$x=1, y=1, z=1 \Rightarrow F = 1$

min terms \Rightarrow to represent F

$$F = \prod M(0, 2, 4, 5) \quad (F' = \prod M(1, 3, 6, 7))$$

$$= (x+y+z) \cdot (x+y'+z) \cdot (x'+y+z) \cdot (x'+y+z')$$

\Rightarrow Product of Sums (POS form) = Product of Max terms

$$* F = xy + x'z$$

(a) POS (b) complement of F

(c) SOP

(d) Canonical POS

$$F = xy + x'z$$

$$F = \overline{xy\bar{z}} + \overline{x'y\bar{z}} \cdot (\overline{x} + \overline{y} + \overline{z}) =$$

$$F = \overline{xy}(\overline{z} + z') + \overline{x'}z(y + y')$$

$$(c) F = \overline{xy} + \overline{x'}z \quad (SOP) \quad M \prod = 7$$

$$(b) F = (\overline{xy} + \overline{x'}z)^1 \quad (POS) \quad \text{we have SOP}$$

$$= (\overline{xy})^1 \cdot (\overline{x'}z)^1 \quad \text{We get POS as compliment}$$

$$= (\overline{x} + y') \cdot (\overline{x} + z')$$

$$F' = (\overline{x} + y') \cdot (\overline{x} + z') \quad \text{or} \quad \text{if we have POS}$$

$$(d) \quad \text{POS: } \overline{xy} + \overline{x'}z \quad \text{we get SOP as compliment}$$

$$= \overline{xyz} + \overline{xy}\overline{z} + \overline{x}\overline{yz} + \overline{x}\overline{y}\overline{z}$$

a) POS

$$a \cdot (b+c) = a \cdot b + a \cdot c.$$

$$\frac{xy}{a} + \frac{x'z}{b} = (xy + x')(zy + z)$$
$$a + bc = (a+b)(a+c)$$

$$= (x'+y)(xy+z)$$

$$= (x+x')(y+x')(xy+z)$$

$$= (x'+y)(xy+z)$$

$$= (x'+y)(x+z)(y+z) \rightarrow \underline{\text{POS}}$$

$$= (x'+y+z \cdot z')(x+y \cdot y'+z)(x \cdot x'+y+z)$$

$$= (x'+y+z)(x'+y+z')(x+y+z)(x+y'+z)$$

$$(x+y+z)(x'+y+z)$$

$$= (x'+y+z)(x'+y+z')(x+y+z)(x+y'+z)$$

$$F = \prod M(4, 5, \emptyset, 2)$$

$$F = \sum m(i; 3, 6, 7) :$$

) Canonical SOP:

$$= xy + x'z$$

$$= xy(z+z') + x'z(y+y')$$

$$= xyz + xyz' + x'y'z + x'y'z'$$

$$* F = yz + x' + xz'$$

06/06/2022

- a) Canonical SOP
- b) Canonical POS
- c) Minimal POS
- d) F
- e) Truth Table.

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	1
1	0	0	1
1	1	1	1
1	1	0	1
1	0	1	0
0	1	1	1

$\begin{matrix} 0 & 1 & 1 \\ 0 & 0 & 1 \\ 0 & 0 & 0 \\ 0 & 1 & 0 \end{matrix}$
 $\begin{matrix} 1 & 1 & 0 \\ 1 & 0 & 0 \end{matrix}$

~~(a)~~ POS =
~~CD'y~~
 $(x+y'+z)$

Canonical SOP = $\sum m(0, 1, 2, 4, 7, 3, 6)$

Canonical POS = $\prod M(5, 6)$.

~~yzxz~~ $\oplus = \oplus^1$ ~~yz~~

$$\begin{aligned}
 F &= yz(x+x') + x'(y+y')(z+z') + x(y+y')z \\
 &= xyz + x'y'z + (x'y + x'y')(z+z') + xyz' + x'y'z' \\
 &= xyz + x'y'z + x'y'z + x'y'z' + x'y'z + x'y'z' + xyz' + x'y'z
 \end{aligned}$$

$$\begin{aligned}
 &= xyz + x'y'z + x'y'z + x'y'z' + x'y'z + x'y'z' + xyz' + x'y'z
 \end{aligned}$$

a) POS

$$\begin{aligned} \overline{a} \cdot y + \overline{a'} \cdot z &= (\overline{a}y + \overline{a'})(\overline{a}y + z) \\ &= (\overline{a} + y)(\overline{a}y + z) \\ &\Rightarrow = (\overline{a} + \overline{a'})(y + \overline{a'})(\overline{a}y + z) \\ &= (\overline{a} + y)(\overline{a}y + z) \\ &= (\overline{x} + \overline{y} + \overline{z})(\overline{x} + \overline{y} + \overline{z})(\overline{y} + \overline{z}) \xrightarrow{\text{POS}} \\ &= (\overline{x} + y + z \cdot \overline{z})(\overline{x} + y \cdot y' + \overline{z})(\overline{x} \cdot \overline{x}' + y + \overline{z}) \\ &= (\overline{x} + y + z)(\overline{x} + y + z')(\overline{x} + y + z)(\overline{x} + y' + z) \\ &\quad (\overline{x} + y + z)(\overline{x} + y + z) \\ &= (\overline{x} + y + z)(\overline{x} + y + z')(\overline{x} + y + z)(\overline{x} + y' + z) \end{aligned}$$

$$F = \prod M(4, 5, \emptyset, 2)$$

$$F = \sum m(1, 3, 6, 7)$$

e) Canonical SOP:

$$xy + \overline{x}y'$$

$$xy(\overline{z} + z') + \overline{x}y'(\overline{y} + y')$$

$$= xyz + xy\overline{z} + \overline{xy}z + \overline{xy}\overline{z}$$

$$= \overline{x} + \overline{y} + \overline{z} + xy + \overline{xy} + \overline{yz} + \overline{xy}z$$

$$* F = yz + \bar{x}' + xz'$$

- a) Canonical SOP
- b) Canonical POS
- c) Minimal POS
- d) F
- e) Truth Table

Max: $x=0$ 06/06/2022

$$\bar{x}' = 1$$

$$\text{Min: } x=1$$

$$\bar{x}' = 0$$

$$y + z \cdot y + yz + \bar{y}x + \bar{y}x \cdot y = 7$$

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

POS =

$$(x+y+z)$$

$$\text{canonical SOP} = \sum m(0, 1, 2, 4, 7, 16)$$

$$\text{Canonical POS} = \prod M(5, 6).$$

$$0 + x'y'z + 0 + (0 + x'y'z + x'y'z + x'y'z + x'y'z) =$$

$$\cancel{x}\cancel{y}\cancel{z} \oplus \cancel{y} = \cancel{x}\cancel{y}z$$

$$F = yz(x+x') + x'(y+y')(z+z') + x(y+y')z$$

$$= x'yz + x'y'z + x'y'z + x'y'z + x'y'z + x'y'z$$

$$= xyz + x'y'z + x'y'z + x'y'z + x'y'z + x'y'z$$

09/06/2022

$$* F = (x+y) \cdot (x'+y')$$

$$F = x \cdot x' + x \cdot y' + y \cdot x' + y \cdot y'$$

$$F = \boxed{xy' + x'y} \rightarrow \text{Canonical SOP}$$

$$F' = [(x+y) \cdot (x'+y')]$$

$$= (x+y)' + (x'+y')$$

$$(F')' = (x'y' + x'y)$$

$$= (x'y')' \cdot (x'y)'$$

$$= (x+y) \cdot (x'+y')$$

$$* F = (x+y+z) (x'+y'+z) (x+y')$$

$$= (xx' + xy' + xz + yx' + yy' + yz + z'x) \\ + z'y' + z'z)(x+y)$$

$$= (xy' + xz + x'y + yz + x'z + y'z)(x+y)$$

$$= xy' + xz + x'y + yz + x'z + y'z + 0 + x'yz + 0 \\ + 0 + x'z'y' + x'y'z' + y'z$$

$$= (x+y)x + (x+z)(x+y)z + (x+z)y = 7$$

$$F = xy' + xz + x'y + yz + x'z + y'z$$

$$= xy' + xz + x'y + yz + x'z + y'z$$


x	y	z	F	\Rightarrow Maxterm form
0	0	0	1	$F = \prod M(1, 2, 3, 6) \Rightarrow \text{POS}$
0	0	1	0	$F' = \sum m(0, 4, 5, 7) \Rightarrow \text{SOP}$
0	1	0	0	
0	1	1	0	
1	0	0	1	$F' = \sum m(1, 2, 3, 6)$
1	0	1	1	$F' = \prod M(0, 4, 5, 7)$
1	1	0	0	
1	1	1	1	$F = \sum m(0, 4, 5, 7)$ \Rightarrow gives canonical SOP \Rightarrow we need to simplify to get minimal SOP.

10/06/2022

* KARNAUGH MAP: [K-Map]

$$F(x, y, z) = \sum m(0, 4, 5, 7).$$

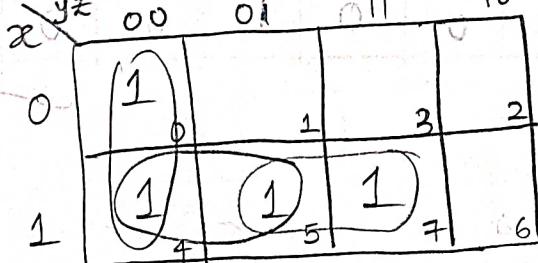The number of cells in a map depends on
the no. of combinations (no. of variables) = 2^n .



$x \rightarrow$ most signif bit

$y \rightarrow$ middle

$z \rightarrow$ least signif bit

$$(x'y' + xy' + xy) \oplus (x'y + x'y')$$

1) Take a map with 2^n cells. ($n = \text{no. of cells}$)

2) Map 1's on to the cells based on function.

3) Grouping 1's. (Grouping can be done only
in horizontal / vertical)

4) Consider grouping of max. possible 1's.

5) Group must be of powers of 2. (2, 4, 8, ...)

$2^0, 2^1, 2^2, 2^3, \dots$

$$\Rightarrow \cancel{y'z' + \alpha z} : y'z' + \alpha z + \alpha y : y'z' + \alpha z$$

This method is used only when it is in canonical.

$\left. \begin{matrix} 00 \\ 01 \\ 11 \\ 10 \end{matrix} \right\}$ Gorey Code: which only one bit changes at a time.

$$\Rightarrow \alpha y' + \alpha z + y'z'$$

$$\alpha(y' + z) + y'z$$

α	$y'z'$	yz	α'	y'	z'	$\alpha y'$	αz	$y'z'$	$y'z$	αz	αz
0	0	0	1	1	1	0	0	1	1	0	0
0	0	1	1	0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0
0	0	0	0	1	1	1	0	1	0	0	0
0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0

If it is 2 based - s

$$= \alpha(y' + z) + y'z'$$

$$\alpha(y' + z) + (y + z)$$

* $F = \sum m(0, 1, 2, 3)$

	00	01	11	10
0	1	1	1	1
1				
2				
3				

$$\bar{x}^1y^1 + \bar{x}^1y : \underline{\underline{x^1}}$$

$$= \underline{\underline{x^1}}$$

* $F = \sum m(0, 1, 6, 7)$

	00	01	11	10
0	1	1	1	1
1				
2				
3				
4				
5				
6				1
7				1

* $F = \sum m(0, 1, 2, 5, 7)$

	00	01	11	10
0	1	1	1	1
1				
2				
3				
4				
5				1
6				1
7				1

* $\sum m(0, 1, 3, 6, 7)$

	00	01	11	10
0	1	1	1	1
1				
2				
3				
4				
5				
6				
7				

* $\sum m(0, 1, 2, 3, 4, 5, 6, 7)$

	00	01	11	10
0	(1) P(1, 0)	(1)	(1)	(1)
1	(1)	(1)	(1)	(1)
2				
3				
4				
5				
6				
7				

* $\sum m(0, 1, 2, 3, 4, 5, 6, 7)$

	00	01	11	10
0	(1)	(1)	(1)	(1)
1	(1)	(1)	(1)	(1)
2				
3				
4				
5				
6				
7				

$$\bar{x}^1z^1 + \bar{x}^1y + yz$$

$$= \underline{\underline{x^1}} + \underline{\underline{xy}}$$

* K-map

	00	01	11	10
0	1			1
1		1		

$$\bar{x}\bar{z}' + \bar{x}yz$$

* Implicant: 1 mapped in K-map.

* Prime Implicant: Group of 1's (Largest / Maximum)

5 implicant

3 Prime implicants

	00	01	11	10
0	1	1	1	1
1			1	1

* Essential Prime Implicant:

Atleast one 1 not covered by any other group.

Ex: $F = \bar{x}y' + \bar{x}z + \bar{xy}$

$$F = \bar{x}y' + yz + \bar{xy}$$

$\therefore \bar{x}y'$ and \bar{xy}
are essential prime implicant

* K-Map (Karnaugh Map):

4 Variable K-map $F = \sum m(0, 1, 7, 9, 11, 12)$

		cd	00	01	11	10
		ab	00	01	11	10
00	00	0	1	3	2	
		4	5	7	6	
01	01	12	13	15	14	
		8	9	11	10	

ab\cd	00	01	11	10
00	1	1		
01			1	
11	1			
10		1	1	

$$a'b'c' + abc'd + abc'd' \\ + ab'd \quad \cancel{+ ab'd}$$

Implicants = 6


$$PI = 4 \\ EPI = 4$$

ab\cd	00	01	11	10
00		1	1	
01		1	1	
11	1			
10		1	1	

$$abd' + a'd + ab'd$$

Implicants = 8

$$P.I = 3 \\ EPI = 3$$

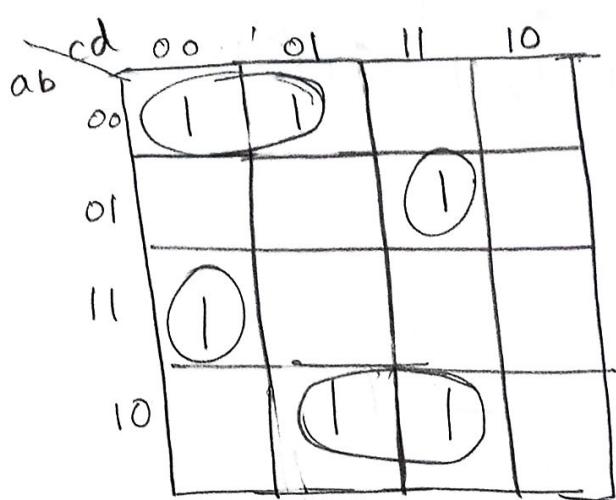


$$a'b'c' + abc'd + abc'd' + ab'd$$

Implicants = 6

$$PI = 4$$

$$EPI = 4$$

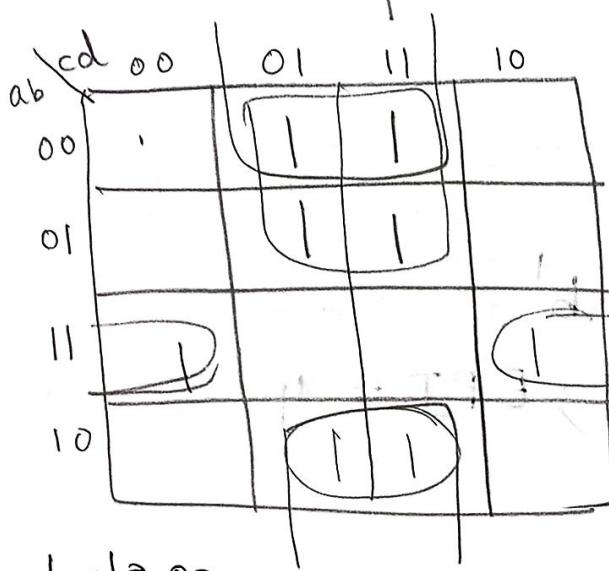

$$abd' + a'd + b'd$$

Implicants = 8


$$P.I = 3 + b'c = 7$$

$$EPI = 3$$

13/06/2022

4 var K-Map
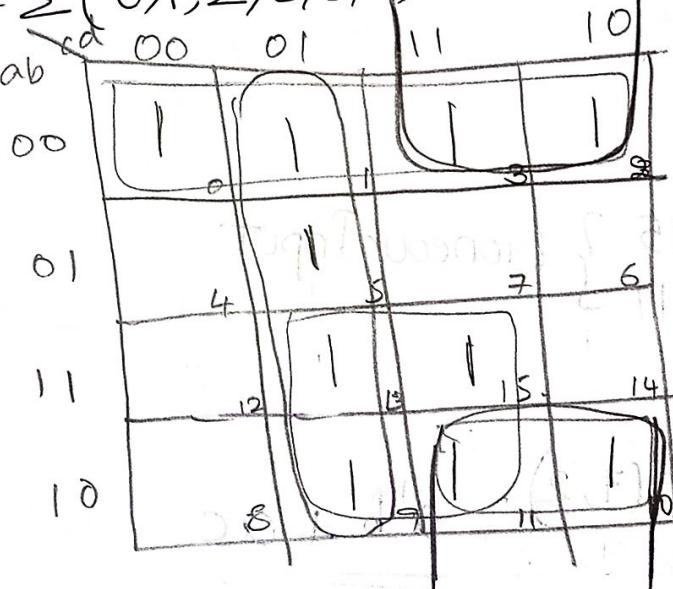
$$F = \sum (0, 1, 2, 3, 5, 9, 10, 11, 13, 15)$$



Implicants = 10

$$PI = 4$$

$$EPI = 4$$

$$a'b' + c'd + b'c + ad$$

$$* \Sigma m(0, 2, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13)$$

ab	cd' 00	01	11	10
00	1			1
01	1	1	1	1
11				
10	1	1	1	1


ac!

$$F = a'd + bcd + a'b + ab'$$

$$\text{Implicants} = 12, P.I. = 4, EPI = 4$$

* Don't care condition:

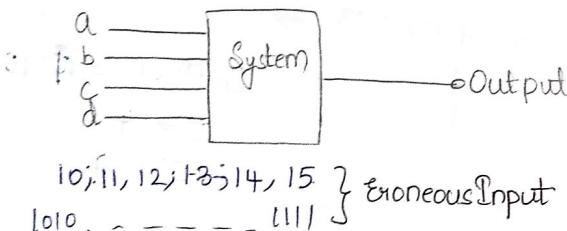* For a particular input; we get an output which is not necessary.



16/06/2022

$$* F = \Sigma m(0, 1, 5) + \Sigma d(7, 2).$$

a	b	c	d	de	00	01	11	10
0	1	1	1		1	1	1	2
1	1	1	1	X	1	1	1	2

$a'b' + ac$

$$* G = \Sigma m(1, 2, 5, 7, 6) + \Sigma d(13, 14, 15, 8).$$

ab	cd	00	01	11	10
00	1	1	1	1	1
01	1	1	1	1	1
11		X	X	X	
10	X	8	9	11	12

$a'c'd + bd + a'cd$

* 5-Variable K-Map:

$$2^5 = 32 \text{ combinations}$$

We use 2 guilds containing 16 cells each.

$$F(a, b, c, d, e) = \Sigma m(0, 1, 4, 7, 10, 15, 20, 22, 26, 30)$$

bc	de	a=0				a=1			
		00	01	11	10	00	01	11	10
00	1	1	1	1	2	15	12	13	18
01	1	1	1	1	6	1	20	21	23
11		12	13	15	14	24	25	31	30
10		8	9	11	10	24	25	27	26

$$F = a'b'c'd' + a'cde + b'cd'e' + bc'de'$$

$$* F(a, b, c, d, e) = \Sigma m(2, 5, 7, 13, 15, 8, 21, 23, 29, 30, 31) + \emptyset(18, 20, 24)$$

	de	00	01	11	10	bc	uv	v
	00	0	1	3	2	00	16	17
	01	4	5	7	6	01	X	18
	11	12	13	15	14	11	28	29
	10	8	9	11	10	10	X	24

$a = 0$

$a = 1$

$$F = b'c'de' + bc'd'e' + a'ce + ace + abcd \\ = b'c'de' + bc'b'd'e' + ce + abcd$$

$$I = 14 \quad P.I = 4 \quad E.P.I = \underline{4}$$



23/06/2022

UNIT-2

TABULATION METHOD:

Purpose: K-Map \rightarrow Simplify Boolean functions to minimum no. of literals

$$F = \sum m(0, 1, 3, 6, 7)$$

Step-1: Group according to no. of 1's

$$\begin{array}{l} \checkmark 0-0000 \\ \checkmark 1-0001 \\ \hline \checkmark 3-0011 \\ \checkmark 6-0110 \\ \hline \checkmark 7-0111 \end{array}$$

Step-2: Group adjacent elements. (only one bit change group)

$$\begin{array}{l} 0, 1 : 00- \\ 1, 3 : 0-1 \\ 6, 7 : 011- \\ 3, 7 : -11 \end{array}$$

Step-3: Cannot group further \rightarrow Stop

Step-4: Prime Implicant Chart. column with only 1 X is called P.I.

	0	1	3	6	7	1 X is called P.I.
*	$a'b'$ (01)	(X)	X			
*	$a'c$ (13)		X	X		
*	bc (3)			X		
*	a, b				(X)	X

$$F = a'b' + a'c + ab$$

(or) $= a'b' + bc + ab'$

$$E.I = 2(a'b' + ab)$$

$$2) F = \Sigma m(0, 1, 5, 6, 9, 11, 12, 13, 15)$$

$$\begin{array}{r} \cancel{10} - 0000 \\ \cancel{11} - 0001 \\ \hline \cancel{15} - 0101 \\ \cancel{6} - 0110 \\ \hline \cancel{9} - 1001 \\ \cancel{12} - 1000 \\ \cancel{12} - 1000 \\ \hline \cancel{13} - 1101 \\ \cancel{15} - 1111 \end{array}$$

Step-1:

$$\begin{array}{r} 2(9-1) \\ 2(4-0) \\ 2(2-1) \\ 2(11-1) \\ 2(5-1) \\ 2(2-0) \\ 2(13-1) \\ 2(6-0) \\ 2(3-1) \\ 1 \end{array}$$

Step-2: underscore should match

$$\begin{array}{r} 0,1: 000- \\ \hline \cancel{1},5: 0-01 \\ \cancel{1},9: -001 \\ \cancel{9},11: 10-1 \\ \cancel{5},13: -101 \\ \cancel{9},13: 1-01 \\ \cancel{12},13: 110- \\ \cancel{11},15: 1-11 \\ \cancel{13},15: 11-1 \end{array}$$

	10	11	15	6	9	11	12	13	15
*ab'd'				X					
*a'b'c'	(X)	X							
*abc'					X				
*c'd'		X	(X)	X		X			
*ad					X	(X)	X	(X)	

$$F = a'bcd' + a'b'c' + abc' + c'd + ad.$$

24/06/2022

$$2) \Sigma m(2, 6, 8, 9, 10, 11, 14, 15)$$

$$\begin{array}{r} 2 - 0010 \\ 6 - 0110 \\ 8 - 1000 \\ 9 - 1001 \\ 10 - 1010 \\ 11 - 1011 \\ 14 - 1110 \\ 15 - 1111 \end{array}$$

Step-I

Step-II

$$\begin{array}{r} \cancel{\sqrt{2}} \cdot 6: 0-10 \\ \cancel{\sqrt{2}} \cdot 10: -010 \\ \cancel{\sqrt{8}} \cdot 9: 100- \\ \cancel{\sqrt{8}} \cdot 10: 10-D \\ \cancel{\sqrt{14}} \cdot 11: 10-1 \\ \cancel{\sqrt{14}} \cdot 14: -110 \\ \cancel{\sqrt{15}} \cdot 15: 101- \\ \cancel{\sqrt{10}} \cdot 11: 101- \\ \cancel{\sqrt{10}} \cdot 14: 1-10 \\ \cancel{\sqrt{11}} \cdot 15: 1-11 \\ \cancel{\sqrt{14}} \cdot 15: 111- \end{array}$$

Step-III

$$\begin{array}{r} 2, 6, 10, 14: --10 \\ 2, 10, 6, 14: --10 \\ 8, 9, 10, 11: 10-\cancel{bcd} \\ 8, 10, 9, 11: 10- - \\ 10, 14, 11, 15: 1-\cancel{a1}- \\ 10, 11, 14, 15: 1-1- \end{array}$$

	2	6	8	9	10	11	14	15
*cd'	(X)	(X)			X		X	
*ab'			(X)	(X)	X		X	
*ac					X	X	X	(X)

$$F = cd' + ab' + ac.$$

$$3) G = \sum m(0, 4, 5, 7, 12, 15) + d(8, 11)$$

	\sum	Step-II
0 - 0000	$\checkmark 0 - 0000$	
4 - 0100	$\checkmark 4 - 0100$	$0, 4, 8, 12, 15$
5 - 0101	$\checkmark 8 - 1000$	$0, 8, 12, 15$
7 - 0111	$\checkmark 5 - 0101$	$4, 5, 12, 15$
12 - 1100	$\checkmark 12 - 1100$	$4, 12, 15$
15 - 1111	$\checkmark 7 - 0111$	$8, 12, 15$
8 - 1000	$\checkmark 11 - 1011$	$5, 7, 12, 15$
11 - 1011	$\checkmark 15 - 1111$	$11, 15$

Step-III:

$$0, 4, 8, 12: \underline{\quad} \underline{00}$$

$$0, 8, 4, 12: \underline{\quad} \underline{00}$$

$$\begin{array}{l} P.I = 5 \\ EPI = 1 \end{array}$$

	0	4	5	7	12	15	8	11
$a'bcd$	X	X						
$a'bd$		X	X					
acd				X				
bcd					X	X		
$*c'd$	(X)	X	(X)	(X)		(X)		

~~F = acd~~ ~~F = c'd~~

$$F = c'd' + a'b'd + acd.$$

$$= c'd' + bcd + a'bc'$$

$$= c'd' + a'b'd + bcd.$$


27/06/2022

$G = \sum m(1, 3, 6) + d(2, 5)$: Design a AND-OR circuit.

1 - 0001
3 - 0011
6 - 0110
2 - 0010
5 - 0101

	bc	00	01	11	10
a	00	1	1	X	1
b	01	0	0	1	1
c	11	0	1	1	0
d	10	1	0	0	1

$$F = a'c + bc'$$

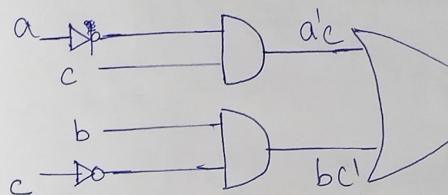

$$G = \sum m(1, 2, 7, 9, 11) + d(12, 8, 13)$$

a	b	cd	00	01	11	10
0	0	0	1	1	1	1
0	1	0	0	1	1	1
1	1	X	X	1	1	1
1	0	X	X	1	1	1

$$\cancel{a'c'd} + b'c'd \quad \begin{matrix} d=0 \\ c=1 \end{matrix}$$

$$+ ab'd + a'b'cd'$$

$$+ a'b'cd$$



$$= \cancel{ac'}(\cancel{b} + \cancel{b}) + b'c'd + a'b'cd'$$

$$+ a'b'cd$$

$$= ac' + b'c'd + a'b'cd' + a'b'cd$$

$$+ a'b'cd$$

$$= b'c'd + ab'd + a'b'cd' + a'b'cd$$

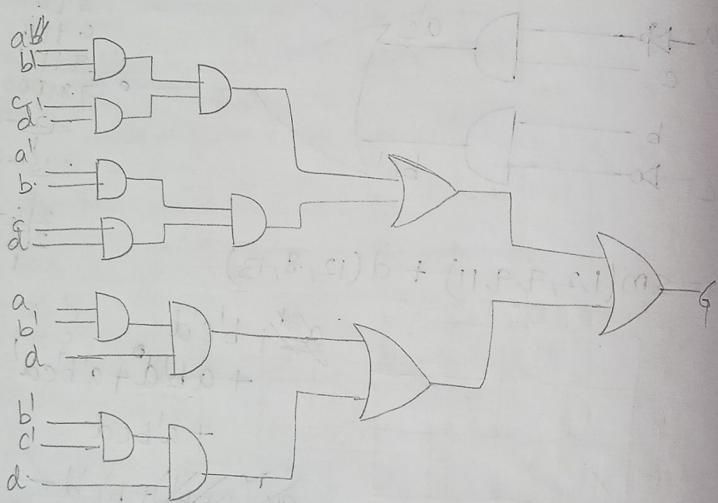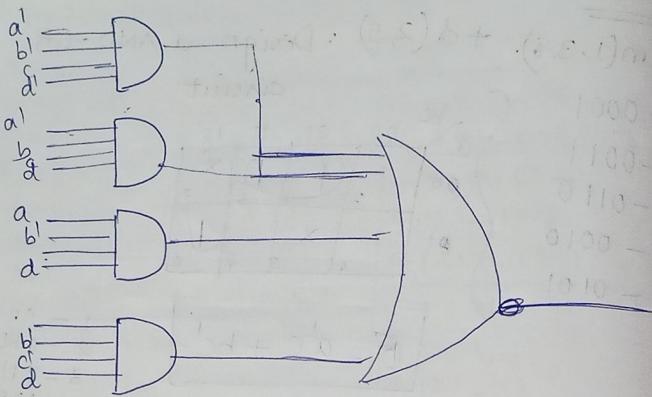

⇒ All the parallel running gates have same time delay.


If the propagation delay of AND gate is 2 msec and OR gate is 3 msec. Calculate the total propagation delay.

→ The amount of time taken to give the output for the given input is called propagation delay.

$$\text{total time} = 2+2+3+3 = 10$$

$$* F = (c+d')(a+b')$$

$$= ac + b'c + ad' + b'd'$$

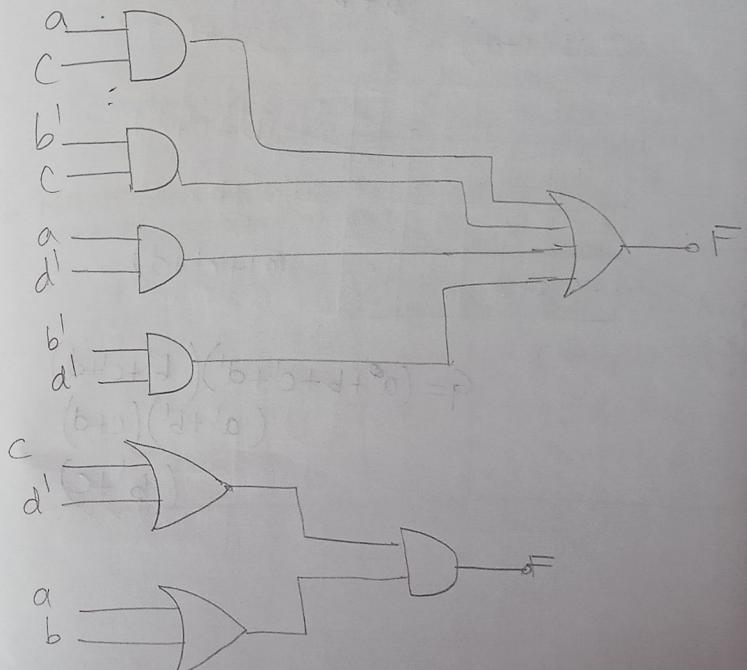

* OR-AND CIRCUIT:

$$F = b'c'd + abd + a'b'cd' + a'bcd$$

$$F = (b+c) + d' + (a+b)d + a+b+c+d$$


	cd	00	01	11	10	
ab	00	0	1	1	0	$(a+b+c+d)$
	01	4	5	7	6	$a+b+c+d'$
	11	X	X	13	15	$(a+b+c+d')$
	10	X	1	1	11	$a+b+d$

	cd	00	01	11	10	
ab	00	0	1	0	2	$a+b+c+d$
	01	0	0	5	7	$b+c+d$
	11	X	X	0	15	$a+b'$
	10	X	X	9	11	$a+c+d$

$(b'+c)$ $(+d)$

$$G = (a^0 + b + c^1 + d^1)(b^1 + c^1 + d)$$

$$(a^1 + b^1)(c + d)$$
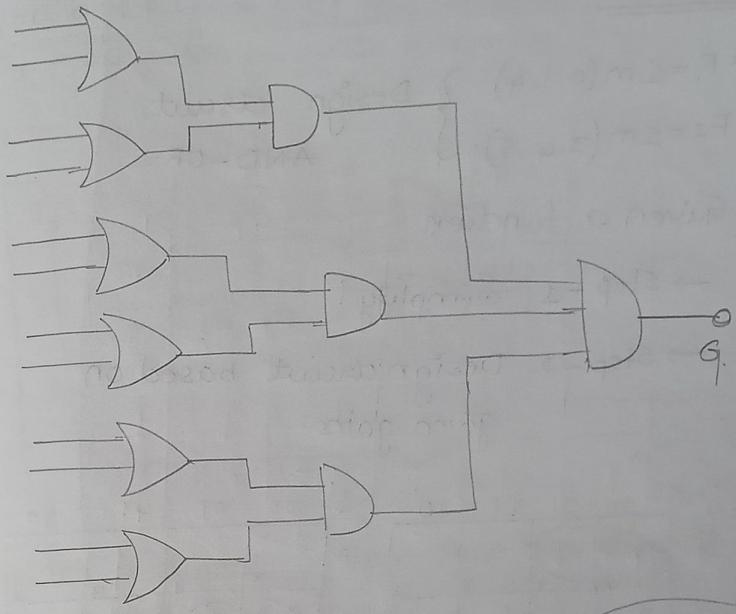
$$(b^1 + c)$$


* NAND and NOR Gates:

x	y	$x \cdot y$	$\bar{x} \bar{N}AND y$	$\bar{x} NOR y$	$x + y$
0	0	0	1	1	0
0	1	0	1	0	1
1	0	0	1	0	1
1	1	1	0	0	1

30/06/2022

$$* F_1 = \sum m(0, 1, 4) \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{Design circuit}$$

$$F_2 = \sum m(3, 4, 5) \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{AND-OR}$$

Given a function:

→ Step-1: Simplify

→ Step-2: Design circuit based on given gates.

a	b	c	00	01	11	10
0	1	1	1	1	0	2
1	0	1	0	1	1	3
			4	5	7	6


F1

a	b	c	00	01	11	10
0	1	1	1	1	0	2
1	0	1	0	1	1	3
			4	5	7	6

F2


$$F_1 = a'b' + b'c'$$

$$F_2 = a'b'c' + ab'$$

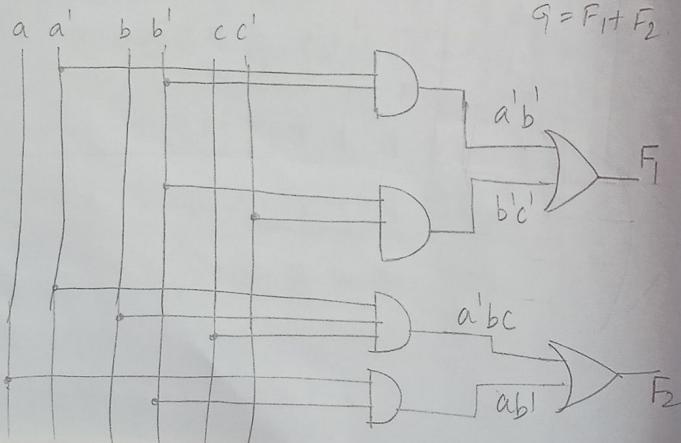

$$* F_1 = a'b' + b'c'$$

$$F_2 = b'c' + ab'$$

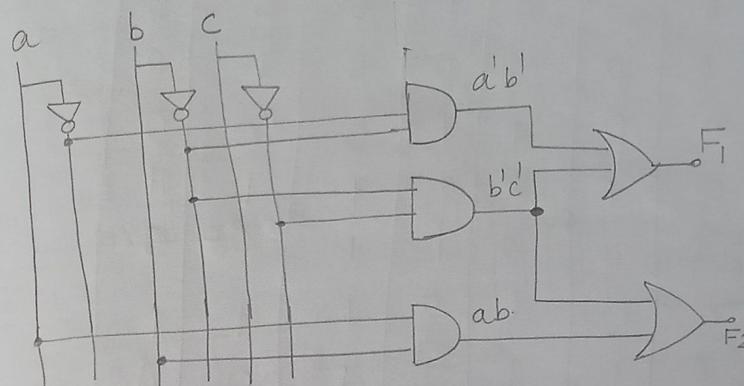

* Consider a digital system that has 3 outputs and takes 4 inputs

→ First O/P is assertive when b is high.

→ Second O/P is assertive when low when the I/O is odd.

→ Third O/P is high if both first O/P & second O/P are high.

next page

a	b	c	d	F1	F2	F3
0	0	0	0	0	1	0
0	0	0	1	0	0	0
0	0	1	0	0	1	0
0	0	1	1	0	0	0
0	1	0	0	1	1	1
0	1	0	1	0	0	0
0	1	1	0	1	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	0
1	1	0	0	1	1	1
1	1	0	1	0	0	0
1	1	1	0	1	1	1
1	1	1	1	1	0	0

$$F_1 = \sum m(4, 5, 6, 7, 12, 13, 14, 15)$$

$$F_2 = \sum m(0, 2, 4, 6, 8, 10, 12, 14)$$


$$F_3 = \sum m(4, 6, 12, 14)$$

F1:

ab	cd	00	01	11	10
00	00	0	1	2	2
01	14	1	1	7	6
11	1	1	1	1	1
10	12	13	15	14	10
	8	9	11	10	

$$F_1 = b$$

Circuit

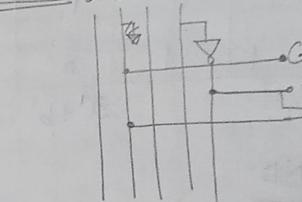

F2:

ab	cd	00	01	11	10
00	10	0	1	3	2
01	1	1	4	5	6
11	1	1	12	13	14
10	1	8	9	11	10

$$F_2 = d'$$

F3:


ab	cd	00	01	11	10
00	0	0	1	3	2
01	14	1	5	7	6
11	1	12	13	15	14
10	8	9	11	10	

$$F_3 = bd'$$

a	b	NAND $(ab)'$	NOR $(a+b)$	XOR $a \oplus b$	XNOR $a \otimes b$
0	0	1	1	0	1
0	1	1	0	1	0
1	0	1	0	1	0
1	1	0	0	0	1

$a' + b'$ $a' b'$ $a'b' + a'b$ $ab + a'b'$

NAND:

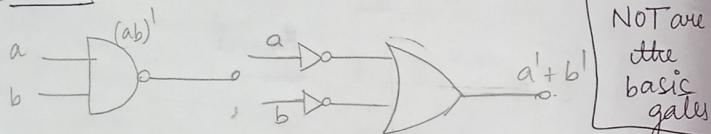


NOR:



Bubbled AND

XOR:

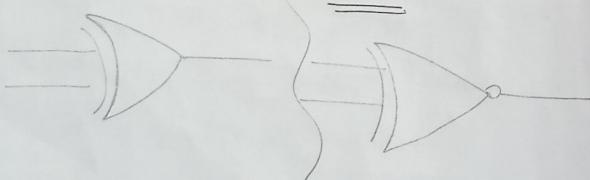

XNOR:

*	A	B	C	D	F
0	0	0	0	0	1
0	0	0	0	1	0
0	0	0	1	0	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	X	
0	1	1	1	0	
1	0	0	0	1	
1	0	0	1	0	
1	0	1	0	1	
1	0	1	1	X	
1	1	0	0	0	
1	1	0	1	1	
1	1	1	0	0	
1	1	1	1	1	

Min POS:

$$F = \Sigma m(0, 2, 4, 8, 10, 13, 15) + d(6, 11)$$

$$F = \prod M(1, 3, 5, 6, 7, 9, 12, 14) + d(6, 11)$$

a	b	Minterm	Maxterm
0	0	$a'b'$	$a+b$
0	1	$a'b$	$a+b'$
1	0	$a'b'$	$a'+b$
1	1	ab	$a'+b'$

cd	00	01	11	10
ab	00	0	0	0
00	0	1	1	2
01	0	0	0	3
11	0	0	1	4
10	0	1	1	5
11	1	0	0	6
11	1	1	0	7
10	1	0	1	8
10	1	1	1	9
11	1	1	0	10
11	1	0	0	11
10	0	1	0	12
10	0	0	1	13
11	0	1	0	14
11	0	0	0	15
10	1	0	0	16

$$F = (a+d')(a'+b'+d) \\ (a'+b+d')(b+d')$$

$$F' = a'd + abd' + b'd$$


$$F = (a+d')(a'+b'+d)(b+d') \\ \text{AND} \leftrightarrow \text{OR} \\ x \leftrightarrow x'$$

DUAL


01/07/2022

* NAND Gate:


1) AND:

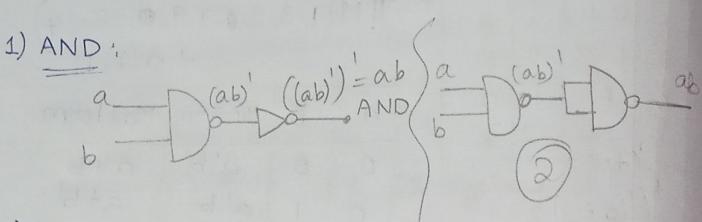


3) OR:

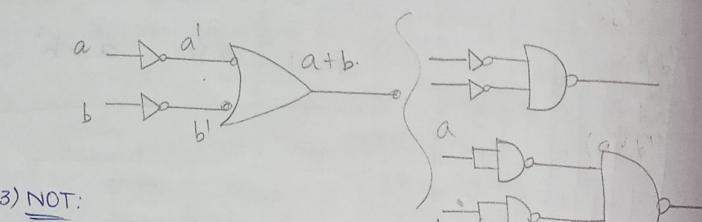

3) NOT:

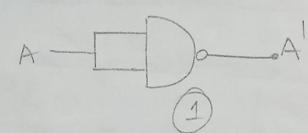


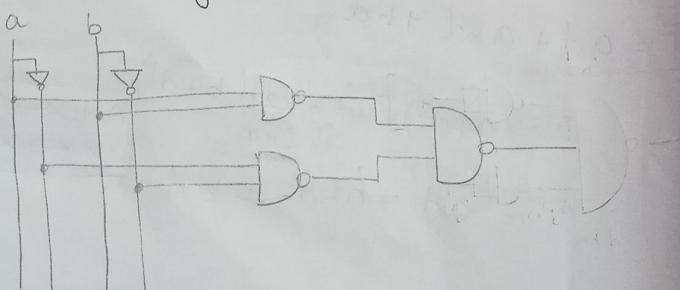* $G = ab + a'b'$ Design a circuit using NAND gates only.



$$* G = xyz' + x'z + y'$$

$$(xyz')' = x'y' + z$$

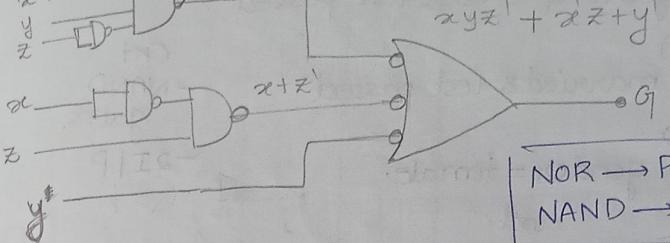


$\boxed{\text{NOR} \rightarrow \text{POS}}$
 $\boxed{\text{NAND} \rightarrow \text{SOP}}$

$$* G = \prod M(1, 3, 7, 9, 11)$$

ab	cd	00	01	11	10
00	0	0	D	D	2
01	4	5	7	6	
11		12	13	15	14
10	8	D	D		10
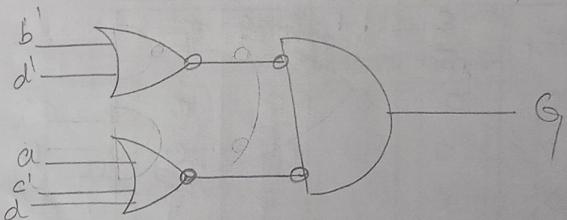
$$\begin{aligned} G &= b'd + a'b'd \\ G &= (b+d')(a+c'+d) \\ &= ab + bc' + bd \\ &\quad + ad' + cd' \end{aligned}$$



$$\sum m(0, 2, 4, 5, 6, 8, 10, 12, 13, 14, 15)$$

ab	cd	00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		12	13	15	14
10					

02/07/2022

* RTA office → Learner's License:
if age ≥ 18 & ≤ 60 & test passed.

(OR) married & test passed

(OR) gender = female.

and

No visual impairment.

CKT
-NAND
gates
-2I|P

a) I/P \rightarrow O/P's

b) TT

c) Simplify


d) CKT using basic

e) Then NAND gates.


Age	Test	$F=1$ Gender	$M=1$ Married	$T=0$ UM=0	$Y=0$ NO=1	$Z=0$ Blind	F
0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0
0	0	0	1	0	0	0	0
0	0	0	1	1	0	0	0
0	0	1	0	0	0	0	0
0	0	1	0	1	1	0	1
0	0	1	1	0	0	0	0
0	0	1	1	1	1	0	1
0	1	0	0	0	0	0	0
0	1	0	0	1	0	0	0

0	1	1	0	1	0	1	
0	1	1	0	1	1	1	
0	1	1	1	0	0	0	
0	1	1	1	0	1	1	
0	1	1	1	1	0	1	
0	1	1	1	1	1	1	
1	0	0	0	0	0	0	
1	0	0	0	0	1	0	
1	0	0	0	1	0	0	
1	0	0	1	0	1	0	
1	0	0	1	0	1	0	
1	0	1	0	0	0	0	1
1	0	1	0	0	1	1	1
1	0	1	0	1	0	1	1
1	0	1	0	1	1	1	1
1	0	1	1	0	0	0	1
1	0	1	1	0	0	1	1
1	0	1	1	0	1	0	1
1	0	1	1	0	1	1	1
1	0	1	1	1	0	0	1
1	0	1	1	1	0	1	1
1	0	1	1	1	1	0	1
1	1	1	1	1	1	1	1
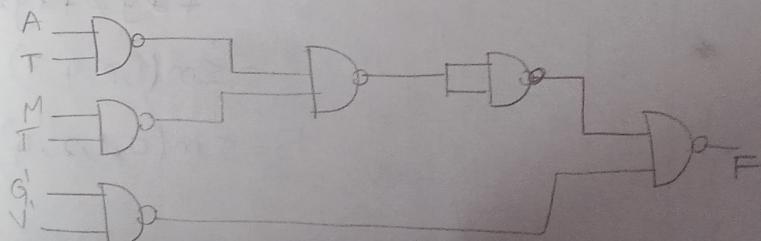
$$F = A \cdot T + M \cdot T + G' \cdot V' \quad \text{Nand gates}$$


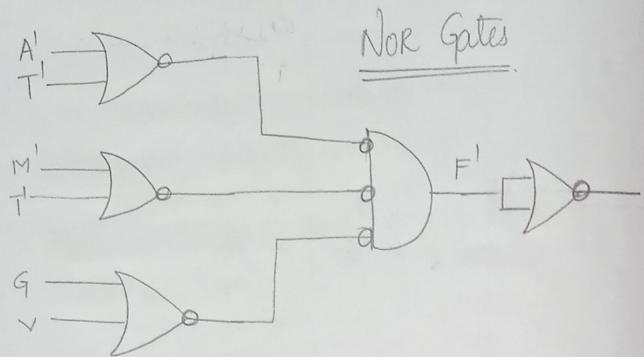
$$POS(F) = [(A' + T')(M' + T')(G + V)]'$$



* Design a circuit that has 2 outputs:
 1st output is 1 iff the no. of 1's in
 the input are odd. 2nd output is 1 iff
 there are atleast 2 zeroes in the input.
 * 3 variable input.

x	y	z	F_1	F_2
0	0	0	0	1
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	0


$$F_1 = x'y'z + \cancel{x'y'z} + \cancel{x'y'z}$$

$$F_1 = x'y'z + x'y'z$$

$$+ x'y'z + x'y'z$$

$$= \sum m(1, 2, 4, 7)$$


$$F_2 = \sum m(0, 1, 2, 4)$$

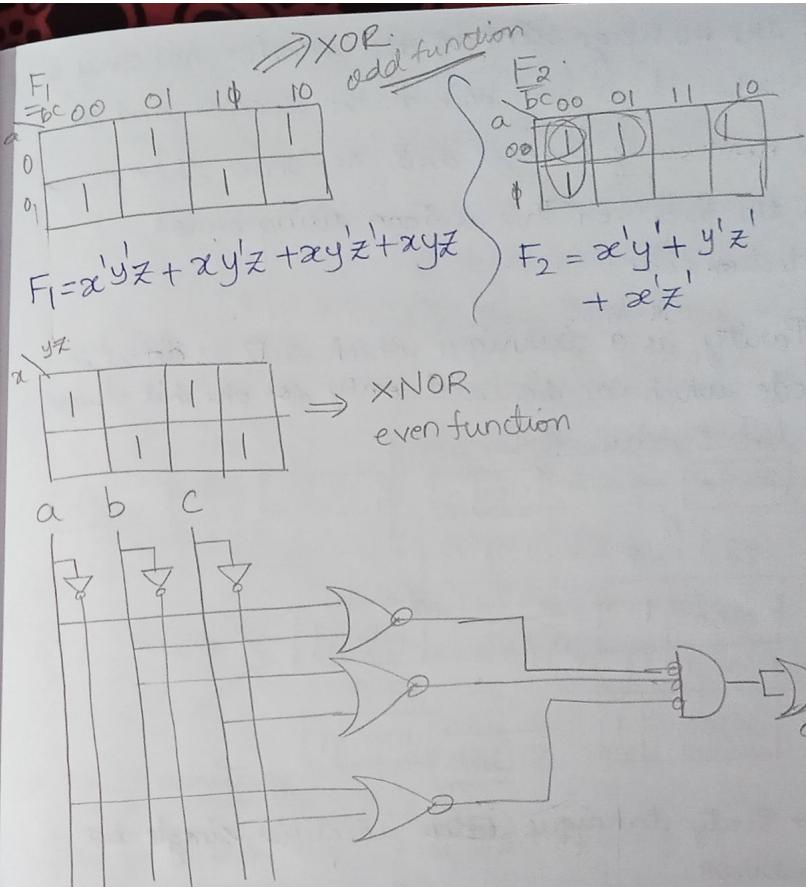

04/07/2022

* Parity :-


- Even parity
- Odd parity

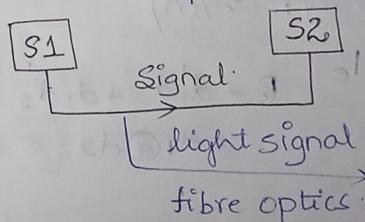

• Error detection and correction codes.

If the message sent by the sender has any errors it is sent back to the sender and do the necessary changes and re-send the message to the receiver. This is done using error detection code.

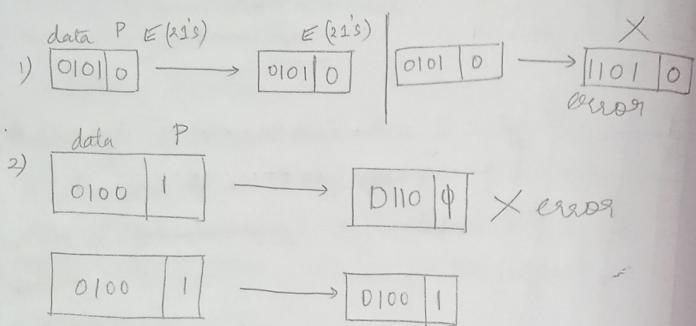* Parity is a technique which acts as detection code which can be used only for one bit change.



→ Parity technique identifies simple bit error.

* Parity Generator: Receiver side / Sender side

* Parity Checker: Receiver side.

⇒ 2 bit parity generator: (even)

d ₁	d ₂	P _e
0	0	0
0	1	1
1	0	1
1	1	0

$P_e = d_1' d_2 + d_1 d_2'$
 $= d_1 \oplus d_2$

d_1 d_2 $\Rightarrow P_e$


⇒ 2 bit parity checker: (Even)

d ₁	d ₂	P _e	P _{ec}
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

1-true
0-false.

$$\begin{aligned}
 P_{ec} &= d_1' d_2 d_3 + d_1 d_2' d_3 \\
 &\quad + d_1 d_2' d_3 + d_1 d_2 d_3' \\
 &= d_1'(d_2 d_3 + d_2' d_3) \\
 &\quad + d_1(d_2' d_3 + d_2 d_3') \\
 &= d_1'(d_2 \oplus d_3) + d_1(d_2 \oplus d_3)
 \end{aligned}$$

$\sum m(0,3,5,6)$

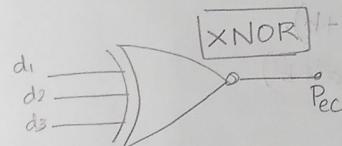


⇒ 3 bit parity generator: (Odd)

d ₁	d ₂	d ₃	P _{og}
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$P_{og} = \sum m(0,3,5,6)$$

↳ even function

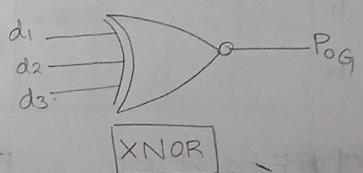

$$* F = ab + a'b'$$

$$F^D = (\overline{a+b}) \cdot (\overline{a+b}) = (\overline{a+b}) \cdot (\overline{a+b})$$

$$F' = (ab + a'b')'$$

$$= (ab)' \cdot (a'b')'$$

$$= (a'+b')(a+b) \cdot$$

F' = Complement each literal in F^D

F^D = change operator

AND \rightarrow OR

OR \rightarrow AND

if constant \rightarrow complement.

* Find F^D of $a'bc + ab'c' + ab$

$$F^D = (a'+b+c)(a+b'+c') \cdot (\overline{a+b})$$

$$F' = (a+b'+c') (a'+b+c) (a'+b')$$

*

ab	cd	00	01	11	10
00		(0)			(0)
01		(0)	0		(0)
11		(0)	0		
10					

$$\underline{F = SOP}$$

$$= \sum m(0, 3, 4, 8, 9, 10, 11, 12, 14)$$

$$F' = \sum m(1, 2, 5, 6, 7, 13, 15)$$

$$F = \prod M(1, 2, 5, 6, 7, 13, 15)$$

$$F' = \prod M(0, 3, 4, 8, 9, 10, 11, 12, 14)$$

for SOP: $F = 1 ; F' = 0$

$$F \cancel{\rightarrow} b \cancel{\rightarrow} d \cancel{\rightarrow} a$$

for POS: $F = 0 ; F' = 1$

$$F = (b+d')(a+c+d')(a+c')$$

$$F = bd + a'c'd' + a'c'd'$$

08/07/2022


UNIT-3

COMBINATIONAL CIRCUITS:

* Design Procedure:


- 1) Identifying I/Ps and O/Ps & assign them label.
- 2) Draw the Truth Table.
- 3) Derive Boolean functions
- 4) Simplify (Reduce no. of literals) function.
- 5) Using gates provided ; design the circuit diagram.

→ O/P is dependent on given I/P.

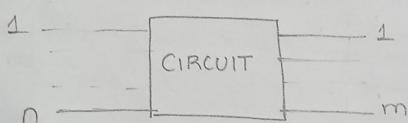

no. of inputs
need not be
equal no. of
outputs.

Analysis:

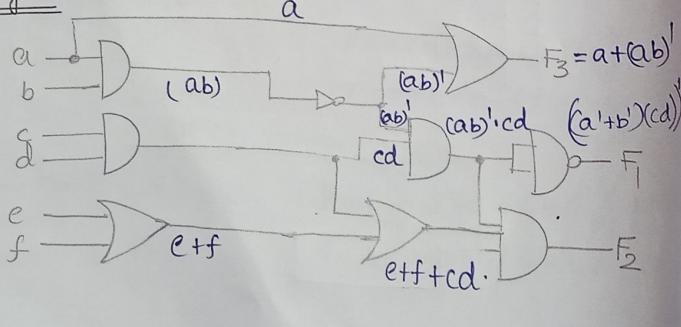

$$F_3 = a + a' + b' = b' + 1 \quad (\text{Simplification})$$

$$F_1 = (a' + b')' + (cd)'$$


$$F_1 = ab + (cd)'$$

$$F_2 = (ab)' cd' (e+f+cd)$$

$$= (ab)' cd'e + (ab)' cd'f + (ab)' cd$$

$$F_2 = (ab)' cd' (e+f+1) = (ab)' cd(e+f)$$

$$F_2 = (ab)' (cd)(e+f)$$

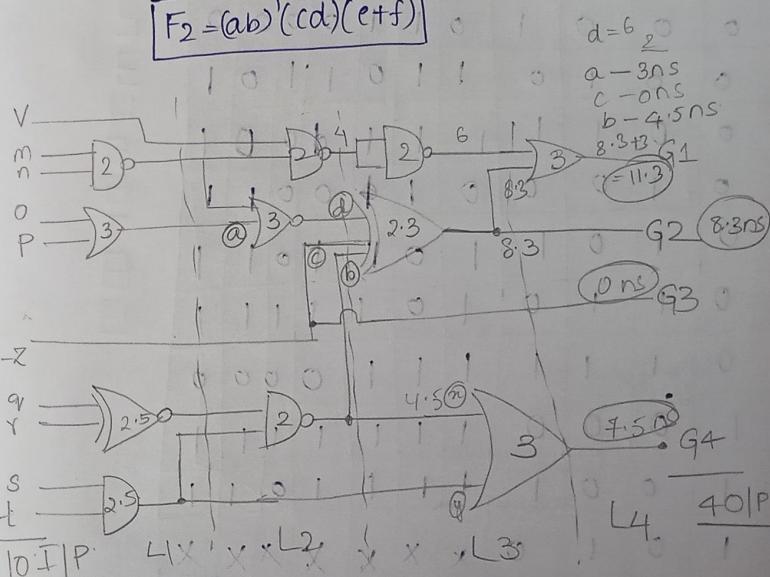

Propagation Delay

Nand - 2ns NOR - 2.5ns

Nor - 3ns

And - 2.5ns


OR - 3 ns

EXOR = 2.3Ns

$$E_4 = [(q \cdot r) st] + st$$

$$(b) + (11'0) = 11$$

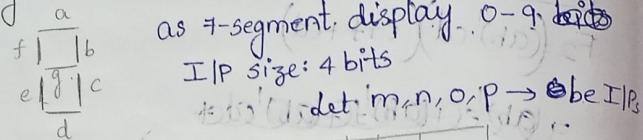* Design a circuit to lit 7-segment display.



$$\begin{aligned} 1 &| 1 & 1 & 1 & 1 & x & x & x & x & x & x \\ a &= \sum m(0, 2, 3, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15) \\ b &= \sum m(0, 1, 2, 3, 4, 7, 8, 9) + d(10, 11, 12, 13, 14, 15) \\ c &= \sum m(0, 1, 3, 4, 5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15) \\ d &= \sum m(0, 2, 3, 5, 6, 8, 9) + d(10, 11, 12, 13, 14, 15) \\ e &= \sum m(0, 2, 6, 8) + d(10, 11, 12, 13, 14, 15) \\ f &= \sum m(0, 4, 5, 6, 8, 9) + d(10, 11, 12, 13, 14, 15) \\ g &= \sum m(2, 3, 4, 5, 6, 8, 9) + d(10, 11, 12, 13, 14, 15) \end{aligned}$$

		00	01	11	10
m	n	1	1	1	1
00	00	1	1	1	1
01	01	1	1	1	1
11	11	X	X	X	X
10	10	X	X	X	X

		00	01	11	10
m	n	1	1	1	1
00	00	1	1	1	1
01	01	1	1	1	1
11	11	X	X	X	X
10	10	X	X	X	X

		00	01	11	10
m	n	1	1	1	1
00	00	1	1	1	1
01	01	1	1	1	1
11	11	X	X	X	X
10	10	X	X	X	X

$$\begin{aligned} a &= \cancel{\alpha z'} + \cancel{\alpha'y'w'} \\ &+ \cancel{\alpha'yw} + \cancel{z} \\ &= \alpha + z + \cancel{\alpha'y'w'} + yw \\ a &= n'p' + m + o + np \end{aligned}$$

$$b = \cancel{\alpha'p}$$

$$b = n' + m + \cancel{m} + o'p' + op$$

$$b = n' + m + o'p' + op$$

$$c = m + n + p + op$$

$$C = m + n + p + o!$$