

It's: Designing of combinational

## logic devices

PLD (Programmable Logic Device)

↳ ROM (Read Only Memory)

↳ PLA (Programmable Logic Array)

↳ PAL (Programmable Array Logic)

Memory:-   
     RAM - volatile   
     ROM - Read

1 Byte = 8 bits


1 KB = 1024 bits =  $2^{10}$

1 MB =  $2^{20}$

1 GB =  $2^{30}$

1 word = 2 Bytes

## Block diagram of memory unit

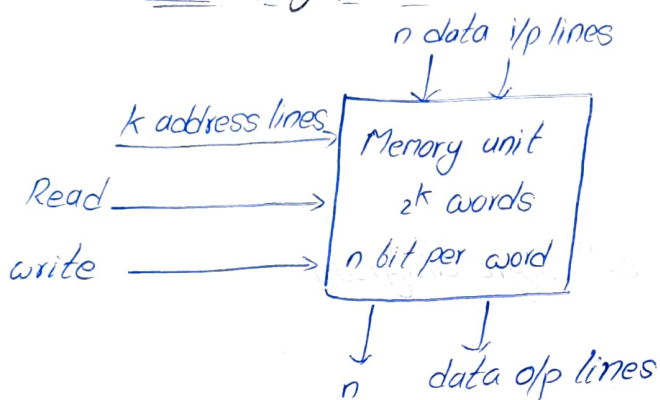


1024 x 16 memory ——— address lines - 10

## memory address

## Memory content

<u>binary</u>	<u>decimal</u>
0000000000	0
0000000001	1
0000000010	2
⋮	⋮
1111111110	1022
1111111111	1023

 

control i/p's to memory chip

memory operation


memory enable

read/write


None

write

read

 


Memory cell logic diagram

 



Block diagram

Diagram of 4x4 RAM

→ input data

 


# ROM block diagram

  

Internal logic diag of 32x8 ROM

## ROM Truth table

<u>Inputs</u>					<u>Output</u>							
$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	1	0	1	1	1	0	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

 


programming ROM using T-T

Q) Design a combinational circuit using ROM. The circuit accepts 3 bit number and o/p's a binary no equal to square of i/p no.

Sol:-

Truth table for given problem

Inputs			Outputs						Decimal
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	0	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

 

Block diagram

ROM Truth table

Inputs			Outputs			
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0


Types of ROM (2M): \*\*\*

- ROM
- PROM - Programmable ROM
- EPROM - Erasable programmable ROM
- EEPROM - Electrical " " ROM


Flash memory

Flash memory devices are similar to EEPROM but have additional built in circuitry to selectively program, and erase the device in circuit without need of a special program.


a) Programmable Read-Only Memory (PROM)

 

b) Programmable array logic (PAL)

 

c) Programmable logic array (PLA)

 

Q) Design a PLA which implements the boolean functions

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$




$$A \oplus 0 = A$$


$$A \oplus 1 = A'$$



 
### a) Programmable Read-Only-Memory (PROM)



### b) Programmable array Logic (PAL)

 


### c) Programmable logic array (PLA)

 

Q) Design a PLA which implements the boolean functions

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

 

Product term		Inputs			Outputs	
		A	B	C	(T) F <sub>1</sub>	(C) F <sub>2</sub>
AB'	1	1	0	-	1	-
AC	2	1	-	1	1	1
BC	3	-	1	1	-	1
A'BC'	4	0	1	0	1	-

Q) Implement the following two boolean functions with PLA

$$F_1(A, B, C) = \Sigma(0, 1, 2, 4)$$

$$F_2(A, B, C) = \Sigma(0, 5, 6, 7)$$

A \ BC	00	01	11	10
0	1	1	0	1
1	1	0	0	0

$$F_1 = \bar{B}\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{C}$$

$$F_1' = AB + AC + BC$$

$$F_1 = (AB + AC + BC)'$$


A \ BC	00	01	11	10
0	1			
1		1	1	1

$$F_2 = AC + AB + \bar{A}\bar{B}\bar{C}$$

PLA programming table

Product term	Inputs			Outputs	
	A	B	C	(C) F <sub>1</sub>	(T) F <sub>2</sub>
AB	1	1	-	1	1
AC	1	-	1	1	1
BC	-	1	1	1	-
A'B'C'	0	0	0	-	1



 

Q) Consider the following boolean functions given in sum of min terms form and design c-c using PAL.

$$w(A, B, C, D) = \Sigma(2, 12, 13)$$

$$x(A, B, C, D) = \Sigma(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \Sigma(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) =$$

