

2) Increase in Bandwidth:

Frequency - Response of an amplifier with & without -ve feedback.

→ Bandwidth is range of frequencies over which gain remains is called bandwidth and it is always measured at -3dB level.

gain in

$$dB = \log \frac{V_o}{V_i}$$

$$dB = \log A$$


$$f_{Lf} = \frac{f_L}{1+AB}$$

$$f_{Hf} = f_H(1+AB)$$

$$BW_f = \frac{BW}{1+AB}$$

f_H = higher cut off frequency without feedback

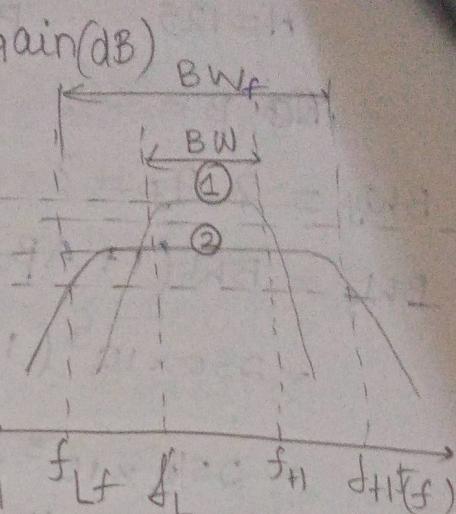f_L = lower cut off frequency without feedback



f_{Lf} = Lower cutoff frequency with feedback

f_{Hf} = Higher cutoff frequency with feedback

⇒ The product of gain & BW of an amplifier with f_B = that of without f_B .

16/02/2022:

Q: An amplifier has open loop gain of 125 and B.W of 250KHz.

(i) If 4% -ve feedback is introduced; find the new bandwidth & gain.

(ii) Band width is restricted to 1MHz; find the feedback ratio.

$$\textcircled{Q} \quad \beta = 4\%$$

(i) $BW_f = ?$ $A_f = ?$

$$BW_f = BW(1 + AB)$$

$$= 250 \times 10^3 \left(1 + \frac{125 \times 4}{100} \right).$$

$$= 250 \times 10^3 \times 6.$$

$$= 150 \times 10^4.$$

$$BW_f = 15 \times 10^5 \text{ Hz}$$

$$BW_f = 1.5 \text{ MHz}$$

$$A_f = \frac{A}{1 + AB} = \frac{125}{6} = \underline{\underline{20.8}}$$

(ii) $BW_f = 1 \text{ MHz}$ $BW = 250 \text{ kHz}$

$$BW_f = BW(1 + AB)$$

$$\frac{10^6}{250 \times 10^3} = 1 + AB$$

$$4 = 1 + AB$$

$$AB = 3.$$

$$\beta = \frac{3}{125} = 0.024.$$

$$\beta = 2.4\%$$

Q: An amplifier has gain of 200 and frequency response from 100Hz to 20kHz. A negative feedback with $\beta = 0.02$ is introduced into the amplifier circuit. Determine the new system.

performance?

$$A_f = 200 \quad BW = 10 \text{ kHz} \quad BW_f = 20 \text{ kHz} \quad B = 0.02$$

$$f_L = 100 \text{ Hz} \quad f_H = 20 \text{ kHz}$$

$$BW = 20000 - 100 = 100(200 - 1) \\ = 19900 \text{ Hz} \\ = 19.9 \text{ kHz}$$

$$BWS = BW(1+AB)$$

$$= 19.9 \times 10^3 (1 + 4)$$

$$= 199 \times 10^2 \times 5$$

$$\boxed{BWF = 99.5 \text{ kHz}}$$

$$f_{LF} = \frac{100}{5}$$

$$f_{AH} = 20 \text{ kHz}$$

$$f_{LH} = \frac{20 \times 5}{5}$$

$$= 100 \text{ kHz}$$

$$A_f = \frac{200}{1 + 4} = \frac{200}{5} = 40$$

$$\boxed{A_f = 40}$$

3) Reduces the Noise:

$$\boxed{N_f = \frac{N}{1+AB}}$$

4) Reduces distortion:

$$\boxed{D_f = \frac{D}{1+AB}}$$

5) Input Impedance increases, and output impedance decreases:

Increasing the I/P impedance of any circuit

reduces loading effect on the source.

Similarly, reducing the O/P impedance improves
O/P ~~sourcing~~ ^{sinking} capability of circuit.

$$Z_{if} = Z_i(1+A_B)$$

$$Z_{of} = \frac{Z_i}{1+A_B}$$

- * An amplifier always uses negative feedback

* OSCILLATORS:

Oscillator is an electronic circuit which is designed to generate a periodic signal of required frequency (specified frequency).

Applications:

- 1) They are used in audio frequency (AF) communication system.
- 2) Radio frequency communication (RF)
- 3) Ultra high frequency ; VHF
- 4) Timing and control circuits
- 5) Timers & clock signals (square wave)

CLASSIFICATION:

- 1) Based on ~~on~~ the type of output signal generated

→ Harmonic : Sinusoidal (Sine function)

→ Non-Harmonic : Triangle, square, ~~etc~~ Sawtooth etc

2) Based on range of frequencies that an oscillator can generate:

- VF : Video frequency ; Audio frequency
- High frequency.
- Micro frequency.

3) Based on the type of feedback circuit:

→ RC oscillators : ~~RC~~ phase shift
• Wein bridge oscillator.

→ LC oscillators:
• Hartley.
• Colpitts.

→ Crystal oscillator:

- Passive components: Resistors, Capacitors; Inductors.
- Active components: Rectifiers, diodes, BJT, FET.

→ Passive components cannot change the signal.
→ Active components can change the type of signal.

17/02/2022

* Conditions for sustained oscillations:

→ Barkhausen's criteria:

$$1) |AB| = 1 \quad \{ [AB = \text{Loop gain}] \rightarrow \text{unity} \}$$

2) Total phase shift around loop must be 0° (or)
 360° . (multiples of 360°)

If the above conditions are not satisfied


and 1) $|AB| < 1 \rightarrow$ damped oscillations

2) $|AB| > 1 \rightarrow$ damped oscillations


3) $|AB| = 1 \rightarrow$ Undamped oscillations

If amplitude of a wave form keeps on changing it turns out to be damped oscillations.


$$|AB| < 1$$

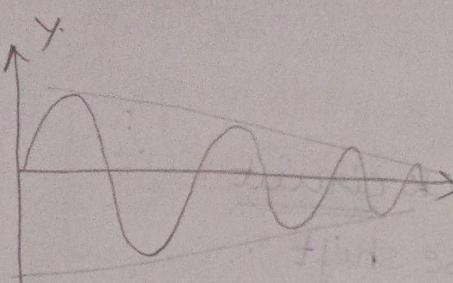

$$|AB| > 1$$

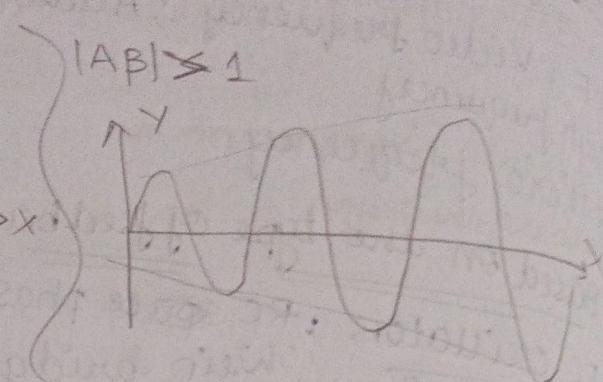



$$|AB| = 1$$

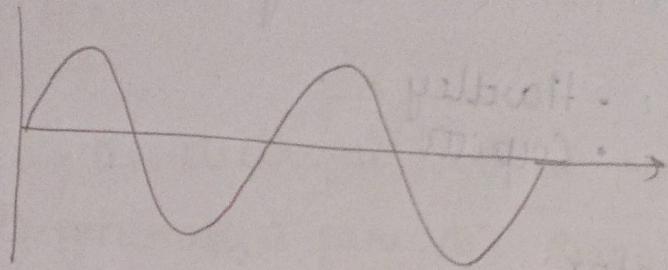

Undamped \Leftrightarrow Sustained oscillator

* GENERAL FORM OF OSCILLATOR:

→ Oscillators use positive feedback.

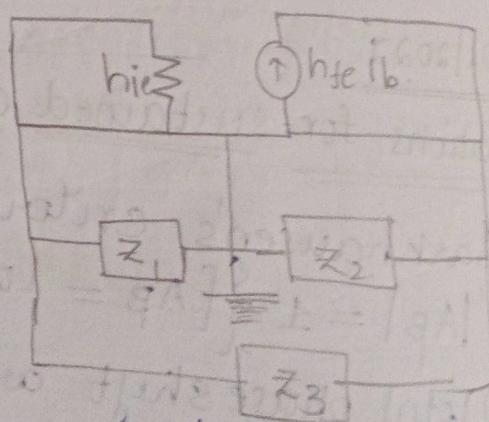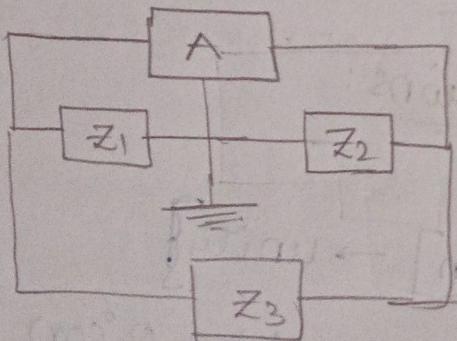

→ An amplifier can be converted into ~~an~~ oscillator; it should be supplying positive feedback.

From the
can be de-
oscillation
following
hie(z)

* HARTLEY


z_1
 z_2
 z_3

hie

From the above general form of oscillator, it can be derived that the condition for sustained oscillations $|AB|=1$ and can be arrived with the following equation

$$h_{ie}(z_1 + z_2 + z_3) + z_1 z_2 (1 + h_{fe}) + z_1 z_3 = 0 \quad (1)$$

* HARTLEY OSCILLATOR:

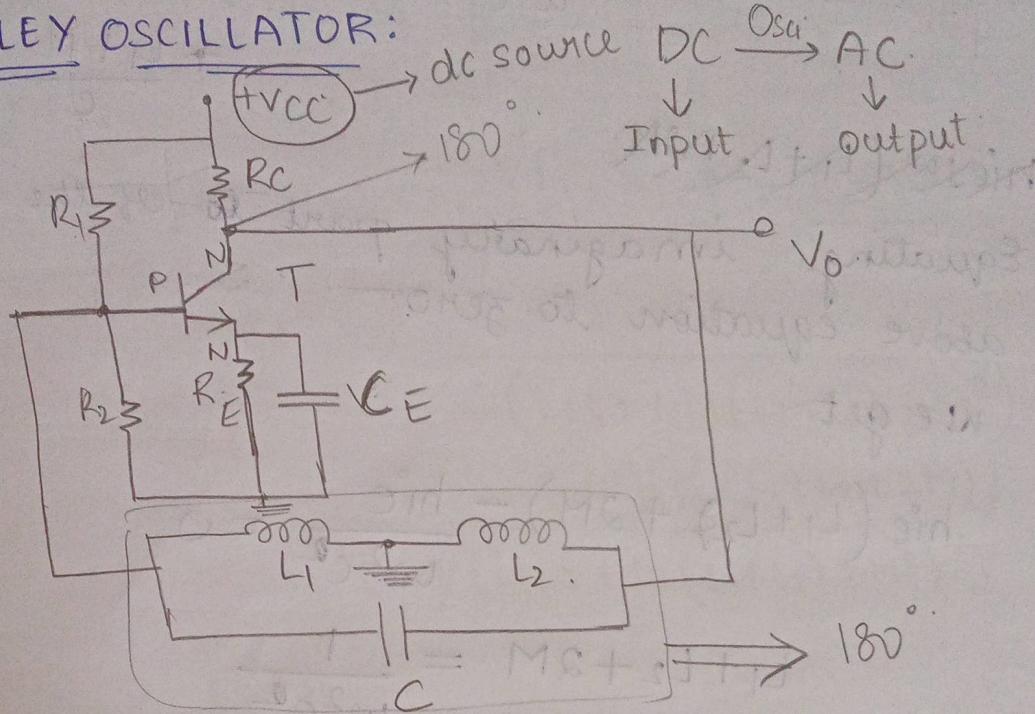

$$z_1 = j\omega L_1 + j\omega M \quad (2)$$

$$z_2 = j\omega L_2 + j\omega M \quad (3)$$

$$z_3 = \frac{1}{j\omega C} \quad (4)$$

total phase

$$\text{Shift} = 180^\circ + 180^\circ \\ = 360^\circ$$

$$h_{ie}(j\omega) \left(L_1 + M + L_2 + M + \frac{1}{j^2\omega^2 C^2} \right)$$

$$+ \left(j^2\omega^2 L_1 L_2 + j^2\omega^2 M L_1 + j^2\omega^2 M L_2 \right) (1 + h_{fe}) \\ + j^2\omega^2 M^2$$

$$+ \frac{L_1}{C} + \frac{M}{C} = 0$$

$$hie j\omega \left(L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right) +$$

$$\oplus \left(-\omega^2 L_1 L_2 - \omega^2 M(L_1 + L_2) - \omega^2 M^2 \right) (1 + h_{fe}).$$

$$hie j\omega \left(L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right) - \omega^2 \left(L_1 L_2 + M(L_1 + L_2) + M^2 \right) (1 + h_{fe}) + \frac{L_1 + M}{C} = 0$$

$$hie j\omega (L_1 + L_2 + 2M)$$

Equating imaginary part of the above equation to zero.

We get.

$$hie (L_1 + L_2 + 2M) - \frac{hie}{\omega^2 C} = 0$$

$$L_1 + L_2 + 2M = \frac{1}{\omega^2 C}$$

$$\omega^2 = \frac{1}{C^2 (L_1 + L_2 + 2M)}$$

$$\boxed{\cancel{\omega = \frac{1}{C(L_1 + L_2 + 2M)}}}$$

$$\boxed{\omega = \frac{1}{\sqrt{C(L_1 + L_2 + 2M)}}}$$

$$2\pi f = \frac{1}{\sqrt{C(L_1 + L_2 + 2M)}}$$

$$f_0 = \frac{1}{2\pi \sqrt{C(L_1 + L_2 + 2M)}} \Rightarrow \text{frequency of output AC signal}$$

Equating real part of eq: ⑤ to zero.

We get

$$\omega^2 (L_1 L_2 + M(L_1 + L_2) + M^2) [1 + h_{fe}] = \frac{L_1 + M}{C}$$

$$\begin{aligned} 1 + h_{fe} &= \frac{L_1 + M}{C(L_1 L_2 + M(L_1 + L_2) + M^2) \omega^2} \\ &= \frac{(L_1 + M) \cancel{\omega^2(L_1 + L_2 + 2M)}}{\cancel{\omega^2(L_1 L_2 + M(L_1 + L_2) + M^2)}} \end{aligned}$$

$$h_{fe} = \underline{\underline{C}}.$$

$$\begin{aligned} h_{fe} &= L_1^2 + L_1 \cancel{L_2} + 2ML_1 + M \cancel{L_1} + M \cancel{L_2} + 2M^2 \\ &\quad - \cancel{L_1 L_2} - M \cancel{L_1} - M \cancel{L_2} - M^2 \\ &\quad \hline L_1 L_2 + M(L_1 + L_2) + M^2. \end{aligned}$$

$$h_{fe} = \frac{\cancel{L_1^2} + 2ML_1 + M^2}{L_1 L_2 + M(L_1 + L_2) + M^2}$$

$$h_{fe} = \frac{(L_1 + M)^2}{(L_1 + M)(L_2 + M)} = \frac{L_1 + M}{L_2 + M}$$

$$\Rightarrow h_{fe} = \beta = \frac{L_1}{L_2}$$

* RC PHASE SHIFT OSCILLATOR:
COLPITTS:


* Hartley can be Colpitts by replacing
 L and C.

∴ There is no mutual

inductance (as

there are no 2 inductors).

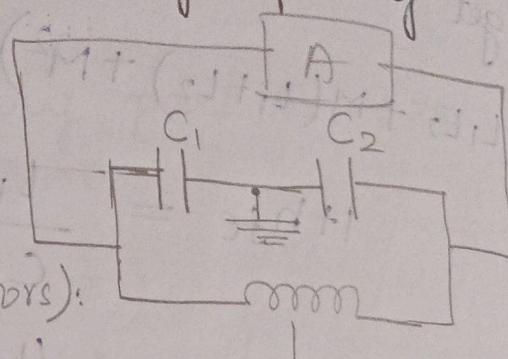2) Capacitors are very small, Size is less, cost also less.
 → No flux.



$$Z_1 = \frac{1}{j\omega C_1}, Z_2 = \frac{1}{j\omega C_2}, Z_3 = j\omega L$$

$$(Z_1 + Z_2 + Z_3)h_{ie} + Z_1 Z_2 (i + h_{fe}) + Z_1 Z_3 = 0$$

$$\frac{h_{ie}}{j^2 \omega^2} \left[\frac{1}{C_1} + \frac{1}{C_2} + j^2 \omega^2 L \right] + \frac{1 + h_{fe}}{j^2 \omega^2 C_1 C_2} + \frac{L}{C_1} = 0$$

$$\omega^2 L = \frac{C_1 + C_2}{C_1 C_2} \quad 1 + h_{fe} = \frac{L}{C_1} (\omega^2 C_1 C_2)$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{L C_1 C_2}}$$

$$h_{fe} = \frac{C_2}{C_1}$$

19/02/20

HARTLEY

Oscillator

(no in

→ All el

tempe


i.e. Δ

ex: R

→ DC

The

RC PHASE SHIFT OSCILLATOR:

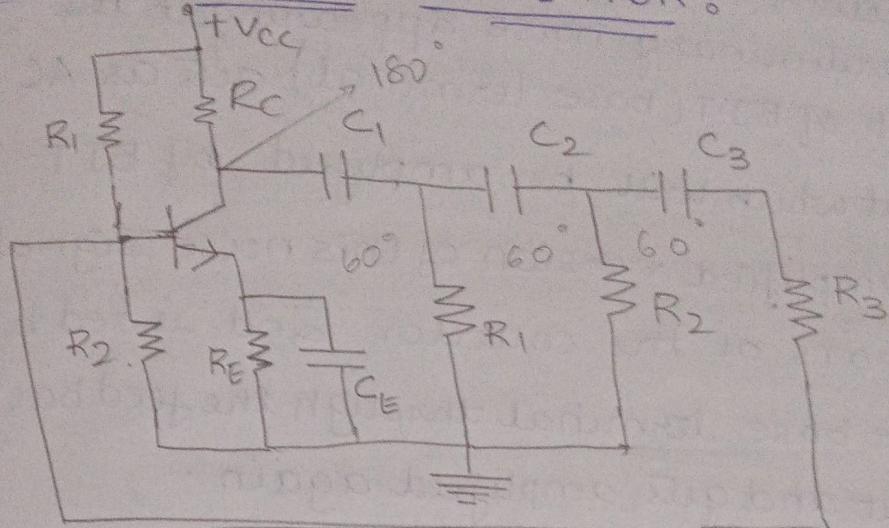

$$\phi = \tan^{-1} \left(\frac{1}{\omega CR} \right)$$

total phase shift = $\frac{1}{\omega CR}$
 $= 180 + 180 = 360^\circ$

$$\therefore R_1 = R_2 = R_3 = R$$

$$C_1 = C_2 = C_3 = C$$

$$f_o = \frac{1}{2\pi RC\sqrt{6}}$$

19/02/2022

HARTLEY OSCILLATOR: working

Oscillators convert DC input to AC output.
 (no input AC supply).

→ All electronic components & devices depend on temperature.

i.e. As temp. varies, their values vary.

Ex: Resistance varies with temp.
 α, β varies with temp in BJT

→ DC power supply V_{cc} also varies.
 These variations introduce noise in the


circuit.

This preliminary noise appearing at the input of BJT (base terminal) acts as AC input which will be amplified by BJT. The amplified version of this noise signal appears at the collector and is fed back to the base terminal through the feedback circuit and gets amplified again. And the procedure repeats.

→ Noise is produced due to the variation in resistances (R_1 & R_2) & V_{CC} acts as AC input.

* We know that;
CE amplifier provides output which is 180° out of phase with input signal i.e. CE configuration output undergoes 180° phase shift (phase reversal occurs).

Only in CE phase reversal takes place

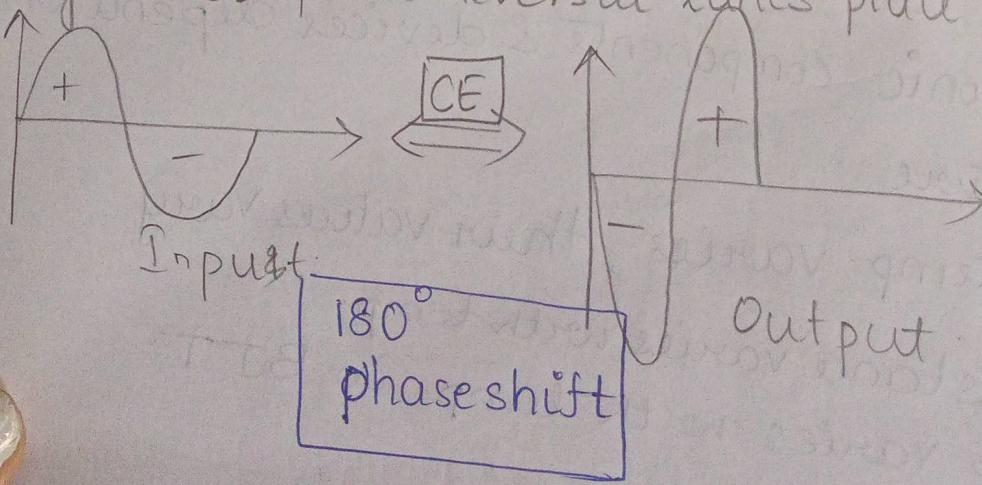

→ Another
By L

23/02/2022

→ Operati
direct
stable

* μA
Multi-stage
I/P

By default

Direct
→ Due to
gain

* It wi
develo
subtr
compo

→ APPLI

• Apar
applic
→ Sia

as AC
by BJT.
use signal
is fed back
feedback.

variation
cts as.

h is
i.e.

80°

→ Another 180° phase shift ~~too~~ is provided
by LC ~~osc~~ feedback/oscillator.


23/02/2022

OPERATIONAL AMPLIFIERS: (OPAMP)

→ Operational amplifier is a multistage, very high gain, direct coupled, -ve feedback amplifier with very high stable gain.

* μA -741 Integrated circuit \Rightarrow 4 amplifiers

Multi-stage:

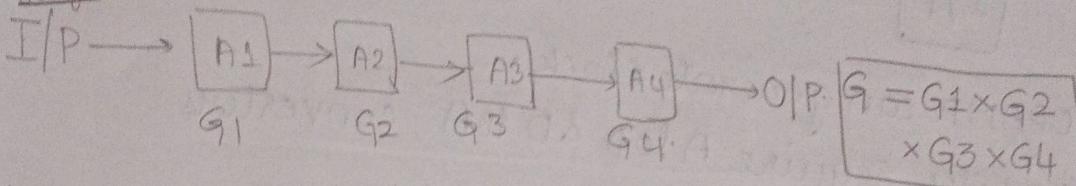

By default, capacitor / inductor / transistor for coupling
↓
Min. requirement for coupling.

Very high gain.

Direct coupling \Rightarrow Only capacitor is used (default).

→ Due to -ve feedback amplifier; it has high stable gain.

* It is called OPAMP because it is originally developed to perform: addition, multiplication, subtraction, ~~and~~ integration, differentiation, comparison.

APPLICATIONS OF OP-AMP:

• Apart from above listed; OPAMP has many applications:


- sign changing
- scale changing

- phase shifting
- oscillator

regulator (Voltage)
 → Control Systems
 → Communication Systems


→ A to D converter
 → D to A
 Analog → A ; Digital → D

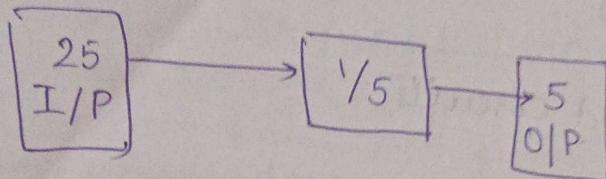- * It can generate square wave, triangular wave,...
- * Design a scale factor; so as to get a required value of output.




- * OPAMP can generate clock.
- * Mobiles require A to D & D to A converters.

* SYMBOL:

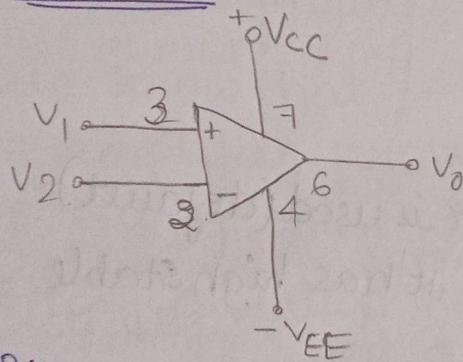

PIN DIAGRAM:

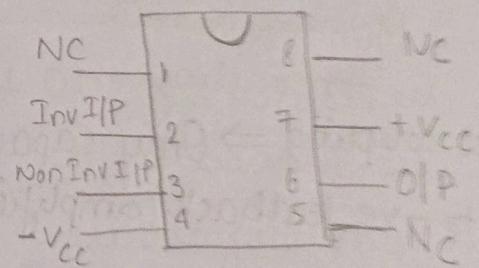

Pin 2 → inverting input → change in sign, wave
 Pin 3 → non-inverting input → change in no sign, wave

-VEE → internally it is using CC configuration
 +VCC → internally it is using CE configuration

* Output of OPAMP (V_o) is given by

$$V_o = A(V_i - V_2)$$

$$= A(V_{id})$$

Differential Input (V_{id})

$$\text{Gain} = \frac{\text{O/P}}{\text{I/P}} = \frac{V_{out}}{V_{in}}$$

Output of Amplifier = Gain times the differential

* IDEAL CHARACTERISTICS OF AN OPERATIONAL AMPLIFIER: 24/02/2022

- Infinite bandwidth
- Infinite Gain
- Infinite CMRR
- Infinite Slew rate
- Infinite I/P Impedance
- zero O/P Impedance
- zero O/P offset voltage.
- No drift characteristics with temperature.

* OPAMP PARAMETERS:

1) Input Offset voltage: / Output offset voltage:

The amount of input voltage required to make the output voltage ~~reaching~~ zero/null (0V) quiescent when both input voltages are equal.

- For μA 741; input offset voltage = 5mV.

2) Input Offset current:

It is the ^{difference} ~~average~~ of 2 input currents flowing in 2 input terminals (2.83).

- For μA741; input offset current = $20nA$

$$i_1 \approx i_2$$

3) Input Bias Current:

The average of 2 input currents I_1 & I_2 .

- For $mA - 741 \Rightarrow 80\text{ nA} = \frac{i_1 + i_2}{2}$

4) CMRR: Common Mode Rejection Ratio:

~~$\text{CMRR} = \left| \frac{A_d}{A_{CM}} \right|$~~

$A_d \rightarrow$ Gain of differential mode. $v_1 \neq v_2$

Noise $\leftarrow A_{CM} \rightarrow$ Gain of Common mode $v_1 = v_2$
 is equal on both terminals $v_1 = v_2$ $\Rightarrow A_{CM} = 0$

$$mA - 741 = 90\text{ dB}$$

CMRR is an ability of an OPAMP ~~to~~ to reject the common mode signals such as thermal noise.

Because CMRR is very high; it is expressed in decibel to reduce the numerical value.
 Ex: $\text{CMRR} = 10^6$;

(Q8)

$$\text{CMRR(dB)} = 10 \log 10^6 \\ = 60$$

$$\boxed{\text{CMRR(dB)} = 10 \log (\text{CMRR})}$$

- Internally; max. noise ~~is~~ is not passed through output.

CMRR is also called figure of merit.

5) Slew

- * gt is voltage
- * gt is a char
- 6) Output
 $\rightarrow O$
 $\rightarrow E$
 $\rightarrow N$


* IDE

5) Slew Rate :

$$SR = \left| \frac{dV_o}{dt} \right|_{\text{max}} \quad \text{1 V/μsec}$$


- * It is the maximum rate of change of output voltage with respect to time (or) frequency.
- * It indicates how fast OPAMP changes its output when there is a change in input.
- 6) Output offset voltage is zero.
 - Offset voltage is not required to balance.
 - Balanced $\Rightarrow V_1 = V_2$
 - No error voltage is required at input.

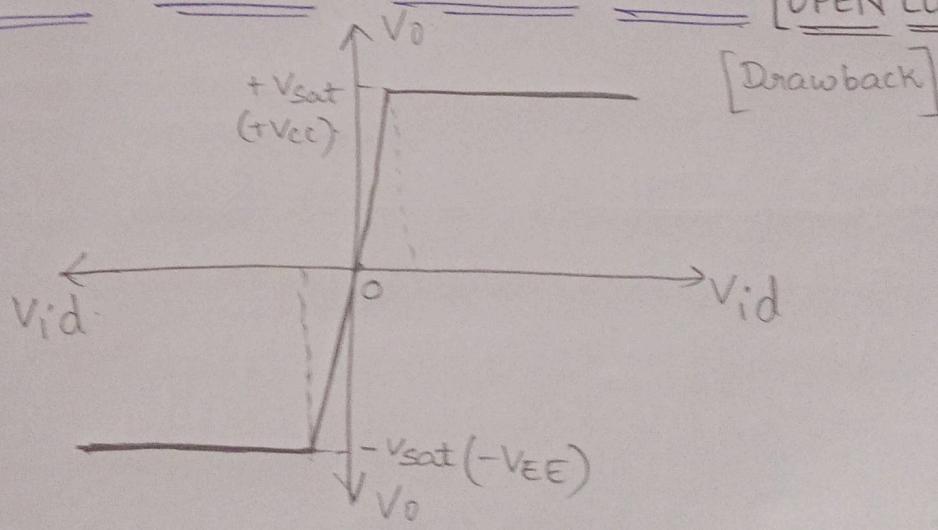* IDEAL VOLTAGE TRANSFER CURVE: [OPEN LOOP]



V_{id} is very small.

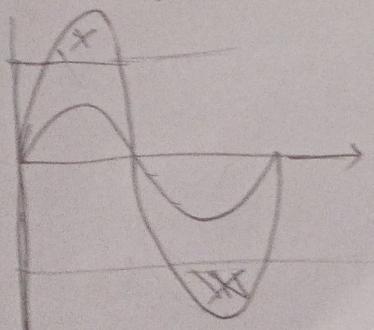V_o can go up to V_{CC} and can go down upto V_{EE}



3) Input Bias Current:

The average of 2 input currents I_1 & I_2 .

$$\text{For } \mu\text{A-741} \Rightarrow 80 \text{nA} = \frac{i_1 + i_2}{2}$$

4) CMRR: Common Mode Rejection Ratio:

$$\text{CMRR} = \left| \frac{A_d}{A_{CM}} \right|$$

$A_d \rightarrow$ Gain of differential mode.

Noise $\leftarrow A_{CM} \rightarrow$ Gain of Common mode

is equal on both terminals $V_1 = V_2$

$$\Rightarrow A_{CM} = 0$$

CMRR is an ability of an OPAMP to reject the common mode signals such as thermal noise.

Because CMRR is very high, it is expressed in decibel to reduce the numerical value.

$$\text{Ex: CMRR} = 10^6$$

$$\text{CMRR(dB)} = 10 \log 10^6 \\ = 60$$

$$\text{CMRR(dB)} = 10 \log (\text{CMRR})$$

Initially, max. noise is not passed through output

CMRR is also called figure of merit

5) Slew Rate:

$$SR = \left| \frac{dV_o}{dt} \right|_{\max} \text{ V/μsec}$$

* It is the maximum rate of change of output voltage with respect to time (or) frequency.

* It indicates how fast OPAMP changes its output when there is a change in input.


6) Output offset voltage is zero.

→ Offset voltage is not required to balance.


$$\rightarrow \text{Balanced} \Rightarrow V_1 = V_2$$

→ No error voltage is required at input

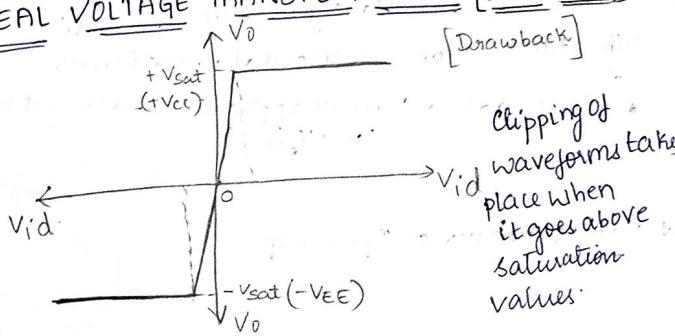* IDEAL VOLTAGE TRANSFER CURVE: [OPEN LOOP]



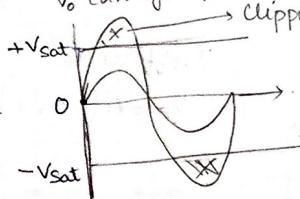V_{id} is very small
V_o can go up to V_{cc} and can go down upto V_{ee}
clipping of waveform



* It can be observed from the output transfer curve that for a small change in input changes V_{id}
output increases rapidly & saturates at +V_{sat} & -V_{sat} as shown. This causes clipping of waveform.

clipping of waveforms take place when it goes above saturation values.

26/02/2022 ∵ OPAMP is used as closed loop for some applications.

* OPAMP IN OPEN-LOOP:

1) Inverting Amplifier

2) Non-inverting Amplifier

3) Differential Amplifier

* DISADVANTAGES OF OPEN-LOOP:

→ Clipping of waveforms.

→ Less Bandwidth.


→ Gain is not stable.

→ It is only used for non-linear applications such as square wave generators & multi

Vibrators: Non-sinusoidal waveforms.


→ Sinusoidal → Linear applications → closed loop (amplifiers).

* CONFIGURATIONS: Open loop:

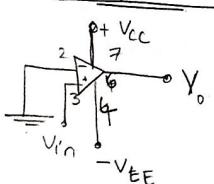


Non-inverting

$$V_0 = A(V_{in})$$

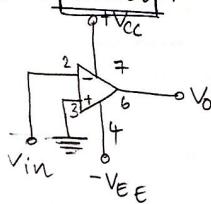

Inverting

$$V_0 = -AV_{in}$$

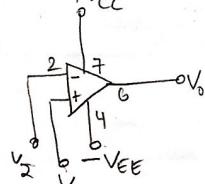

Differential

$$V_0 = A(V_1 - V_2)$$

CLOSED LOOP OPAMP CONFIGURATIONS:

→ VIRTUAL GROUND CONCEPT:

* As we know, gain of OPAMP is very high;

$$\text{Let gain} = 2 \times 10^5 = A$$

$$\text{Let output voltage } V_0 = 10V$$

$$V_{id} = \frac{V_0}{A} = \frac{10}{2 \times 10^5} = 0.5 \times 10^{-4}$$

$$= 5 \times 10^{-5} = 0.05mV$$

→ As we know that input impedance of OPAMP is very high.

assume IP impedance = 2MΩ


$$I = \frac{0.05 \times 10^{-3}}{2 \times 10^6}$$

$$= 2.5 \times 10^{-11}$$

$$I_{in} = 2.5 \times 10^{-2} \text{ nA}$$

$$I_{in} = 0.025 \text{ nA}$$

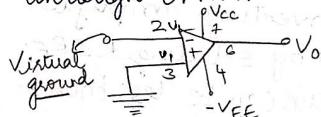* Very small & negligible current is flowing through OPAMP.



* For inverting circuit, 3 is already grounded; but due to above assumptions, 2 is said to be at virtual ground.


* Input voltage $V_{id} = 0.05mV$ and $I_{in} = 0.025 \text{ nA}$ say that input voltage & current are negligible.

$$V_{id} \approx 0 \Rightarrow V_1 = V_2$$

$V_1 \rightarrow$ already grounded

$V_2 \rightarrow$ virtual ground.


* For non-inverting:

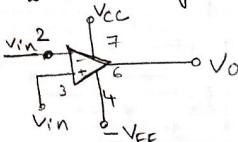

Q2/03/2022

* CLOSED LOOP OPAMP CONFIGURATIONS:

1) Inverting Amplifier:

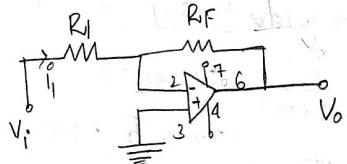

$$i_1 = i_f \text{ (VG concept).}$$

$$\text{pin 2} \Rightarrow \text{VG}$$

$$V_G = 0$$

$$I_G = 0$$


$$\frac{V_i}{R} = \frac{V_G - V_o}{RF}$$

\Rightarrow From the expression
 \rightarrow Gain is $-ve$

\rightarrow User can decide
the gain of
inverting amplifier
 \otimes by selecting R & RF

\rightarrow Gain can be less than 1

2) Non Inverting Amplifier:

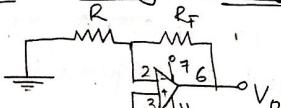


$$V_i = \frac{R_1}{R_1 + R_2} V$$


$$V_2 = \frac{R_2}{R_1 + R_2} V$$

? Only
when
one end
is grounded

Voltage divider:

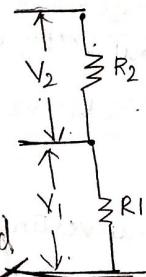

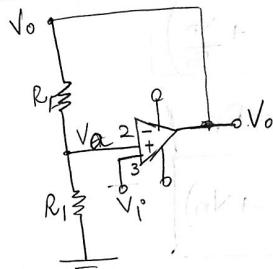As we can from
circuit, Output
is connected back
to pin 2, inverting
input; hence it
 $-ve$ feed back



Voltage across R_1 = Voltage across
pin 2.

$$V_a = \frac{R_1}{R_1 + R_F} V_o$$

$$V_a = \frac{R_1}{R_1 + R_F} V_o$$

Acc. to virtual ground concept

$$V_i = V_a = \frac{R_1}{R_1 + R_F} V_o$$


$$\frac{V_o}{V_i} = \frac{R_1 + R_F}{R_1}$$

$$\frac{V_o}{V_i} = 1 + \frac{R_F}{R_1}$$

Voltage gain in
non-inverting closed loop
amplifier

\rightarrow Gain is $+ve$
 \rightarrow always greater than 1
 \rightarrow User can decide the gain by changing R_1 &
 RF .

3) Adder:

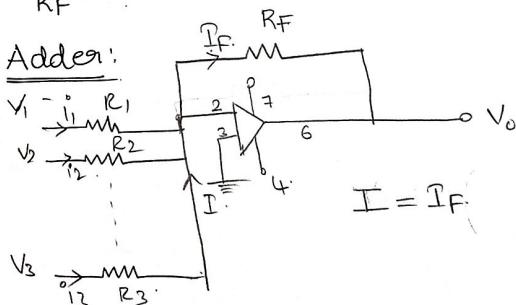

$$I = I_F$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots + \frac{V_n}{R_n} = \frac{V_o}{R_F}$$

$$V_o = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

$$V_o = R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

if $R_1 = R_2 = \dots = R_n$.

$$V_o = \frac{R_F}{R} (V_1 + V_2 + V_3 + \dots + V_n)$$

if $R_F = R \Rightarrow$ gain is 1.

$$V_o = R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$


if $R_1 = R_2 = \dots = R_n$.

$$V_o = \frac{R_F}{R} (V_1 + V_2 + V_3 + \dots + V_n)$$

if $R_F = R \Rightarrow$ gain is 1.

03/03/2022

4) Subtractor:

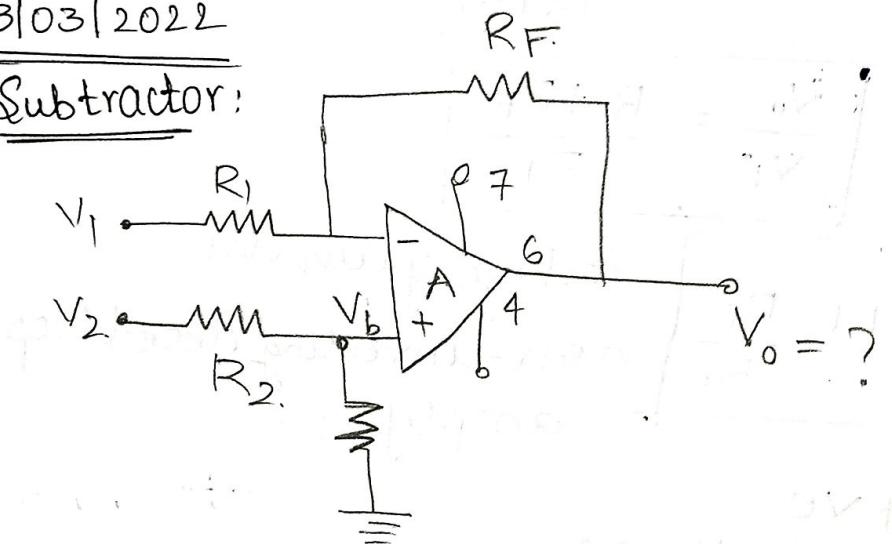

Super-position principle:

let V_{o1} be the o/p when $V_2=0$ (muted)

let V_{o2} be the o/p when $V_1=0$ (muted)

Acc. to superposition principle; o/p V_o is the sum of individual outputs

$$V_o = V_{o1} + V_{o2}$$

$V_1=0 \rightarrow$ Non-inverting

$V_2=0 \rightarrow$ Inverting

$$V_{o1} = -\frac{R_F}{R_1} V_2$$

$$V_{o2} = \left(1 + \frac{R_F}{R_1}\right) V_1$$

$$V_b = \frac{R_3}{R_2 + R_3} V_2$$

$$V_{o2} = \left(1 + \frac{R_F}{R}\right) \left(\frac{R_3}{R_2 + R_3}\right) V_2$$

Assume $R_F = R_1 = R_2 = R_3 = R$

$$V_{o1} = -V_1$$


$$V_{o2} = 2\left(\frac{1}{2}\right)V_2 = V_2$$

$$V_o = V_2 - V_1$$

$$V_o = -V_1 R_F + \frac{(1+R_F)}{2R} V_2$$

5) Differential integrator form:

OPamp constructed as
integrator:

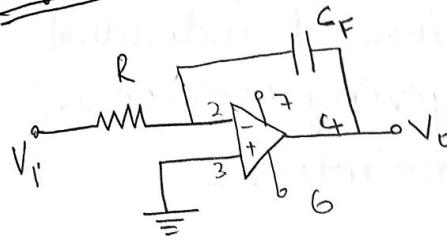

Current through capacitor = $C \frac{d(V_1 - V_2)}{dt}$

$$i = C \cdot \frac{d(V_1 - V_2)}{dt}$$

$$-\frac{V_o}{R} = C_F \frac{d(V_o)}{dt}$$

$$-\frac{1}{RC_F} \int V_o dt = \int dV_o$$

$$V_o = -\frac{1}{RC_F} \int V_o dt$$


$$V_o = -\frac{V_i}{R} \cdot \frac{1}{C \omega}$$

$$V_o = -\frac{V_i}{R} R_F$$

$$= -\frac{V_i}{R} \cdot X_C \quad \omega = \frac{2\pi}{T}$$

$$V_o = -\frac{V_i}{R} \cdot \frac{T}{C \cdot 2\pi}$$

6) Differential

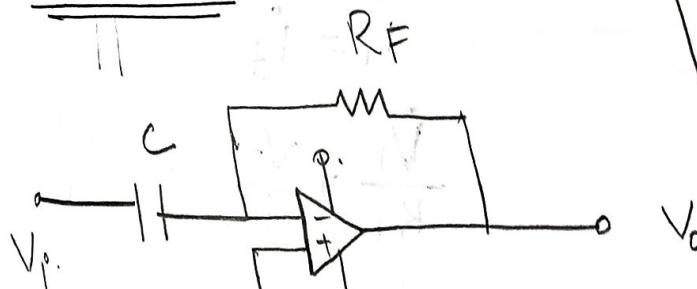

$$\frac{V_o}{R_F} = -\frac{V_i}{X_C}$$

$$-\frac{V_o}{R_F} = C \frac{d(V_i)}{dt}$$

$$V_o = -C \frac{d(V_i)}{dt} \cdot R_F$$

* Opamp can be constructed as differentiator by connecting resistor and capacitor as shown in above circuit.

* Differentiation is decomposing of input i.e. it is used to identify sudden change in input signal.


• Output signal is differential form of input.

* Integration is accumulation of individual points in the signal and giving common level for those ~~sig~~ in that time interval.

* Differentiator \rightarrow High Pass Filter

Integrator \rightarrow Low pass filter

1)

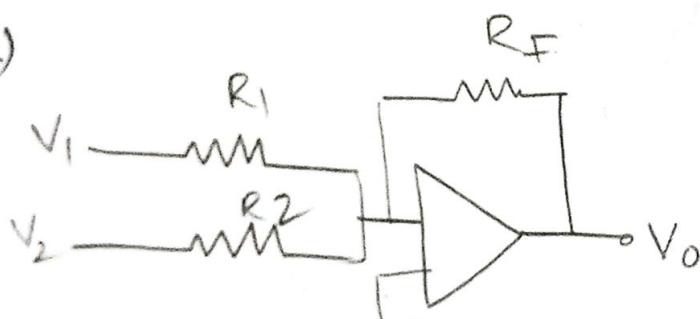

$$R_2 = R_1 = 4\text{ k}\Omega$$

$$R_F = 8\text{ k}\Omega$$

~~Inverting~~

$$\overset{\circ}{i}_1 = \overset{\circ}{i}_f$$

$$\frac{\overset{\circ}{V}_1}{R_1} + \frac{\overset{\circ}{V}_2}{R_2} = -\frac{\overset{\circ}{V}_o}{R_F}$$

$$\frac{V_1}{4} + \frac{V_2}{4} = -\frac{V_o}{8^2}$$


$$V_o = -2(V_1 + V_2)$$

$$V_1 = 5V, V_2 = 3V, V_o = -16V$$

$$V_o = -\frac{R_F}{R} (V_1 + V_2)$$

$$\frac{-R_F}{R} = \frac{-16}{8} = -2$$
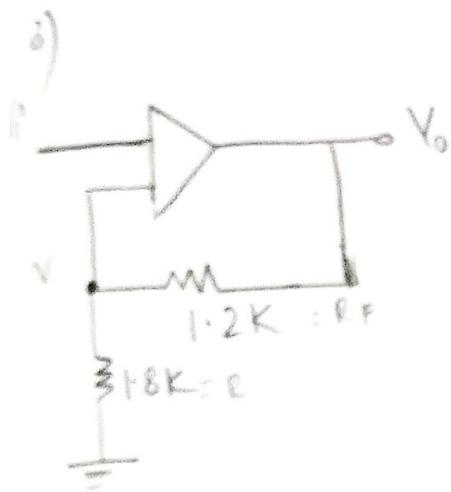
$$\boxed{\frac{R_F}{R} = \text{Gain} = 2}$$



$$V_i = 0.4V$$

$$V_o = 0.4 \left(1 + \frac{1.2}{1.8} \right)$$

$$= 0.4 \left(1 + \frac{2}{3} \right)$$

$$\boxed{\frac{2.0}{3} = 0.66V}$$

4) $R_F = 150k\Omega, V_i = 0.4$

$$\text{Gain} = 3.2.$$

$$1 + \frac{R_F}{R} = 3.2$$

$$R_2 = ?$$


$$R = \frac{150 \times 10^3}{3.2}$$

$$V_o = 3.2 \times 0.4$$

$$\boxed{R = 68.1k\Omega}$$

$$\boxed{V_o = 12.8V}$$

$3k$

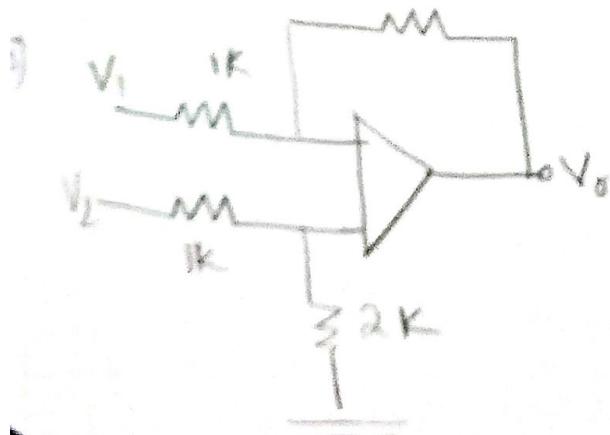

$$V_1 = 2V$$

$$V_2 = 3V$$

$$V_o = ?$$

~~$$V_o = -\frac{3}{1+3} \times 2 + \left(1 + \frac{3}{1} \right) \cdot \left(\frac{3}{3.2} \right) \cdot 3$$~~

$$\begin{aligned}
 V_o &= -\frac{V_1 R_F}{R_1} + V_2 \left(\frac{R_3}{R_2 + R_3} \right) \left(1 + \frac{R_F}{R_1} \right). \\
 &= -\frac{-2 \times 3}{1} + \frac{3}{2} \left(-\frac{2}{3} \right) \times \left(1 + \frac{3}{1} \right) \\
 &= -6 + 8 = 2V
 \end{aligned}$$

