

DC CIRCUITS:

→ Charge (q):

→ Electric current is the rate of change of charge per unit ~~current~~ time.

$$I = \frac{V}{R} \quad i = \frac{dq}{dt}$$

DC → remains constant with respect to time

AC → changes wrt to time periodically.

→ Voltage or potential difference is the energy required to move a charge from one point to another. (Voltage (V))

→ Power is the rate of change of energy per unit time. (Power (W))

$$P = VI$$

$$P = \frac{dW}{dt}$$

$$I = \frac{dq}{dt}$$

$$V = \frac{dW}{dq}$$

→ Energy is the capacity to do work.

→ Independent source: provides current or voltage completely independent of other circuit elements.

→ Dependent source: provides voltage or current which is controlled by another voltage or current.

Types of Independent Sources:

- Voltage Source
- Current Source.

Types of Dependent Sources:

- Voltage dependent voltage source.
- Voltage dependent current source.
- Current dependent current source.
- Current dependent voltage source.

→ Ability to resist the flow of current is called resistance.

→ Ability to the flow of current is called conductance.

$$R = \frac{\rho l}{A}$$

R → resistance
 ρ → resistivity
l → length of conductor
A → area of conductor.

→ According to Ohm's law; voltage (V) across a resistor is directly proportional to current flowing through it.

$$V \propto i$$
$$V = iR$$

* Short circuit: $R \rightarrow 0$; $V = 0$

Open circuit: $R \rightarrow \infty$; $I = 0$

→ $b = l + n - 1$

$b \rightarrow$ branches

$n \rightarrow$ nodes

$l \rightarrow$ independent loops

→ Elements in series \rightarrow same current, diff. voltage.

Elements in parallel \rightarrow same voltage, diff. current.

* KIRCHOFF'S LAW:

KCL: Algebraic sum of incoming (or) outgoing currents at a given node is zero.

KVL: Algebraic sum of voltages around a closed path is zero.

* Voltage Division:

If resistances are in series I is same

$$V_1 = \frac{R_1 V}{R_1 + R_2}; \quad V_2 = \frac{R_2 V}{R_1 + R_2}$$

* Current Division:

If resistances are in parallel; V is same

$$I_1 = \frac{R_2 I}{R_1 + R_2}; \quad I_2 = \frac{R_1 I}{R_1 + R_2}$$

* Method of Analysis:

→ Nodal Analysis (KCL):

Selecting nodes and applying KCL to get current in each branch.

$I =$ high potential to low potential

$$I = \frac{V_{\text{high}} - V_{\text{low}}}{R}$$

* Super Node: A super node is formed by enclosing a voltage source b/w 2 non-reference nodes and an element in parallel with it.

→ Mesh Analysis (KVL):

Applicable only for planar circuits

Mesh is a loop which do not contain any other loop within it.

Apply mesh currents to each mesh and apply KVL to each mesh and we get currents.

* Super Mesh: A super mesh results when 2 meshes have a current source in common.

* Bilateral: Behaves same in any direction

* Unilateral: Behaves different in different directions.

* Linearity: $O/P \propto I/P$.

* Active: Finite amount of power in infinite time.

* Super Position Theorem:

In any linear bilateral active network containing more than one source; the response in any element is equal to the individual responses due to each source.


Voltage sources: Short circuited | Current sources: Open circuited.

* Source Transformation:

Replacing a voltage source in series with resistor by a current source in parallel with resistor or vice versa.

* Thevenin's Theorem

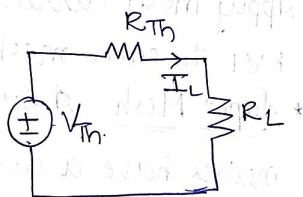This states that any linear bilateral active network can be replaced by an equivalent circuit consisting of voltage V_{Th} with resistor R_{Th} in series.



V_{Th} = open circuiting load terminals & measuring voltage across it.

R_{Th} = Equivalent resistance b/w terminals A & B by replacing sources with their internal resistances.


$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = I_L R_L$$

$$V_L = \frac{R_L V_{Th}}{R_{Th} + R_L}$$

* Norton's Theorem:

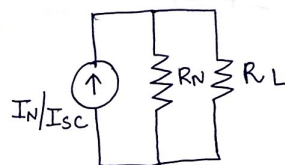This states that any linear bilateral active network can be replaced by an equivalent circuit consisting of current I_N with resistor R_N in parallel.



I_N = short circuiting load terminals & measuring current across it.

R_N = Equivalent resistance b/w terminals A & B replacing sources with IRs.

$$\therefore R_N = R_{Th}$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = R_N$$

* Maximum Power Transfer theorem:

Maximum power will be transferred from source to load when $R_L = R_s / R_{Th}$.


$$P = I_L^2 R_L$$

$$P_{in} = \frac{V_{Th}^2}{2R_{Th}}$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

* Tellegen's Theorem:

$$\sum P = 0$$

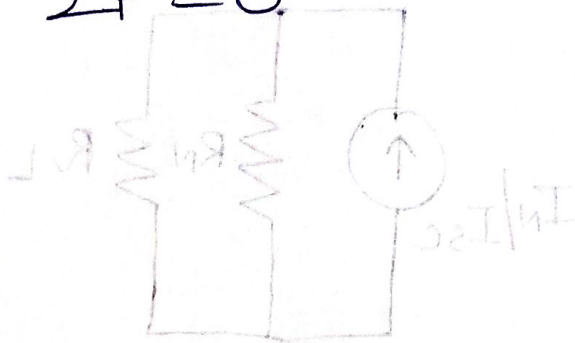

$P = \text{power}$