

19/06/2022

K. SREE INDIRA
SIVANI

BEE ASSIGNMENT-1

1602-21-733-052

CSE-A

1) Following the voltmeter setup of Fig: 2.6; design a voltmeter for the following multiple ranges:

(a) 0-1V (b) 0-5V (c) 0-50V (d) 0-100V.

Assume that the internal resistance $R_m = 2k\Omega$ and the full scale current $I_{fs} = 100\mu A$.

2) Calculate V_0 and I_0 in the circuit. 32V, 800mA

* $70\Omega \parallel 30\Omega$

$$R_1 = \frac{70 \times 30}{100} = 21\Omega$$

Let Voltage across $R_1 \Rightarrow V_1$

* \therefore Resistors 5Ω & 20Ω are \parallel .

$$R_2 = \frac{5 \times 20}{25} = 4\Omega$$

\therefore Voltage across R_2 is V_0

Total current $I = \frac{200}{21+4} = 8A$

current across ' 70Ω ' is I_1

current across 20Ω is I_2

$$V_1 = 21 I_1 = 21 \times 8 = 168V$$

$$V_2 = 4 I_2 = 4 \times 8 = 32V$$

$$I_2 = \frac{32}{20} = 1.6A$$



at C:

$$I_1 = I_0 + I_2$$

$$I_0 = 2.4 - 1.6 = 0.8A = 800mA$$

\therefore Current flowing through 5Ω resistor = 800mA

Voltage across 5Ω is 32V.

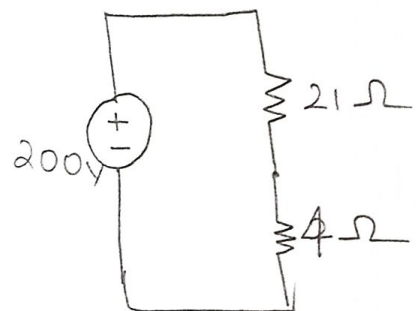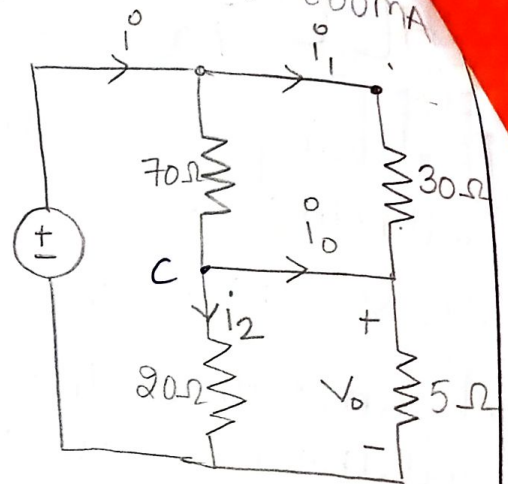

$$I_1 = \frac{V_1}{70} = \frac{168}{70} = \frac{84}{35} = \frac{12}{5}$$

$I_1 = 2.4A$

3) Find I in the circuit:

$$\therefore R_1 = 12\ \Omega$$

$$R_2 = \frac{20 \times 5}{20 + 5} = 4\ \Omega$$

$$R_3 = 15 \parallel (15 \parallel 15)$$

$$= 15 \parallel \left(\frac{15 \times 15}{15 + 15} \right)$$



$$= 15 \parallel \frac{15}{2} \Rightarrow \frac{15 \times 15/2}{15 + 15/2} = 5\ \Omega$$

$$R_4 = 5\ \Omega$$

$$R_5 = \frac{24 \times 8}{24 + 8} = 6\ \Omega$$

$$R_{eq} = 12 + 4 + 5 + 5 + 6 = 32\ \Omega$$
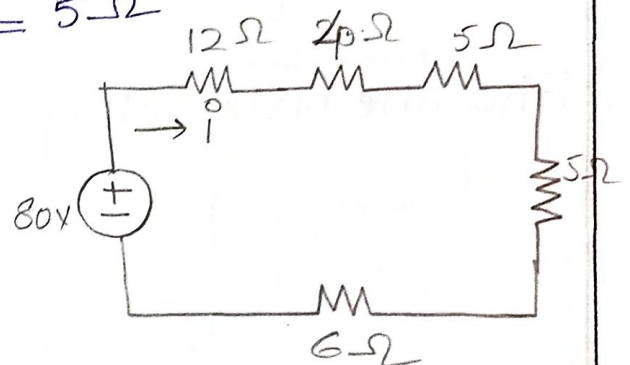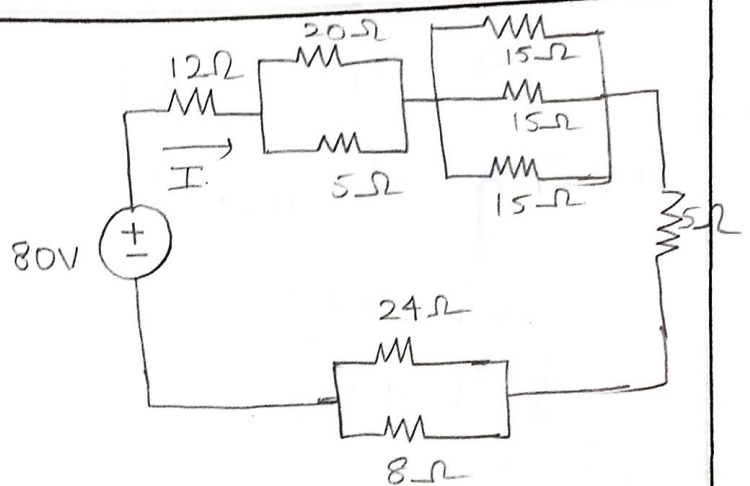
$$I = \frac{80}{32} = \frac{5}{2} = \underline{\underline{2.5\text{A}}}$$



4) For the circuit shown; find the node voltages:

$\therefore V_1, 2V, V_2$ become a supernode

and $10\ \Omega$ resistor is included


\therefore At super node.

Apply KCL

$$2 = \frac{V_1 - 0}{2} + \frac{V_2 - 0}{4} + 7$$

$$-5 = \frac{2V_1 + V_2}{4}$$
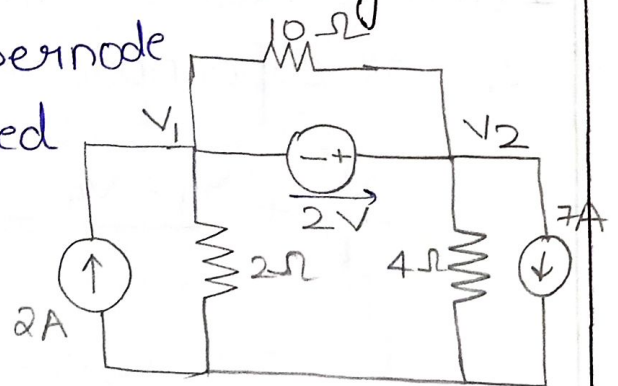
$$\boxed{2V_1 + V_2 = -20} \quad \text{--- (1)}$$



$$V_2 - V_1 = 2V \quad \text{--- (2)}$$

Solving V_1 and V_2

$$2V_1 + V_2 = -20$$

$$-V_1 + V_2 = 2$$

$$3V_1 = -22$$


$$V_1 = -7.33V$$

$$V_2 = 2 + V_1$$

$$= 2 - 7.33V$$

$$V_2 = -5.33V$$

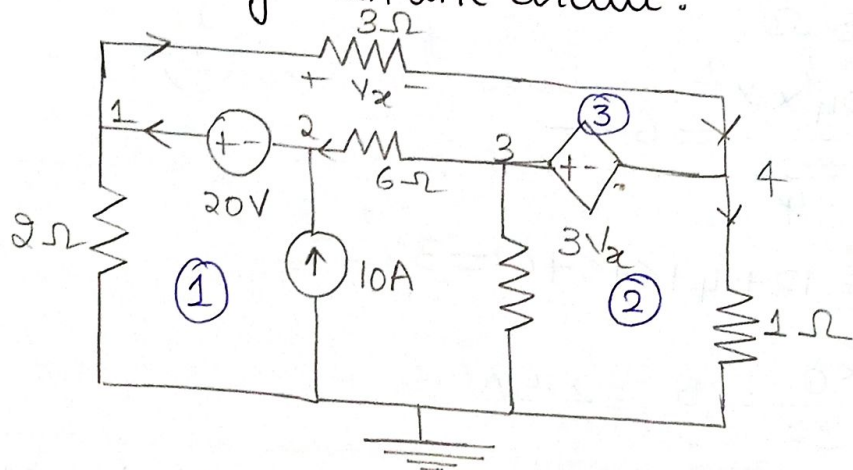5) Find the node voltages in the circuit:



1 and 2 nodes forms a super node:

∴ at super node apply KCL

$$\frac{V_1}{2} + \frac{V_1 - V_4}{3} = 10 + \frac{V_2 - V_3}{6}$$

$$3V_1 + 2V_1 - 2V_4 = 60 + V_2 - V_3$$

$$5V_1 + V_2 - V_3 - 2V_4 = 60 \quad \text{--- (1)}$$

$$V_1 - V_2 = 20 \quad \text{--- (2)} \quad V_1 = 20 + V_2$$

* 3 and 4 form a supernode
at super node; apply KCL

$$\frac{V_3}{4} + \frac{V_3 - V_2}{6} + \frac{V_4}{1} = \frac{V_1 - V_4}{3}$$

$$3V_3 + 2V_3 - 2V_2 + 12V_4 = 4V_1 - 4V_4$$

$$4V_1 - 5V_3 + 2V_2 - 16V_4 = 0 \quad \text{--- (3)}$$

$$V_3 - V_4 = 3V_x \quad \text{--- (4)}$$

~~Apply KVL in each loop~~

①

$$V_x = V_1 - V_4$$

$$V_3 - V_4 = 3V_1 - 3V_4$$

$$3V_1 - V_3 - 2V_4 = 0$$

$$V_1 = V_2 + 20$$

$$3V_2 - V_3 - 2V_4 = -60 \quad \text{--- (6)}$$

$$6V_2 - 5V_3 - 16V_4 = -80 \quad \text{--- (7)}$$

Solve (5), (6), (7) to get V_2, V_3, V_4 .

$$V_2 = +16.67V \quad V_3 = 13.33V \quad V_4 = -16.66V$$

$$V_1 = 26.67V$$

① becomes

$$100 + 5V_2 + V_2 - V_3 - 2V_4 = 0$$

$$6V_2 - V_3 - 2V_4 = -100 \quad \text{--- (5)}$$

5) For the bridge network ; find i_o using mesh analysis.

\therefore ① forms a Wheat-stone bridge

\therefore $2k\Omega$ resistor can be ignored.

$$\therefore R_1 = 2k\Omega$$

~~R_2~~

For mesh ①

$$+56 - 2i_1 - 6(i_1 - i_2) - 4(i_1 - i_3) = 0$$

$$56 = 12i_1 - 6i_2 - 4i_3 \Rightarrow \boxed{6i_1 - 3i_2 - 2i_3 = 28} \quad \text{--- ①}$$

For mesh ②

$$-6(i_2 - i_1) - 6i_2 - 2(i_2 - i_3) = 0$$

$$-14i_2 + 6i_1 + 2i_3 = 0$$

$$\boxed{3i_1 - 7i_2 + i_3 = 0} \quad \text{--- ②}$$


For mesh ③

$$-2(i_3 - i_2) - 4i_3 - 4(i_3 - i_1) = 0$$

$$-10i_3 + 2i_2 + 4i_1 = 0$$


$$\boxed{2i_1 + i_2 - 5i_3 = 0} \quad \text{--- ③}$$
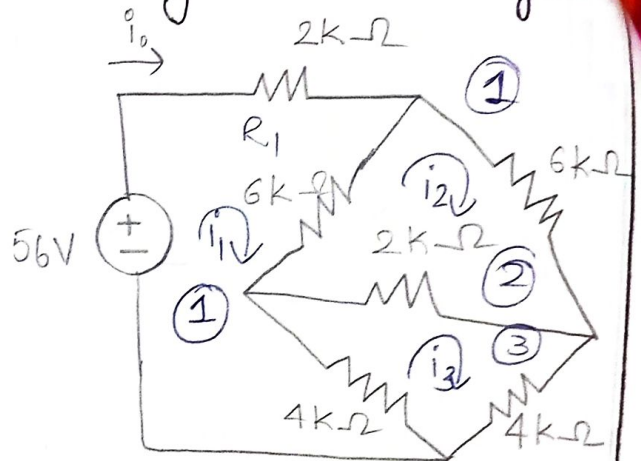
$$\boxed{\begin{aligned} i_1 = i_o &= 8\text{mA} \\ i_2 = i_3 &= 4\text{mA} \end{aligned}}$$



Find the Thevenin equivalent of the circuit at terminals a and b.

i) Remove current source:

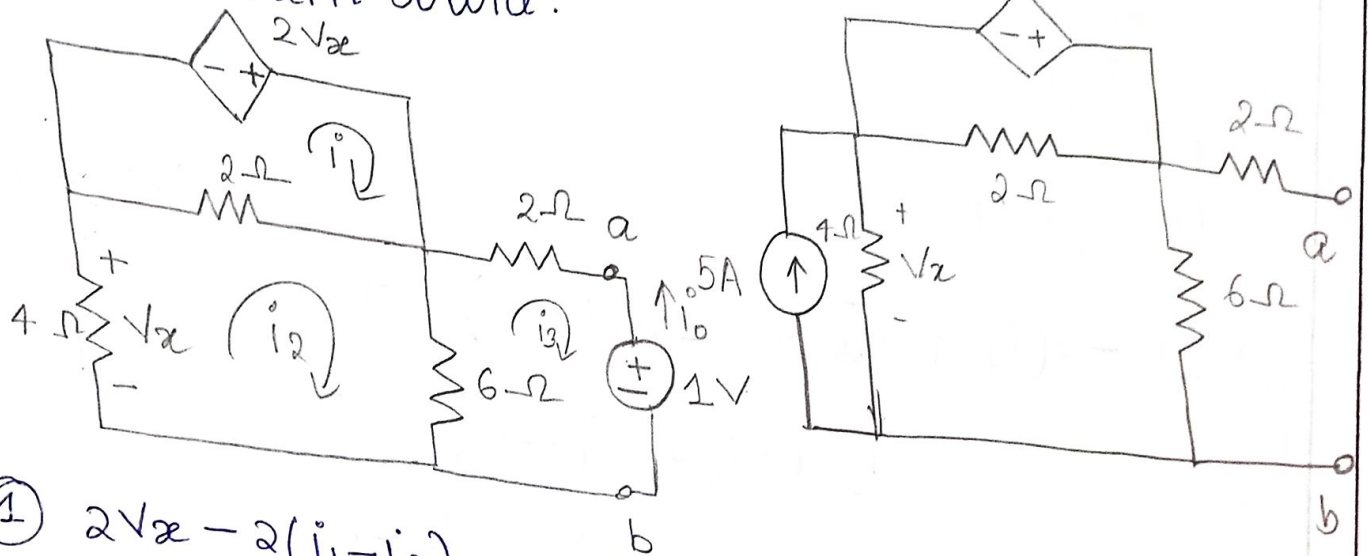

$$\textcircled{1} \quad 2V_x - 2(i_1 - i_2) = 0$$

$$V_x = i_1 - i_2 = -4i_2$$

$$i_1 = -3i_2$$

$$\textcircled{2} \quad -4i_2 - 2(i_2 - i_1) - 6(i_2 - i_3) = 0$$

$$-12i_2 + 2i_1 + 6i_3 = 0$$

$$6i_2 - i_1 - 3i_3 = 0$$

$$6i_2 + 3i_2 - 3i_3 = 0$$

$$9i_2 = 3i_3$$

$$i_3 = 3i_2$$

$$\textcircled{3} \quad -6(i_3 - i_2) - 2i_3 - 1 = 0$$

$$-8i_3 + 6i_2 - 1 = 0$$

$$8i_3 - 6i_2 + 1 = 0$$


$$24i_2 - 6i_2 + 1 = 0$$

$$i_2 = -1/18 \text{ A}$$

$$i_3 = -\frac{1}{6} \text{ A}$$

$$i_1 = +\frac{1}{6} \text{ A}$$
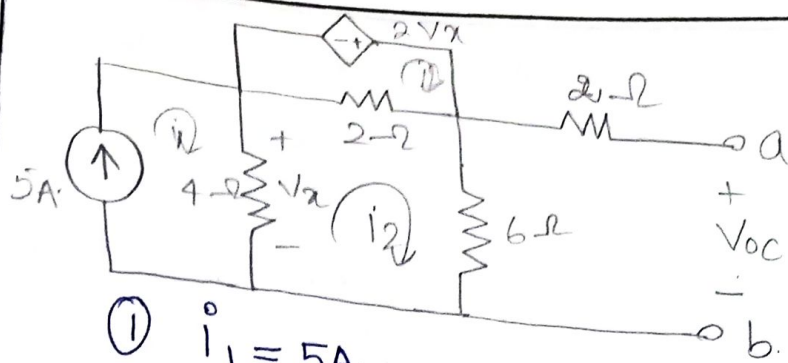
$$R_{Th} = \frac{1 \text{ V}}{-1/6} = \underline{\underline{6 \Omega}}$$



$$\textcircled{1} \quad i_1 = 5A$$

$$\textcircled{2} \quad -2(i_2 - i_3) + V_{oc} - 4(i_2 - i_1) = 0$$

$$V_{oc} = 6i_2$$

$$-6i_2 + 2i_3 + 4i_1 - 6i_2 = 0$$

$$6i_2 - 2i_3 - 4i_1 + 6i_2 = 0$$

$$6i_2 - i_3 - 2i_1 = 0$$

$$\boxed{6i_2 - i_3 = 10}$$

$$\textcircled{3} \quad -2V_x + 2(i_3 - i_2) = 0$$

$$i_3 - i_2 = V_x$$

$$4(i_1 - i_2) = V_x$$

$$4(5 - i_2) = V_x$$

$$i_3 - i_2 = 20 - 4i_2$$

$$3i_2 + i_3 = 20$$

$$6i_2 - i_3 = 10$$

$$9i_2 = 30$$

$$\boxed{i_2 = \frac{10}{3} A}$$

$$\cancel{i_2} \cdot V_{oc} = 6i_2$$

$$= 6 \times \frac{10}{3}$$



$$\boxed{V_{oc} = 20V}$$

7) Obtain V_o in the circuit using source transformation
 Convert current sources $3A$, $2A$, and $5A$ into
 voltage source forming single mesh.

$$\Rightarrow V_1 = 3 \times 4 = 12V$$

$$V_2 = 5 \times 6 = 30V$$

$$V_3 = 9 \times 2 = 18V$$

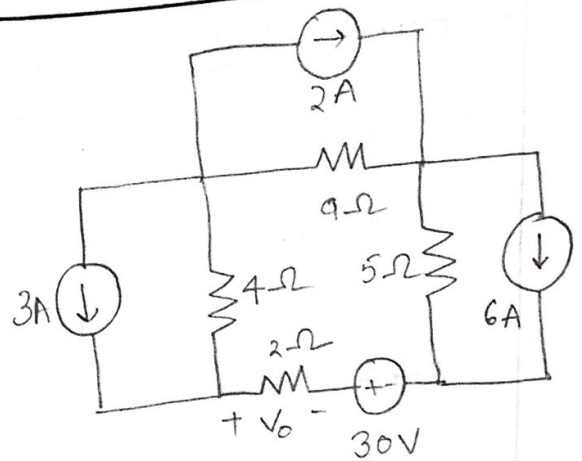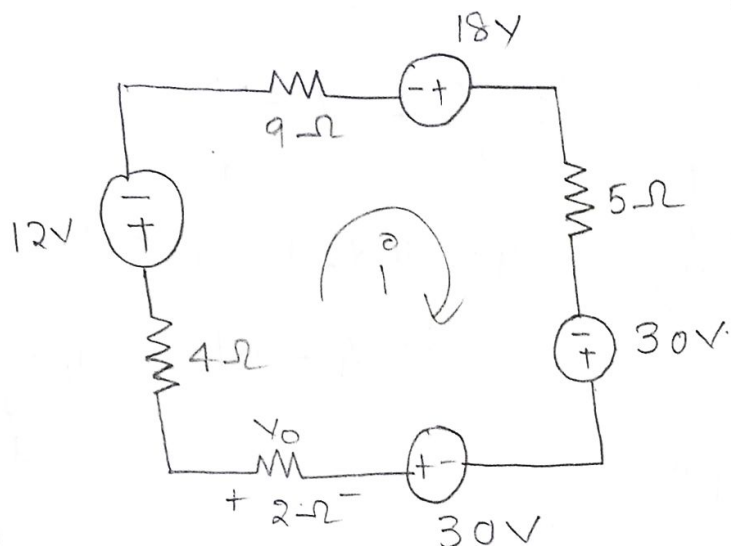

Applying KVL

$$-4i - 12 - 9i + 18 - 5i + 30 + 30 - 2i = 0$$



$$-i(20) + 66 = 0$$

$$i = \frac{66}{20} = \frac{33}{10}$$

$$i = 3.3A$$

$$V_0 = 2i = 6.6V$$

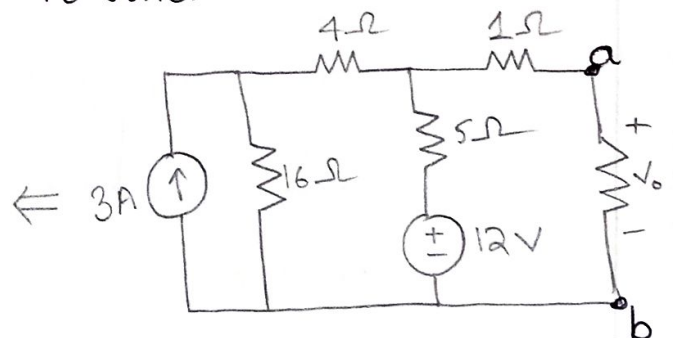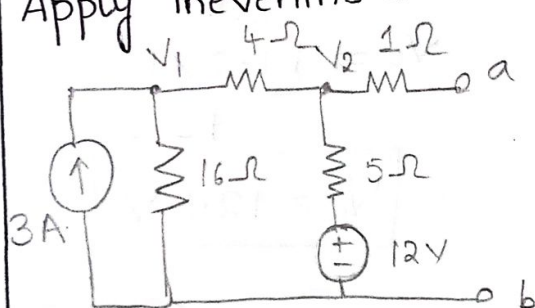8) Apply Thevenin's theorem to find V_0 in the circuit



Apply Nodal analysis:

at V_1

$$3 = \frac{V_1}{16} + \frac{V_1 - V_2}{4}$$

$$48 = V_1 + 4V_1 - 4V_2$$

$$\boxed{5V_1 - 4V_2 = 48}$$

— (1)

Solve (1) & (2)

$$5V_1 - 4V_2 = 48$$

$$-5V_1 - 9V_2 = -48$$

$$5V_2 = 96$$

$$V_2 = \frac{96}{5} = 19.2 \text{ V}$$

at V_2

$$-\frac{V_2 - 12}{5} + \frac{V_2 - V_1}{4}$$

$$\frac{12 - V_2}{5} + \frac{V_1 - V_2}{4} = 0$$

$$48 - 4V_2 + 5V_1 - 5V_2 = 0$$

$$\boxed{5V_1 - 9V_2 = -48}$$

— (2)

$$\boxed{V_2 = V_{Th} = 19.2 \text{ V}}$$

For R_{Th}


$$(1+5) \parallel (4+16) = 1 + (5 \parallel (4+16))$$

$$= 6 \parallel 20$$

$$R_{Th} = \frac{6 \times 20}{26} = 1 + 4 = 5 \Omega$$


For R_{Th}

$$= 1 + \frac{5 \times 20}{25}$$

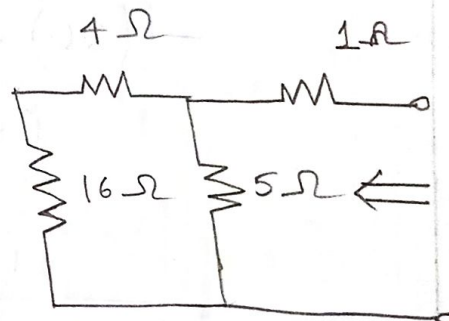

$$\boxed{R_{Th} = 5 \Omega}$$

\Rightarrow

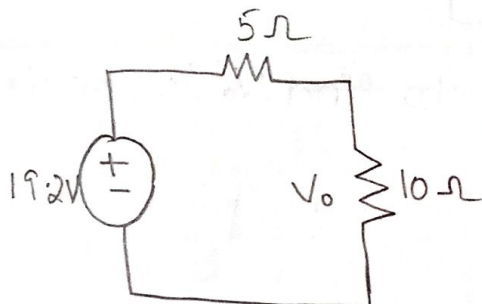

$$V_o = \frac{6.4}{1+5} \times 10$$

$$\boxed{V_o = 12.8 \text{ V}}$$

7) determine the maximum power that can be delivered to the variable resistor R .

Thevenin's equivalent at R

$$R_{Th} = 10 \parallel 20 + 25 \parallel 5$$

$$= \frac{10 \times 20}{30} + \frac{25 \times 5}{30}$$

$$= \frac{20}{3} + \frac{25}{6}$$


$$R_{Th} = \frac{65}{6} \Omega$$

$$V_a - V_{Th} - V_b = 0$$

$$V_{Th} = 30V$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(30)^2 \times 6}{4 \times 65} = \frac{180 \times 90}{4 \times 65} = \frac{270}{13}$$

$$P_{max} = 20.77W$$

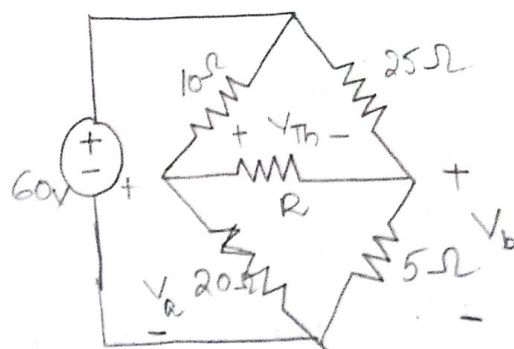

Voltage division Rule:

$$V_a = \frac{20}{30} \times 60$$

$$V_a = 40V$$

$$V_b = \frac{5}{30} \times 60$$

$$V_b = 10V$$

- 10) The Thevenin equivalent at terminals a-b of the linear network shown is to be determined by measurement. When a $10\text{ k}\Omega$ resistor is connected to terminals a-b; the voltage V_{ab} is measured as 6V. When a $30\text{ k}\Omega$ resistor is connected to terminals a-b, V_{ab} is measured as 12V. Determine
- (a) The Thevenin equivalent at terminals a-b
 - (b) V_{ab} when a $20\text{ k}\Omega$ resistor is connected to terminals a-b.