

$$500 = \frac{50 \times 10^{-3} \times 2 \times N \times 8}{2 \times 8}$$


$$500 = \frac{50 \times 10^{-3} \times 2 \times N \times 8}{2 \times 8}$$

$$N = \frac{10^4}{8} = \frac{2500}{2} = 1250 \text{ rpm}$$

03/08/2022
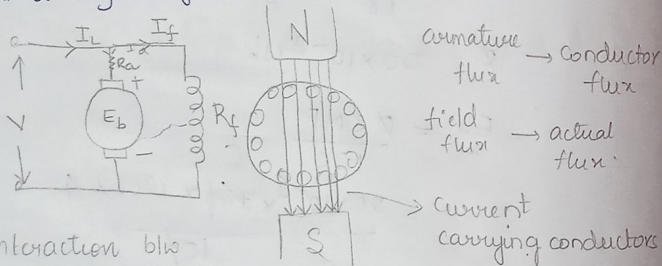
### \* DC MOTOR:

Whenever we place a current carrying conductor in a magnetic field, there is a force developed.



Interaction b/w armature & field flux

$$I_L = I_a + I_f$$

$$V = I_a R_a + E_b \rightarrow \text{back emf: opposes the source voltage}$$

$$V - I_a R_a - E_b = 0$$

SHUNT MOTOR:

$$E_b = V - I_a R_a$$


$$I_a = \frac{V - E_b}{R_a}$$

$$E_b = \frac{\phi Z N}{60} \times \frac{P}{A}$$

$$\phi E_b = 0 ; N = 0$$

$$I_a = \frac{V}{R_a}$$

\*  $E_b$  controls the current  $I_a$

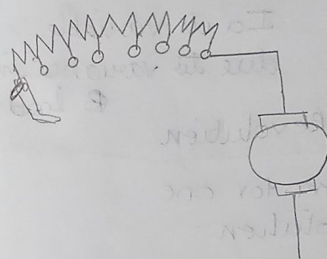

Starter is used to limit the starting

current.

$$I_a = \frac{V - E_b}{R_a}$$

\* Also at the beginning  $E_b = 0$


$\therefore$  current  $I_a$  is

very high; to control this current, starter is used

$$I_a = \frac{V}{R_a}$$

\* We need to limit the starting current to avoid the damage to the circuit

### \* SERIES MOTOR:

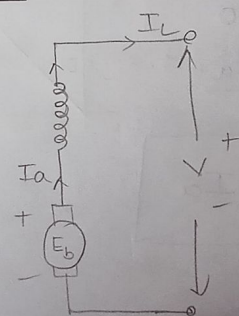

$$I_L = I_{sc} = I_a$$


$$E_b - I_a R_a - V = 0$$

$$E_b = I_a R_a + V$$

$$I_a = \frac{E_b - V}{R_a}$$

06/08/2022

# \* TORQUE / N DC MOTOR:

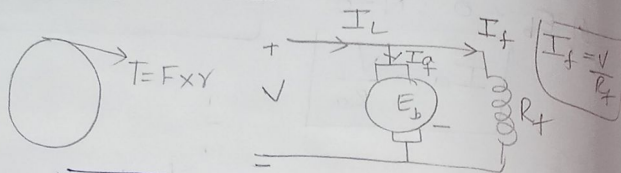

$$P_m = E_b I_a$$

$I_a$  is variable due to variance in load.

Power =  $\frac{\text{Workdone / Revolution}}{\text{Time taken for one revolution}}$

$$= \frac{(F \times 2\pi r) \times \frac{1}{60/N}}{1} = (Fr) \frac{2\pi N}{60}$$

$$= Fr \cdot 2\pi f = (Fr) \omega$$

$$P = T \omega$$


$$E_b I_a = T \omega$$

$$\frac{P \phi N}{60} \times \frac{Z}{A} I_a = T \cdot \frac{2\pi N}{60}$$

$$T = \frac{P \phi Z I_a}{2\pi A}$$

$$T = \frac{Z P}{2\pi A} \phi I_a$$

$$T \propto I_a$$

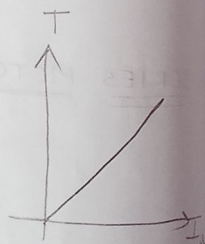


$$E_b = \frac{\phi Z N}{60} \times \frac{P}{A}$$

$\phi$  varies with  $I_f$   
 $N \rightarrow$  varies.


$$N \propto \frac{E_b}{\phi}$$

$$N \propto V - I_a R_a$$

$$E_b = V - I_a R_a$$

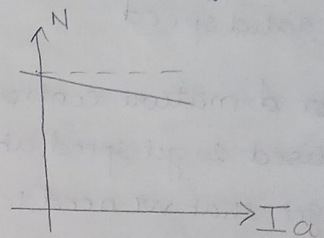


$$N \propto \sqrt{s} T$$

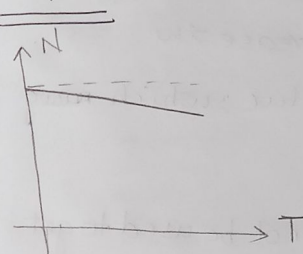

## \* Speed control of DC shunt motor (or) Separately excited DC Motor.

- We need start the circuit with a minimum speed.

$$N \propto \frac{E_b}{\phi}$$

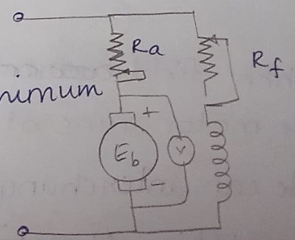

$V_a$  can be varied with armature resistance  $R_a$  at max and  $R_f$  is max to start the circuit with min speed.



→ When the rated voltage and ~~rated~~ field current are applied; we get the rated speed.

~~for~~ Armature control method cannot be used to get speed above rated value. To get that we need to increase the resistance over rated value; which ~~may~~ will damage the circuit.


Field control method cannot be used to get speed below rated value. To get that we need to increase the resistance over rated value.

\* When field ~~current~~ windings are opened the motor runs at a very high speed.

\* We can interchange the direction of the rotation of motor by either interchanging the armature (or) field polarities.

10/08/2022

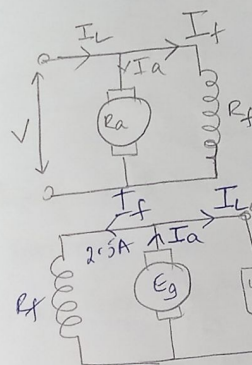\*  $V = 250V$      $R_a = 0.12\Omega$      $R_f = 100\Omega$   
 $I_L = 80A$



$$I_f = \frac{V}{R_f}$$

$$= 2.5A$$

$I_a = 77.5A$  Flux in a shunt motor is constant due to constant  $V$  &  $I_f$

$$\frac{\text{Speed as generator}}{\text{Speed as motor}} = ?$$

Motor:  $N_m \propto E_b$   
 Generator:  $N_g \propto E_g$

$$E_b = V - I_a R_a$$

$$= 250 - 77.5 \times 0.12$$

$$= 240.7V$$

$$E_g = V + I_a R_a$$

$$= 250 + 82.5 \times 0.12$$

$$= 259.9V$$

$$\frac{N_g}{N_b} = \frac{259.9}{240.7} = 1.08$$

\*  $V = 200V$      $R_a = 0.4\Omega$      $I_a = 2A \rightarrow$  no load current

$I_a = 50A \rightarrow$  Loaded conditions.  
 $N = 1200 \text{ rpm}$

$$E_o = V - I_a R_a = 200 - 2 \times 0.4$$

$$= 200 - 0.8$$

$$= 199.2V$$

$$E_i = V - I_a R_a = 200 - 50 \times 0.4$$

$$= 200 - 20 = 180V$$

$$N \propto \frac{E_b}{\phi}$$


$$\frac{N_1}{N_0} = \frac{E_d}{E_0}$$

$$N_0 = \frac{1200 \times 199.2}{180}$$

$$= \underline{1328 \text{ rpm}}$$

10/08/2022

## TRANSFORMER

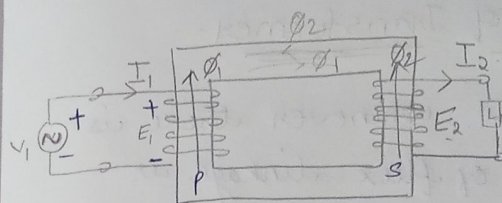

$E_1$  = Self induced emf

$\therefore$  emf is induced due to the source

The transformer just step up or down the voltage; but total power on either side remains same  $V_1 I_1 = V_2 I_2$

Due to the flux developed in primary coil there is a flux developed in secondary coil;  $E_2$  = Mutually induced emf

Principle: Faraday's Law of Induction

$E_1$  is time dependent / varying voltage.

Lenz Law: Effect should oppose the cause.

- Constant flux machine.

- Whenever there is no load; the reduction in initial flux  $\phi_1$  due to  $\phi_2$ ; therefore, the source supplies a flux  $\phi_2'$  equal to  $\phi_2$  but opposite in direction.

$\therefore$  Therefore, the overall flux in the



transformer is  $\phi$

\* EMF equation of Transformer:

By Faraday's law; whenever there is a rate of change of flux linkage in a conductor; there is emf induced.

$$\text{Avg emf/turn} = E_{\text{avg/turn}} = \frac{d\phi}{dt} = \frac{\phi_m - 0}{\frac{1}{4f}}$$

$$K_f = \frac{\text{Rms value}}{\text{Avg value}} = 1.11$$

$$\text{Rms value} = E_{\text{rms/turn}} = 4f\phi_m(1.11)$$
$$E_{\text{rms/turn}} = 4.44f\phi_m$$

$$E_1 = 4.44f\phi_m N_1$$
$$E_2 = 4.44f\phi_m N_2$$

\* Transformer Ratio (K)  $= \frac{E_2}{E_1} = \frac{N_2}{N_1}$

$K > 1 \rightarrow$  Step-Up Transformer

$K < 1 \rightarrow$  Step-Down Transformer

$K = 1 \rightarrow$  Isolation Transformer