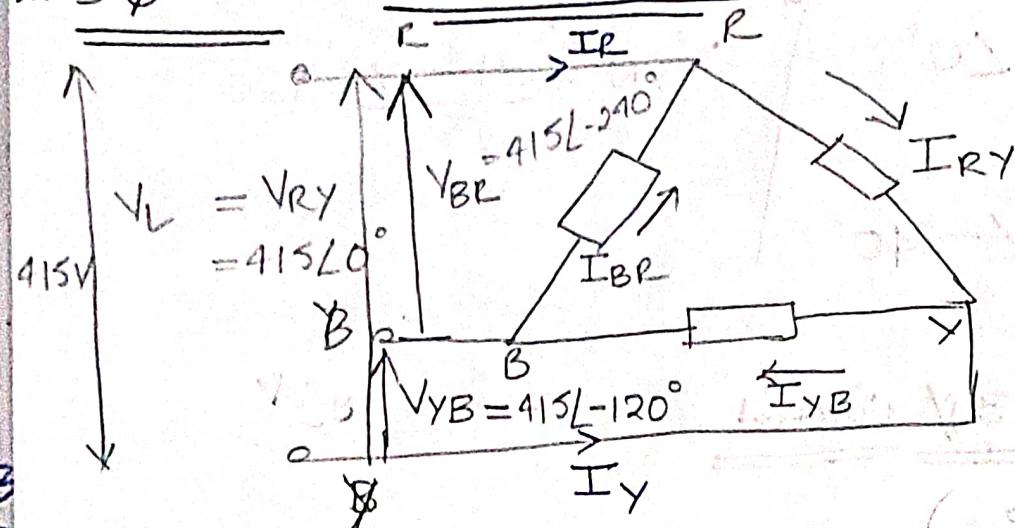


\* All phases will have equal voltages i.e.  
balanced circuit.

### \* 3Φ DELTA CONNECTION:



at R

$$I_R + I_{BR} \neq I_{RY}$$

$$I_R = 415 I_{RY} - I_{BR}$$

$$= \frac{415}{5} L - 30^\circ - \frac{415}{5} L - 240^\circ$$

$$= \sqrt{3} \times 83 \angle -30^\circ$$

29/07/2022

$$I_{RY} = 50A$$

### \* DC GENERATOR:


→ Generator: Mechanical Energy to Electrical energy.

\* Faraday's Law of electromagnetic induction: Whenever flux linkage is present emf is generated.


Conductor System: Armature

Field System: Flux system (field)

Electromagnets:

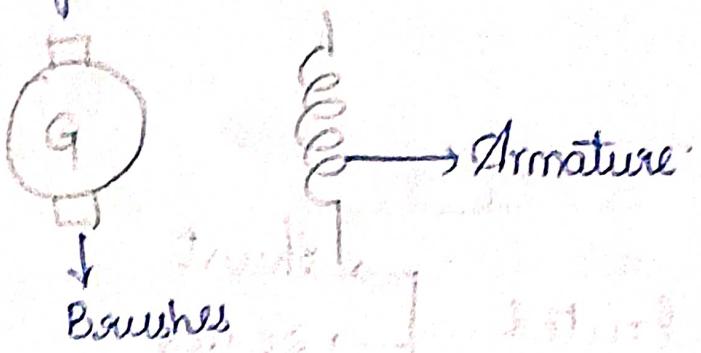

\* DC Generator: flux/field lines

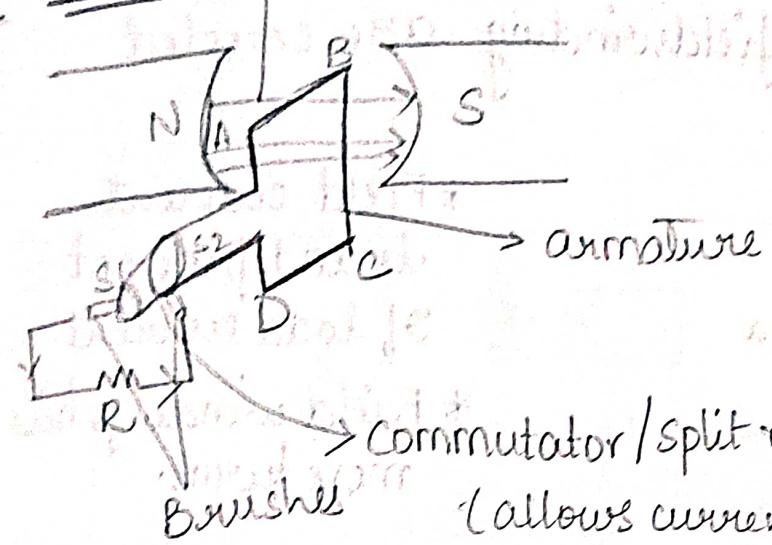

→ TYPES OF GENERATOR:

Separately excited


Self excited

Giving energy to field winding: exciting

→ Separately excited: Giving energy from separate source.

→ Self excited: Giving energy through self.

→ Separately Excited:

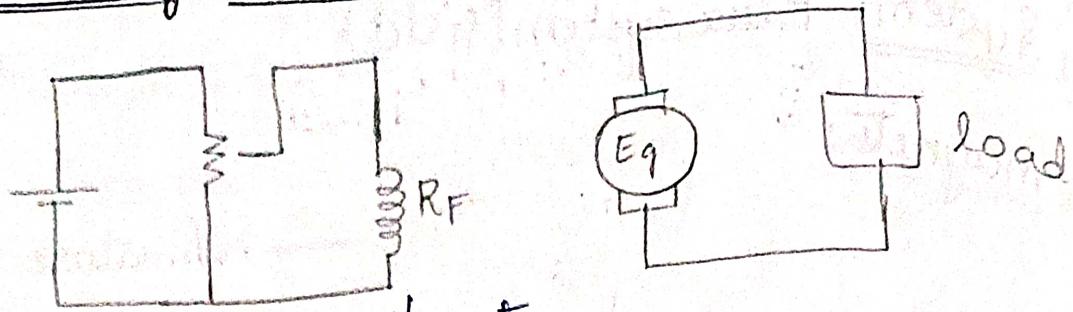


Self Excited:  
→ Shunt  
→ Series  
→ Compound

SHUNT: Armature & fieldwinding are coupled.




→ Shunt Generator:

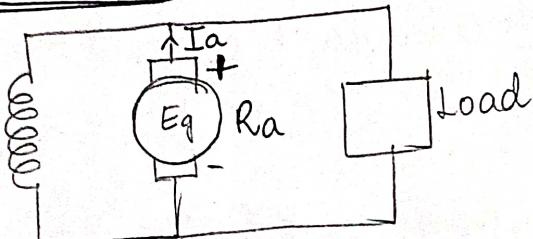


- \* Field current is independent of load current.
- \* Field winding has more turns.

→ Series Generator:

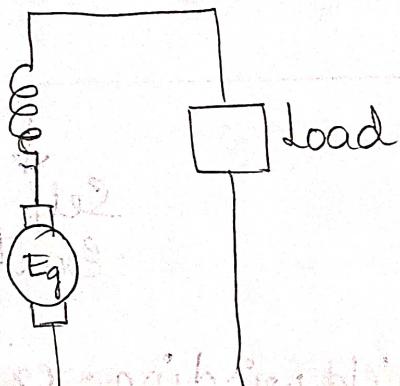


- \* Load will decide the DC current.
- \* Field winding has less turns of very thick wire.

→ Compound Generator:

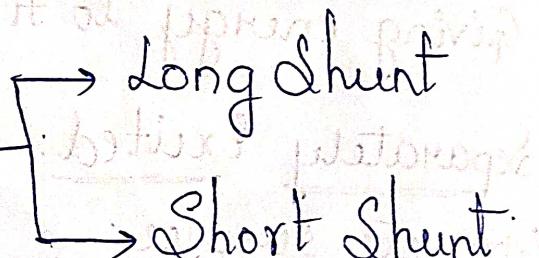


Combination of Series + Shunt = compound.

→ LONG SHUNT: Connecting series to shunt

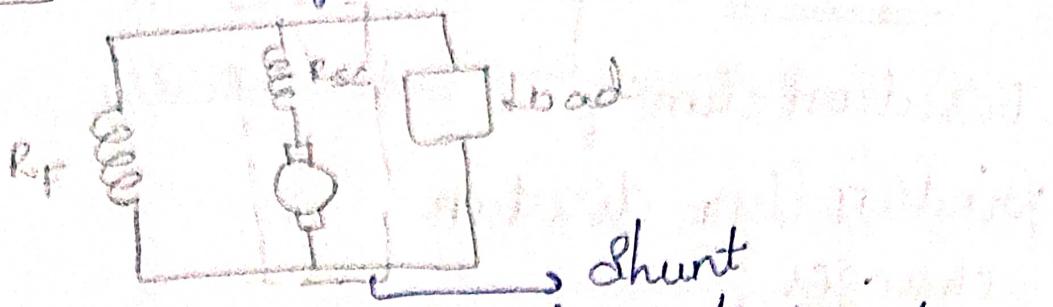


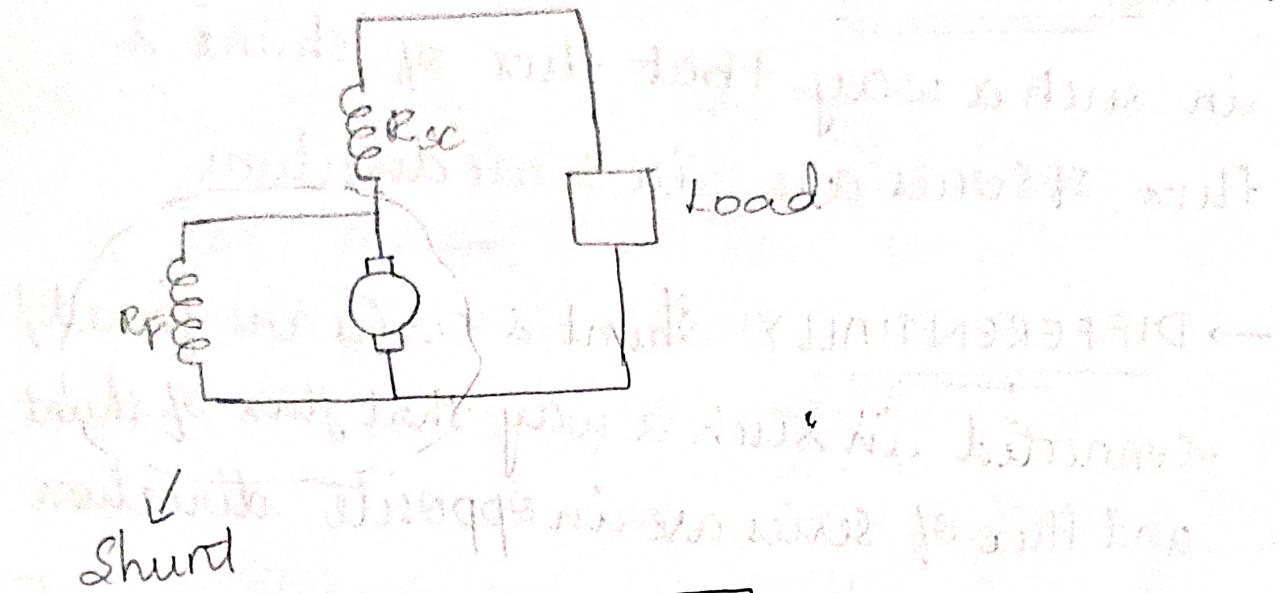→ SHORT SHUNT: Connecting shunt to series




## GENERATORS

Separately Excited

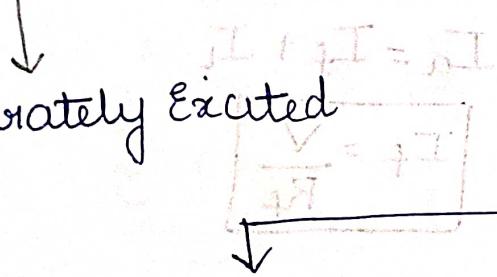

Series

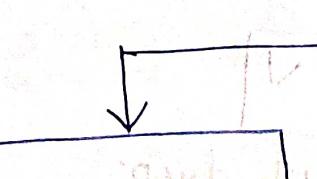

long  
Shunt

Self-Excited

Shunt

Compound


Short  
Shunt

Cumulatively


Differen-  
tially

\* Compound: → Cumulatively  
 → Differentially  
 based on dim. of  
 winding flux direction  
 changes

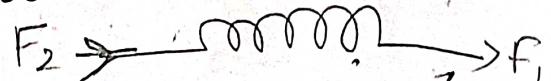→ CUMULATIVELY: Shunt & series are joined  
 in such a way that flux of shunt &  
 flux of series are in same direction




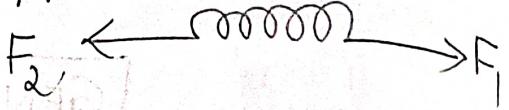→ DIFFERENTIALLY: Shunt & series are joined  
 connected in such a way that flux of shunt  
 and flux of series are in opposite direction



30/07/2022

### \* SHUNT GENERATOR:

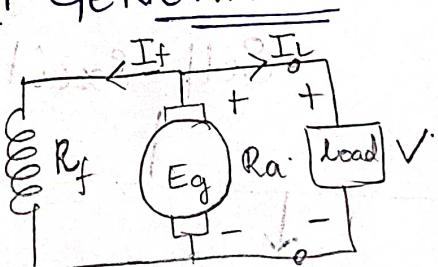

$$I_a = I_f + I_L$$


$$I_f = \frac{V}{R_f}$$

$$E_g - I_a R_a - V = 0$$

$$E_g - I_a R_a = V$$

↓  
Brush drop.

### \* SERIES GENERATOR:

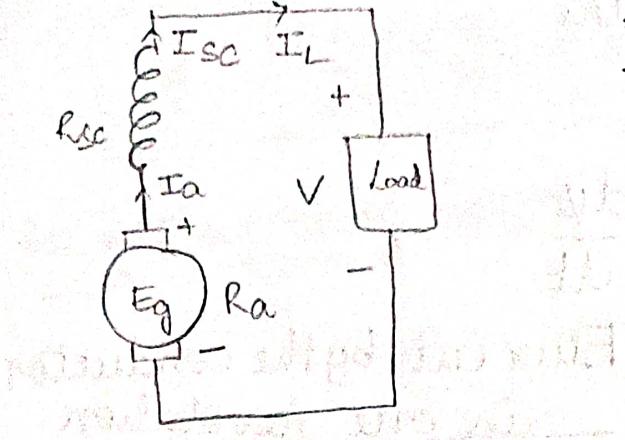


$$I_a = I_{sc} = I_L$$

$$E_g - I_a R_a - I_a R_{sc} - V = 0$$

$$V = E_g - I_a R_a - I_a R_{sc}$$

↓  
Brush  
drop.

\* Long Shunt:

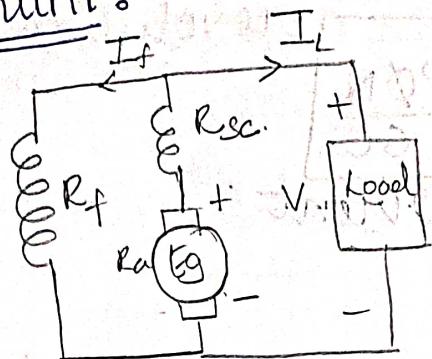

$$I_f = \frac{V}{R_f}$$

$$I_a = I_{sc}$$


$$I_a = I_f + I_L$$

$$E_g - I_a R_a - I_a R_{sc} - V = 0$$

$$V = E_g - I_a R_a - I_a R_{sc}$$

↓  
Brush  
drop.

\* Short Shunt:

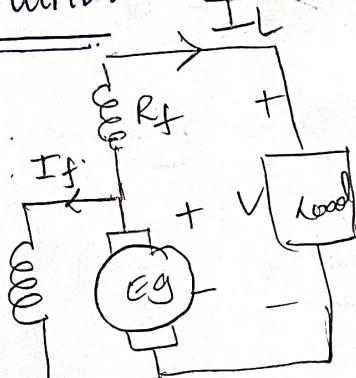

$$I_L = I_{sc}$$

$$E_g - I_a R_a - I_L R_{sc} - V = 0$$

$$V = E_g - I_a R_a - I_L R_{sc}$$

↓  
Brush  
drop.

\* EMF equation of a DC generator:

$\phi = \text{Flux/Pole in wb.}$

$p = \text{No. of poles}$

$z = \text{total no. of conductors in armature}$

$N = \text{Speed of armature in rpm.}$

$A = \text{No. of parallel paths}$

Emf of conductor /

$$= \frac{d\phi}{dt}$$

Emf induced

= Flux cut by the conductor  
in one revolution

Time taken for one revolution.

$$e = \frac{d\phi}{dt} = P\phi N / 60$$

No. of parallel paths  $\propto$  current

Lap windings:  $A = p \Rightarrow$  i.e. parallel paths depends on poles.

Wave windings:  $A = 2 \Rightarrow$  constant

Ex:

100 conductors

Lap:  $P = A = 4$

$\frac{100}{4} = 25$  conductors sets are connected in series to source

$V = 25V$  and all 4 paths are parallel

Wave:  $A = 2$

$\frac{100}{2} = 50$  conductors

$$V = 50V$$

$$E_g = \frac{P\phi N}{60} \times \frac{Z}{A} = \frac{\phi Z N}{60} \times \frac{P}{A}$$

for lap winding : ~~A=2~~

$$E_g = \frac{\phi Z N P}{60 A \cancel{2}}$$

for wave winding :  $A=2$

$$E_g = \frac{\phi Z N P}{120}$$

$$* P = 4 \quad A = 2, \quad Z = 720 \quad N = 1000 \text{ rev/min} \quad \phi = 20 \text{ mWb}$$

$$n = \frac{1000}{60} = \frac{50}{3}$$

$$\phi = 20 \times 10^{-3} \text{ wb}$$

$$E_g = \frac{\phi Z N P}{120}$$

$$= \frac{20 \times 10^{-3} \times 720 \times 1000 \times 4}{120}$$

$$= 480 \text{ V}$$

$$* P = 8 \quad Z = 12 \quad \phi = 50 \times 10^{-3} \quad E_g = 300 \text{ V}$$

option shows per slot 40 slots

$$\boxed{\text{total no. of conductors}} = 12 \times 40$$

$$= 480$$

$$E_g = \frac{\phi Z N P}{60 A}$$

$$500 = \frac{f\phi \times 10^{-3} \times 12 \times N \times 8}{60 \times 8}$$

$$N = ?$$

$$500 = \frac{f\phi \times 10^{-3} \times 480 \times N \times 8}{60 \times 8}$$


$$N = \frac{10^4}{8} = \frac{2500}{8} = 1250 \text{ rpm}$$

B  
E  
E

03/08/2022
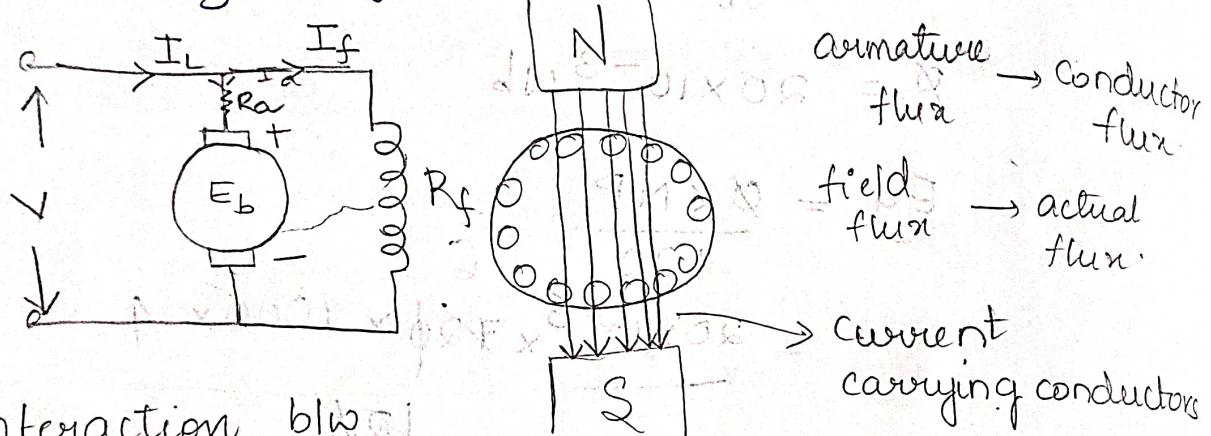
### \* DC MOTOR :

Whenever we place a current carrying conductor in a magnetic field; there is a force developed.



Interaction b/w armature & field flux.

○ → inward.

⊗ → outward.

$$I_L = I_a + I_f$$

$$V = I_a R_a + E_b \rightarrow \text{back emf: opposes the source voltage}$$

$$V - I_a R_a - E_b = 0$$

SHUNT MOTOR:

$$E_b = V - I_a R_a$$


$$I_a = \frac{V - E_b}{R_a}$$

$$E_b = \frac{\phi Z N}{60} \times \frac{P}{A}$$

If  $E_b = 0 ; N = 0$

$$I_a = \frac{V}{R_a}$$

\*  $E_b$  controls the current  $I_a$

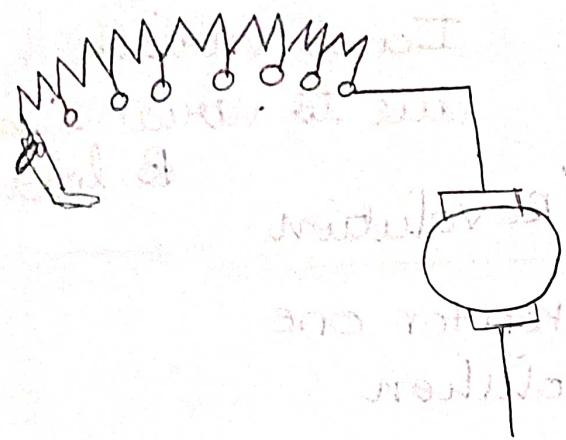

Starter is used to limit the starting current.


$$I_a = \frac{V - E_b}{R_a}$$

\* Also at the beginning  $E_b = 0$  ~~the starting current~~  
∴ current  $I_a$  is very high; to control this current; starter is used to avoid the damage to the circuit

\* We need to limit

$$I_a = \frac{V}{R_a}$$

### \* SERIES MOTOR:

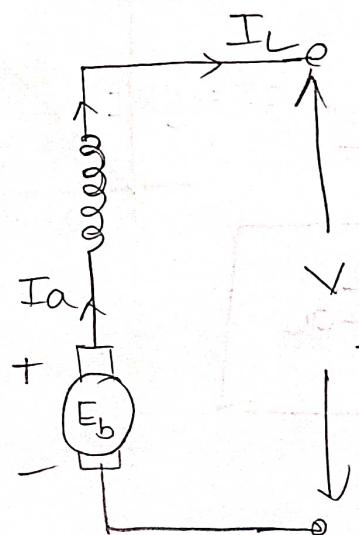

$$I_L = I_{SC} = I_a$$

$$E_b - I_a R_a - V = 0$$

$$E_b = I_a R_a + V$$

$$I_a = \frac{E_b - V}{R_a}$$

$$500 = \frac{5\phi \times 10^{-3} \times 12 \times N \times 8}{\phi \times 8}$$

$$500 = \frac{5\phi \times 10^{-3} \times 480 N \times 8}{\phi \times 8}$$



$$N = \frac{10^4}{8} = \frac{2500}{8} = 1250 \text{ rpm}$$

B  
E  
EE

03/08/2022
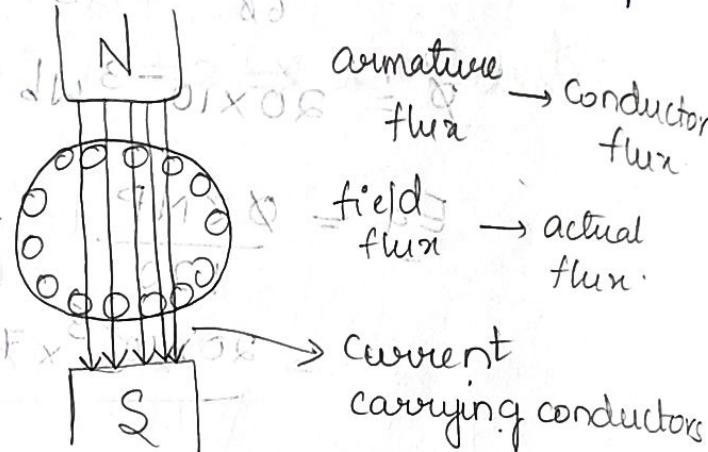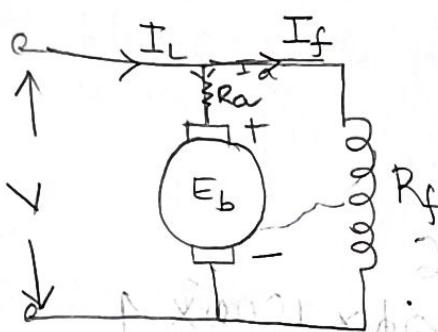
### \* DC MOTOR:

Whenever we place a current carrying conductor in a magnetic field; there is a force developed.



Interaction b/w armature & field flux.

$$I_L = I_a + I_f$$

$$V = I_a R_a + E_b \rightarrow \text{back emf: opposes the source voltage}$$

$$V - I_a R_a - E_b = 0$$

$$I_a = \frac{V - E_b}{R_a}$$

SHUNT MOTOR:


$$E_b = V - I_a R_a$$

$$E_b = \frac{\phi Z N}{60} \times \frac{P}{A}$$

If  $E_b = 0$ ;  $N = 0$

$$I_a = \frac{V}{R_a}$$

$E_b$  controls the current  $I_a$

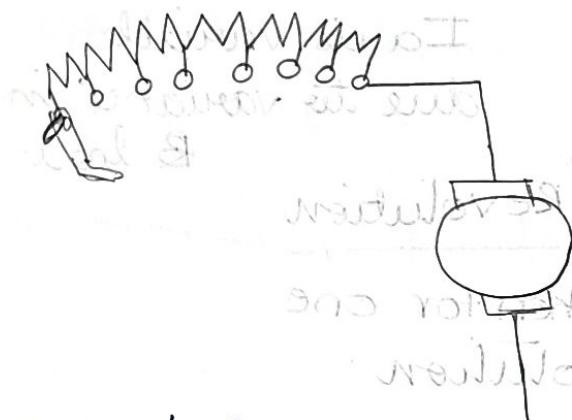


Starter is used to limit the starting current

$$I_a = \frac{V - E_b}{R_a}$$

- \* Also at the beginning  $E_b = 0$ . current  $I_a$  is very high; to control this current; starter is used
- \* We need to limit the starting current to avoid the damage to the circuit

### SERIES MOTOR:

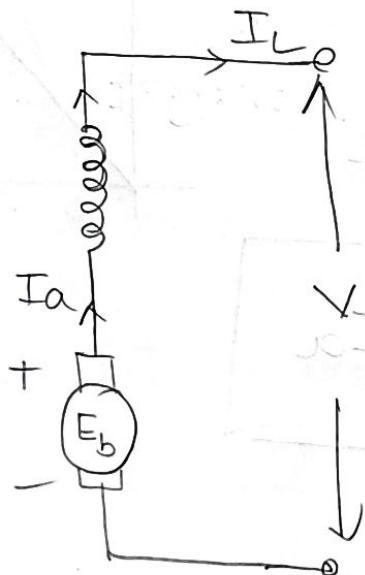

$$I_L = I_{SC} = I_a$$


$$E_b - I_a R_a - V = 0$$

$$E_b = I_a R_a + V$$

$$I_a = \frac{E_b - V}{R_a}$$

06/08/2022

## \* TORQUE IN DC MOTOR:

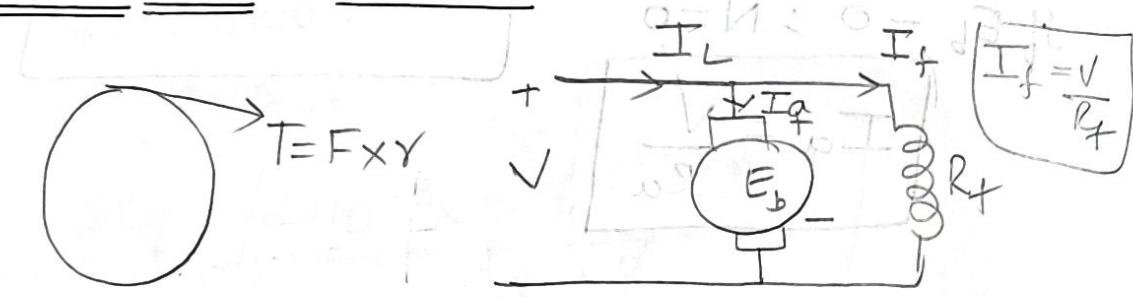

$P_m = E_b I_a$   
base & projected  
atmosphere onto similar st

$I_a$  is variable  
due to variance in  
B. load.

Power = Work done / Revolution

$$\frac{V - E_b}{R_f} = \frac{V}{R_f} \text{ Time taken for one revolution}$$

similar to base rev

$$\text{Time taken for one revolution} = \frac{(F_r \times 2\pi r) \times 1}{(F_r) \frac{2\pi N}{60}} = \frac{2\pi N}{60} \text{ sec.} \quad \text{split. due to load}$$

$$= F_r \cdot \frac{2\pi r}{60} = (F_r) \omega$$


$$P = \frac{V}{R_f} \text{ input power}$$

$$E_b I_a = T \omega$$

$$\frac{P \phi N}{60} \times \frac{\pi}{A} I_a = T \cdot \frac{2\pi N}{60}$$

$$T = \frac{P \phi \pi I_a}{2\pi A}$$

$$V = V - \theta \phi I_a$$

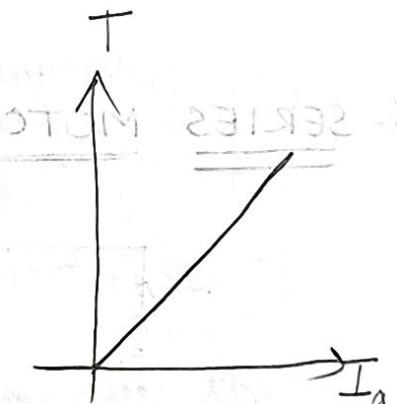

$$T = \frac{Z P}{2\pi A} \phi I_a$$


$T \propto I_a$

$$E_b = \frac{\phi Z N}{60} \times \frac{P}{A}$$

$\phi$  varies with  $I_f$   
 $N \rightarrow$  varies.

$$N \propto \frac{E_b}{\phi}$$


$$E_b = V - I_a R_a$$

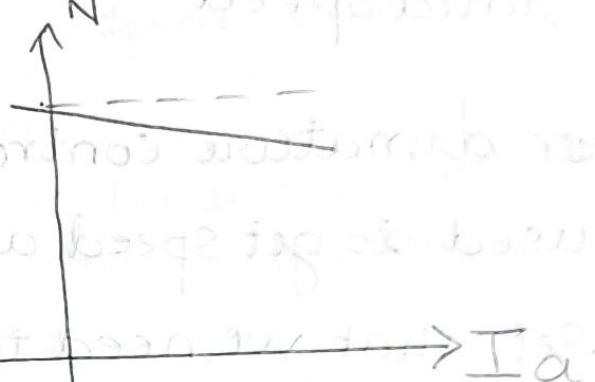

\* Speed control of DC shunt motor. (or)  
Separately excited DC Motor.

- We need start the circuit with a minimum speed.

$$N \propto \frac{E_b}{\phi}$$

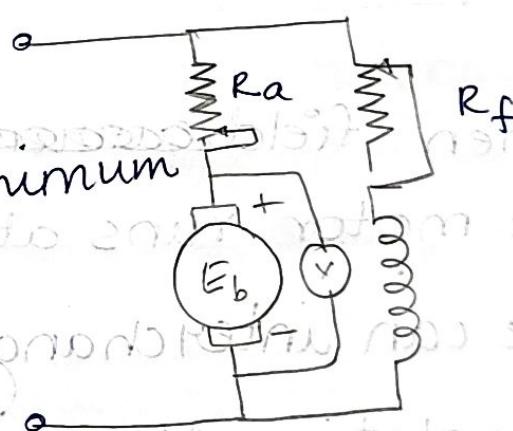

$V_a$  can be varied with armature resistance.

$R_a$  at max and  $R_f$  is made to start the circuit with min speed.

→ When the rated voltage and field current are applied; we get the rated speed.

~~For~~ Armature control method cannot be used to get speed above rated value. To get that we need to increase the resistance over rated value; which will damage the circuit.

Field control method cannot be used to get speed below rated value. To get that we need to increase the resistance over rated value.

\* When field ~~current~~ windings are open, the motor runs at a very high speed.


\* We can interchange the direction of the rotation of motor by either interchanging the armature (or) field polarities.

~~Exodus~~  
t the

10/08/2022


$$* V = 250V$$
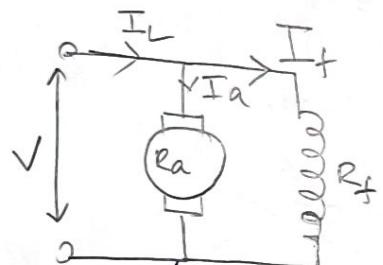
$$I_L = 80A \quad R_a = 0.12\Omega \quad R_f = 100\Omega$$



$$I_f = \frac{V}{R_f} = 2.5A$$

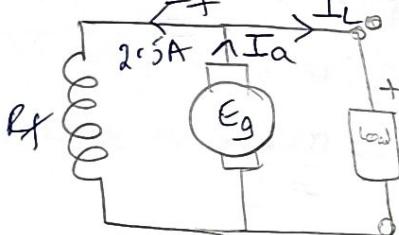Speed as generator  
Speed as motor. = ?  
I\_a = 77.5A Flux in a shunt  
motor is constant  
due to constant V & I



$$I_a = 80A \quad \text{Motor: } N \propto E_b + 2.5 \\ = 82.5A \quad \text{Generator: } N_g \propto E_g$$

to get  
we  
calculated

$$E_b = V - I_a R_a \\ = 250 - 77.5 \times 0.12 \\ = 240.7V$$

$$E_g = V + I_a R_a \\ = 250 + 82.5 \times 0.12 \\ = 259.9V$$

$$\frac{N_g}{N_b} = \frac{259.9}{240.7} = \underline{\underline{1.08}}$$

Open: \*  $V = 200V \quad R_a = 0.4\Omega \quad I_a = 2A \rightarrow$  no load current

$I_a = 50A \quad ? \quad N = 1200 \text{ rpm}$  → Loaded conditions.

$$E_o = V - I_a R_a = 200 - 2 \times 0.4 \\ = 200 - 0.8 \\ = 199.2V$$

$$E_i = V - I_{a1} R_a = 200 - 50 \times 0.4 \\ = 200 - 20 = 180V$$

$$N \propto \frac{E_b}{\phi}$$

10/08/20

$$\frac{N_1}{N_0} = \frac{E_d}{E_0}$$

$$N_0 = \frac{1200 \times 199.2}{180}$$

$$= 1328 \text{ rpm}$$

(to reduce no. of poles)  
220 volt at 50 Hz

$$220 \text{ volt } 50 \text{ Hz } 2 \times 10^6 = I$$

$$220 \text{ volt } 50 \text{ Hz } A = 2.3$$

$$220 + V = E$$

$$E = V - I R_o$$

$$V_p =$$

$$220 + I R_o = E$$

$$\frac{80.1}{80.1} = \frac{R_o P_{loss}}{F \cdot 0.48} = \frac{R_o}{M}$$

Due to

other  
coil

Princ

$E_1$  is

length

- Con


- Whe  
in

the  
 $\Phi_2$  b

∴ The

10/08/2022

# TRANSFORMER

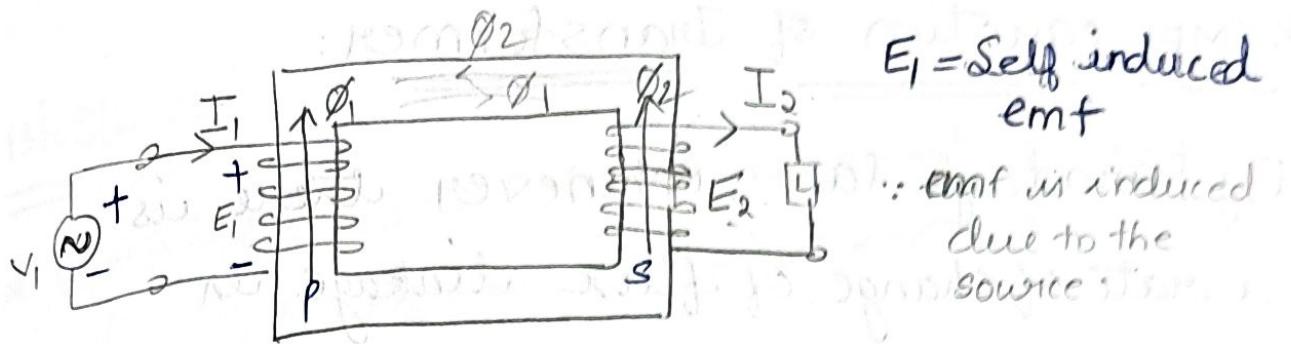

The transformer just step up or down the primary voltage; but total power on either side remains same:

$$V_1 I_1 = V_2 I_2$$

Due to the flux developed in primary coil there is a flux developed in secondary coil:

$$E_2 = \text{Mutually induced emf}$$

$H.I = \text{Electromagnetic force}$

Principle: Faraday's Law of Induction

$E_1$  is time dependent / varying voltage

Lenz Law: Effect should oppose the cause.

- Constant flux machine.

- Whenever there is no load; the reduction in initial flux  $\Phi_1$  due to  $\Phi_2$ ; therefore, the source supplies a flux  $\Phi'_2$  equal to  $\Phi_2$  but opposite in direction.

$\therefore$  Therefore, the overall flux in the

Transformer is  $\emptyset$ , ~~MATERIAL~~

### \* EMF equation of Transformer:

By Faraday's law; whenever there is a rate of change of flux linkage in a conductor; there is emf induced.

$$\text{Avg emf/turn} = E_{\text{avg/turn}} = \frac{d\phi}{dt}$$

$$\text{No flux linkage in leakage} = \phi_m = 0$$

$$E_{\text{avg/turn}} = 4f\phi_m$$

$$K_f = \frac{\text{Rms value}}{\text{Avg value}} = 1.11$$

$$\text{Rms value} = E_{\text{rms/turn}} = 4f\phi_m(1.11)$$

$$E_{\text{rms/turn}} = 4.44 f\phi_m$$

$$E_1 = 4.44 f\phi_m N_1$$

$$E_2 = 4.44 f\phi_m N_2$$

$$* \text{Transformer Ratio (K)} = \frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$K > 1 \rightarrow$  Step-Up Transformer

$K < 1 \rightarrow$  Step-Down Transformer

$K=1 \rightarrow$  Isolation Transformer.

13/08/2022

$$* E_1 = 3300V \quad E_2 = 25V \quad A = 125\text{cm}^2 \quad f = 50\text{Hz}$$

~~area~~  $= 125 \times 10^{-4}\text{m}^2$

$$\begin{aligned} B_m &= \frac{\phi_m}{A} = \frac{E_2}{4.44fN_2} \\ &= \frac{250}{4.44 \times 50 \times 70 \times 125 \times 10^{-4}} \\ &= 1.289\text{T} \end{aligned}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$N_1 = \frac{3300}{250} \times 70$$

↓  
1

$$= 924$$

$$\left[ \frac{2N}{1N} = \frac{E_1}{E_2} = \frac{3}{1} \right] *$$

$$* N_1 = 800 \text{ primary turns} \quad V_{ac} = E_1 = 100V$$

$$E_2 = ? \text{ secondary voltage}$$

$$\frac{N_1}{N_2} = \frac{E_1}{E_2} \Rightarrow E_2 = \frac{E_1 N_2}{N_1}$$

$$= \frac{100 \times 200}{800} = 25V$$

$$\text{Volts per turn} = \frac{V_1}{N_1} = \frac{100}{800} = 0.125$$


$$\text{Volts per turn} = \frac{\sqrt{2}}{N_2} = 0.125$$

### \* Ideal transformer:

Properties:

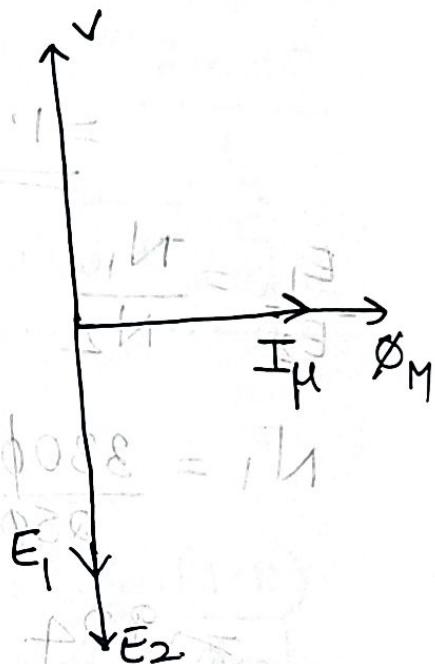- 1)  $\mu = \infty$ : ability to produce flux with a min MMF (Magnetomotive force)
- 2) Copper loss ( $I^2 R$ ) is neglected.
- 3)  $R_1 = 0; R_2 = 0 \Rightarrow$  purely inductive.
- 4) No leakage flux
- 5) core loss = 0.

$$* \boxed{\frac{E_2}{E_1} = \frac{I_1}{I_2} = \frac{N_2}{N_1}}$$



17/08/2022

### \* Magnetising & de-magnetising

\* Magnetic reversal : magnetising & demagnetising

demagnetising : Heat loss developed due to core mechanical vibrations

is called HYSTERESIS LOSS.


If the area of the loop is max. losses are more and vice versa

By using appropriate material we

can reduce the hysteresis loss.

$H \rightarrow$  Magnetic field density

$B \rightarrow$  Magnetic flux density

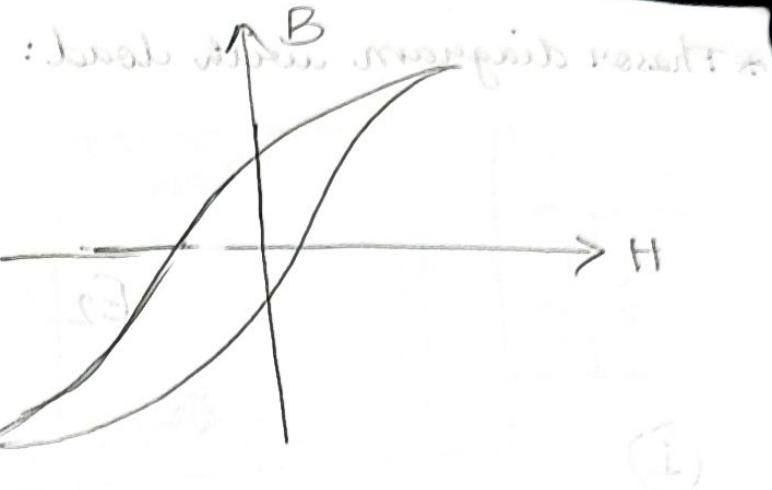

### EDDY CURRENT LOSSES:

- Heat developed due to the eddy current developed in the core ( $\because$  closed circuit) will cause eddy current losses.

$$\Rightarrow I^2 R \text{ loss}$$


- Losses can be reduced using ~~co~~ laminated core.

\* Ideal transformer with no load but having core loss:

### Phasor diagram:

$$I_o = \sqrt{I_w^2 + I_m^2}$$


= No load ~~core loss~~ current.

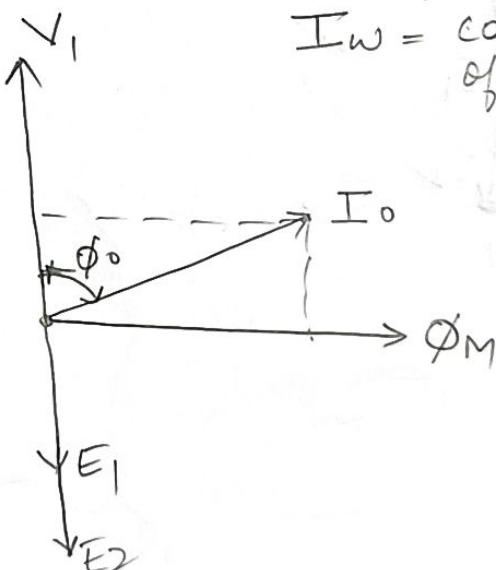

$I_\mu$  = Magnetising loss component of current

$I_w$  = core loss component of current

# \*Phasor diagram with load:

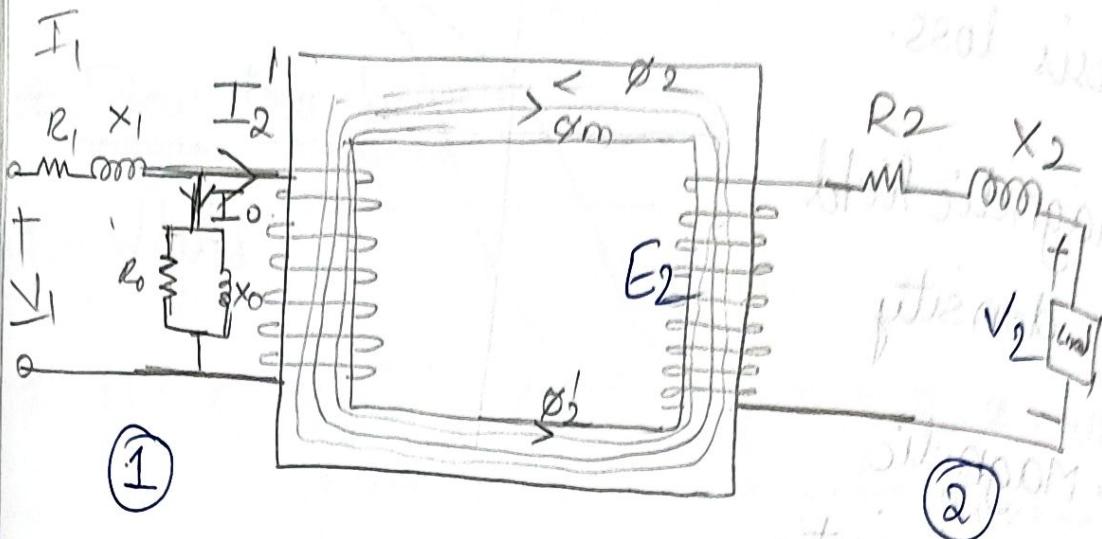

Flux linking in the same coil: flux leakage.

①

$$V_1 = E_1 + I_1(R + jX_1)$$

~~V1 lags V~~

$$\because V_1 = \text{source } I_1 +$$

$$V_2 \text{ lags } E_2$$

~~E2 lags V2~~

$$E_2 = \text{source}$$

